
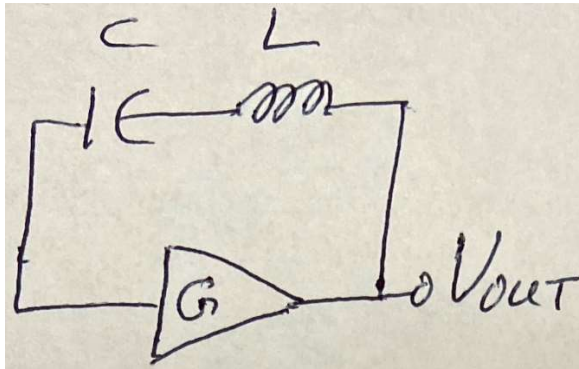


Capacitive Sensing

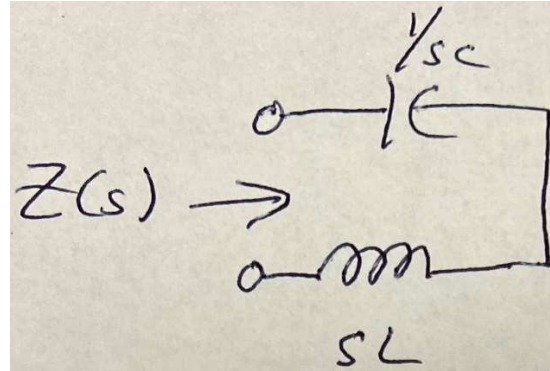1. Capacitor Interface Circuitry: LC Oscillators



and



Assume that $G = 1|0^\circ$.

G is the amplifier gain.

$$Z(s) = \frac{1}{sC} + sL \rightarrow Z(j\omega) = \frac{-j}{\omega C} + j\omega L$$

At $\omega = \frac{1}{\sqrt{LC}} \rightarrow Z(j\omega) = 0|0^\circ$, i.e. a short, allowing the circuit to oscillate at this frequency.

So, $\omega_n = \frac{1}{\sqrt{LC}}$: assume L is fixed and C is our sensor.


The output, V_{OUT} , is a sinusoidal signal where $f \propto \frac{1}{\sqrt{C}}$: the frequency is a nonlinear function of $C(t)$ or $C(x)$.

This is the common operation of LC oscillators.


2. Capacitor Interface Circuitry: Switched-Capacitor Circuits

Switching a capacitor on and off can make it behave like a resistor, under certain conditions.

Consider:

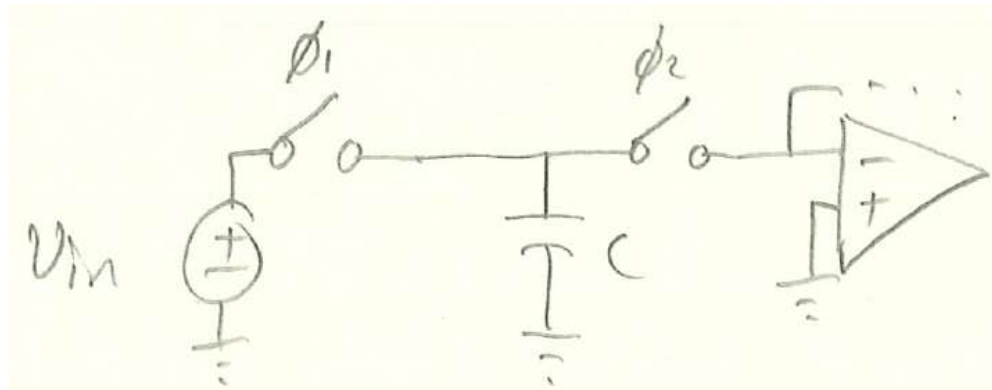

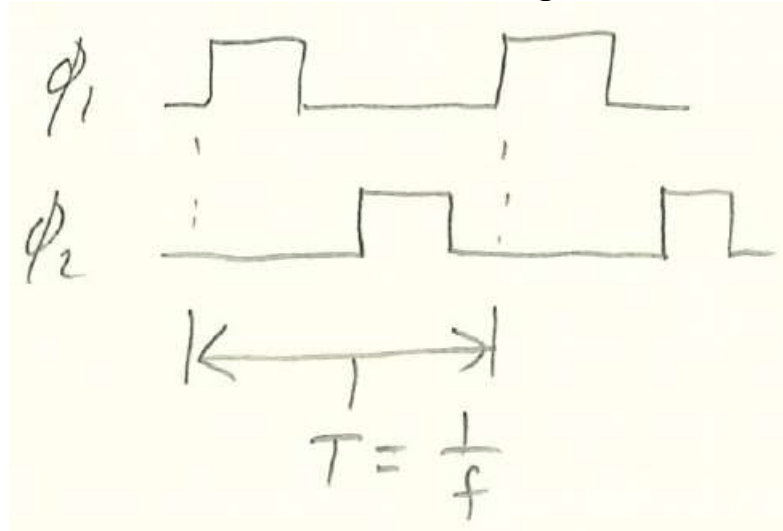
ϕ_1 and ϕ_2 are clocked waveforms that turn on and off the two switches: “1” = closed or a short, “0” = open or infinite resistance:



Both switches can be off at the same time, but never both on at the same time. They both operate at the same frequency, f , with period $T = 1/f$.


The rest of the op amp circuit (feedback network, etc.) is not shown. The ϕ_2 switch is connected to a virtual ground through the op amp circuit.

When $\phi_1 = 1$ and $\phi_2 = 0$:

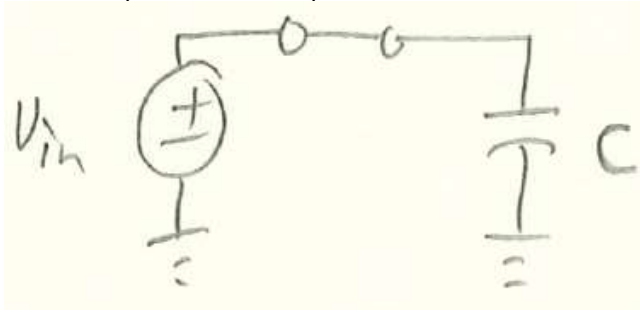

Charge, q , is stored on C : $q = Cv_{in}$.

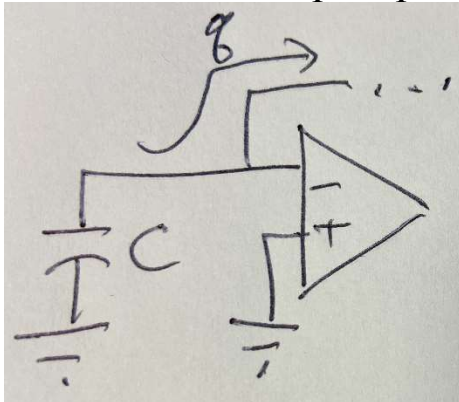Next, when $\phi_1 = 0$ and $\phi_2 = 1$, q is transferred through the virtual ground to the rest of the op amp circuit, fully discharging C :



For a given T , q charge moves through the circuit. Therefore, we can model this as:

$$i = \frac{dq}{dt} \approx \frac{\Delta q}{\Delta t} = \frac{q}{T} = \frac{Cv_{in}}{T} = Cf v_{in}$$

The current, i , is proportional to v_{in} . Therefore, we can define an equivalent resistance, R_{eq} :

$$R_{eq} = \frac{v_{in}}{i} = \frac{1}{Cf}$$

This is called a switched-capacitor resistor.

It is applicable to low-pass systems where $f \gg$ system bandwidth.

A LPF can be added at the circuit output to attenuate switching noise.


It can be used as a frequency tunable resistor.

In CMOS analog ICs, it's often used for resistors because on-chip capacitors have much tighter fabrication tolerances than on-chip resistors, particularly for audio signal processing applications:


For a 20 kHz BW \rightarrow use $f \sim 200$ kHz

MOSFETS (single or paired) are typically used as the switches.

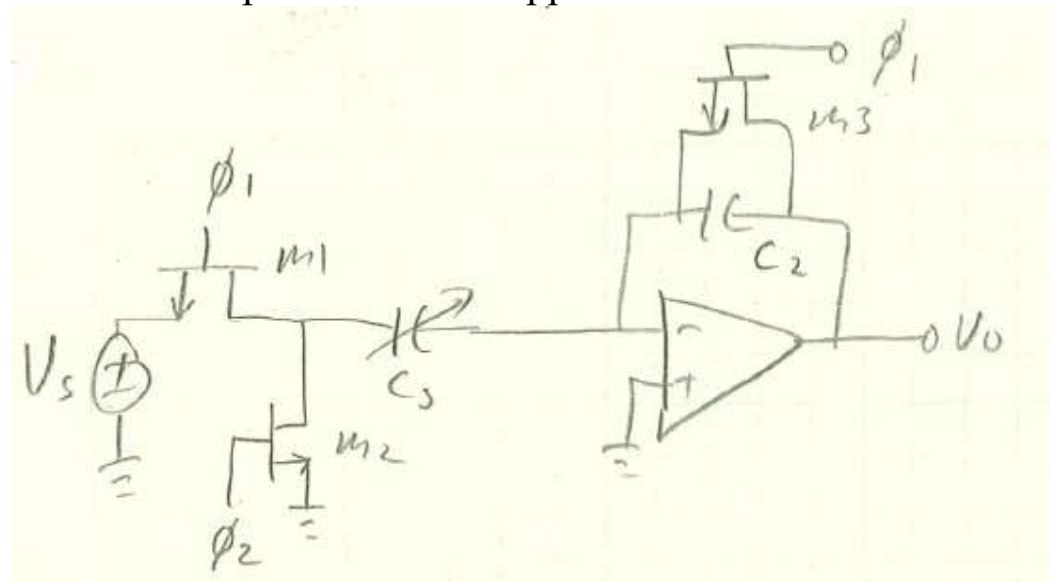Consider a capacitive sensor application:




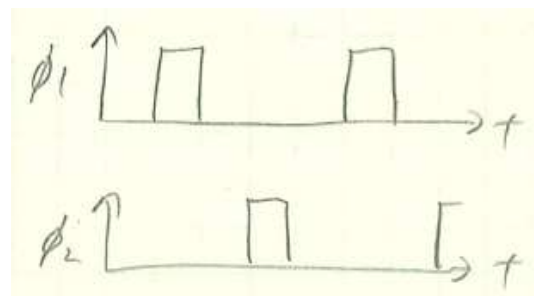M_1 , M_2 , and M_3 are MOSFET analog switches. C_s is the sensor.




non-overlapping clock waveforms

When $\phi_1 = 1$ and $\phi_2 = 0$:

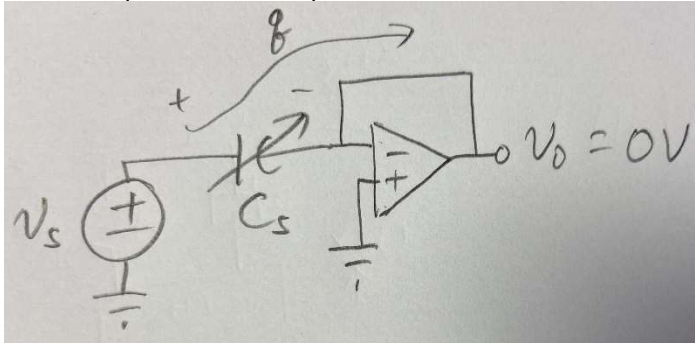

Charge $q = C_s v_s$ is stored on C_s .

Then when $\phi_1 = 0$ and $\phi_2 = 1$:

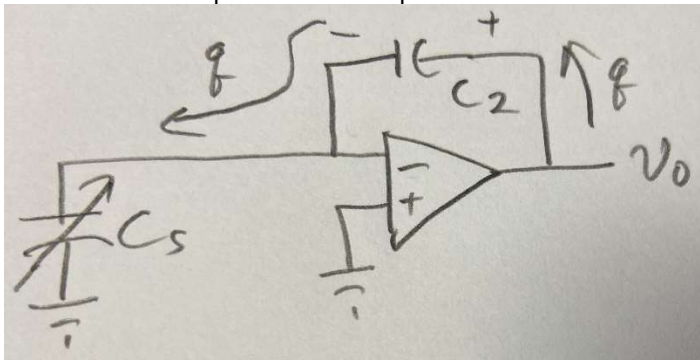

Charge q flows out of C_s to ground, requiring q to flow through C_2 :

$$v_o = \frac{q}{C_2} = \frac{C_s v_s}{C_2} \rightarrow \phi_2 = 1 \text{ and } \phi_1 = 0. \text{ However, } v_o = 0 \text{ V otherwise.}$$

Assuming that ϕ_2 has a 50% duty cycle, averaged over time: $v_o \approx \frac{C_s v_s}{2C_2}$.


But, if you only measure v_o when $\phi_2 = 1$, then use $v_o = \frac{C_s v_s}{C_2}$.

With fixed v_s and C_2 , C_s is converted to a voltage, v_o , proportional to it.


Therefore, this circuit is called a charge amplifier, and has a gain of v_s/C_2 .

3. Capacitor Interface Circuitry: Phase or State Delay Circuits

Consider this circuit:

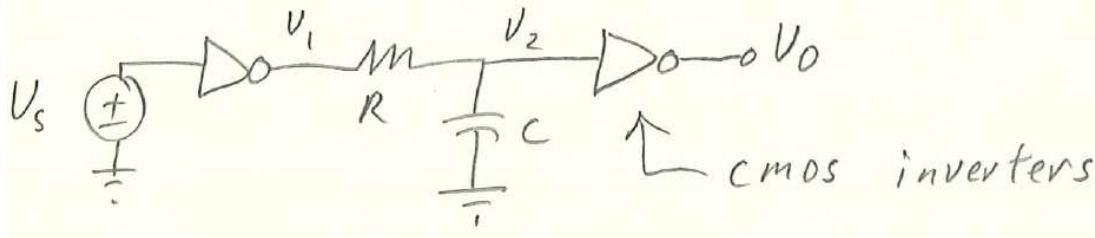

Let V_s be a pulse train:

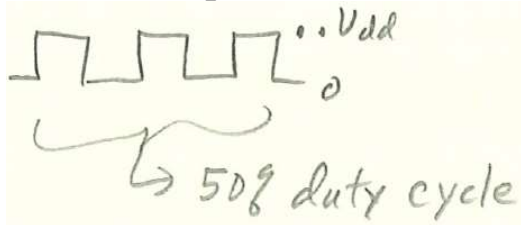

$$V_{tr} = \frac{V_{dd}}{2} \rightarrow \text{inverter trip voltage}$$

$$V_2 = V_1(1 - e^{-t/RC})$$

Solve for $t = f(RC)$ for $V_1 = V_{dd}$ and $V_2 = V_{tr}$

$$\text{Therefore, } \frac{V_{dd}}{2} = V_{dd}(1 - e^{-t/RC})$$

$$\text{Or: } \frac{1}{2} = 1 - e^{-t/RC}$$

$$\text{Or: } e^{-t/RC} = \frac{1}{2}$$


$$\text{Leading to: } t = -RC \ln(0.5) = 0.693RC$$

The last inverter squares up the signal out of the RC subcircuit.

Therefore, the pulse train is delayed $0.693RC$ s through the RC subcircuit.

Note: this assumes that C fully charges to V_{dd} or discharges to 0 V before the next state change \rightarrow otherwise the delay is not a linear function of C.

Let's expand the circuit to this:

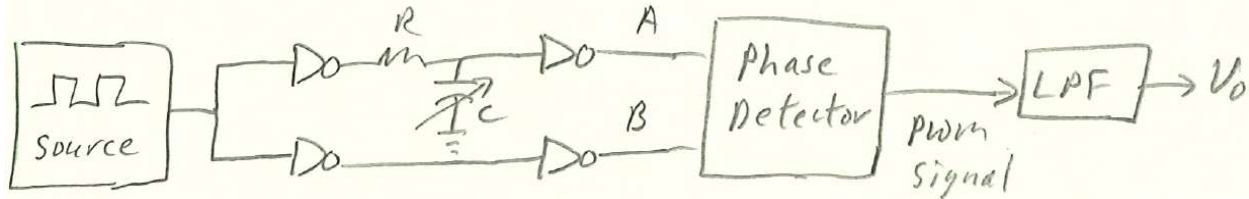

Now there are two parallel inverter paths, one with RC_s and one without.

RC_s delays signal A compared to signal B.

The Phase Detector compares the logical signals, A and B, and produces a pulse width modulated (PWM) output signal.

Consider the Exclusive OR (EXOR) gate:

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

} only high when $A \neq B$

Therefore, pulse width (and duty cycle) is proportional to how out of phase A and B are (0° to 180°).


In phase: $Q = 0$

180° out of phase: $Q = 1$

The average or DC value of the PWM signal is proportional to the PWM duty cycle, which is proportional to C_s . The low pass filter (LPF) produces V_o , which primarily consists of this DC term, which is proportional to C_s .

To optimize this capacitive sensor interface circuit:

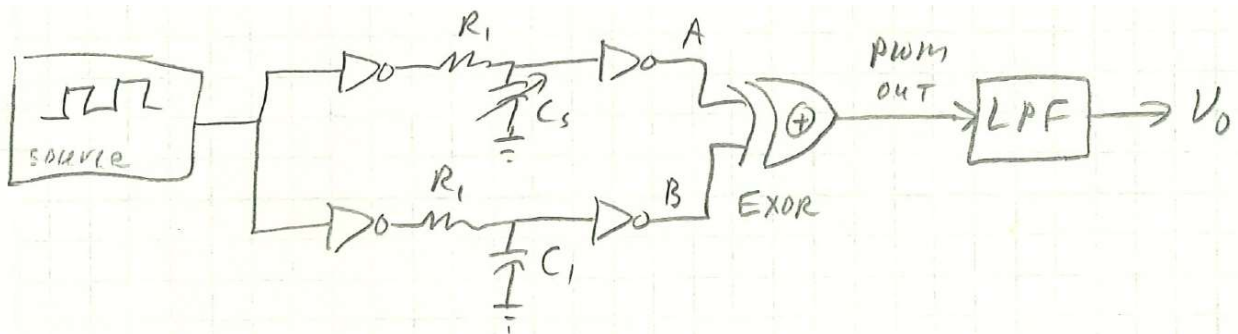
- (1) For the EXOR phase detector: we do not want a phase difference near 0° or 180° to avoid phase jitter issues.
- (2) To avoid excessive nonlinear distortion, limit the phase delay range from the sensor to 45° , and place that about 90° (67.5° to 112.5°).
- (3) Add a fixed RC delay stage in the lower inverter chain to achieve this:



Signal A's minimum delay differs from signal B by 67.5° , and signal A's maximum delay differs from signal B by 112.5° . One of the two resistors can be potentiometer so that the interface circuit can be tuned.

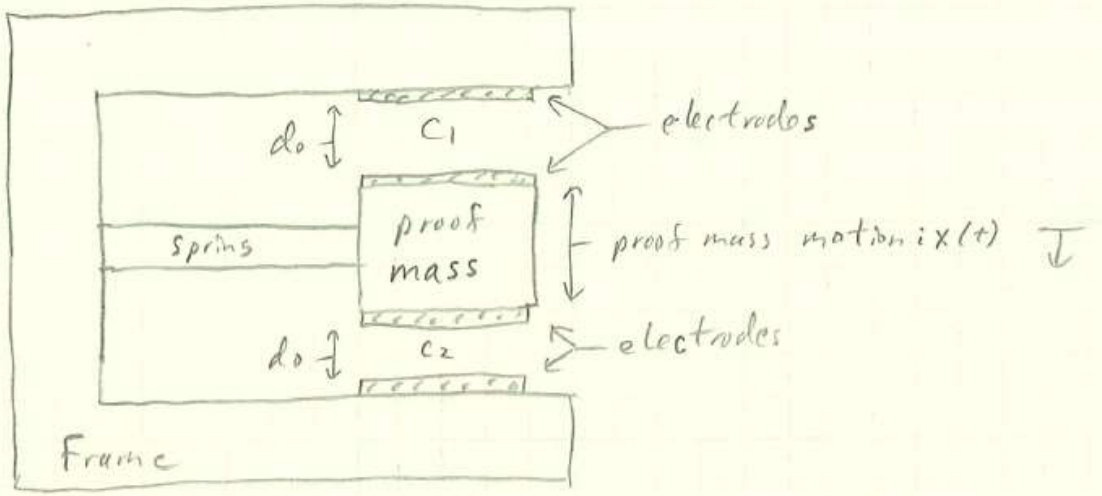
4. Capacitor Interface Circuitry: AC Voltage Division

Sometimes the MEMS device is designed to produce a differential capacitance:




$$C_1 = \frac{\epsilon_0 \epsilon_r A}{d_1} = \frac{\epsilon_0 \epsilon_r A}{d_0 + x(t)} \quad \text{and} \quad C_2 = \frac{\epsilon_0 \epsilon_r A}{d_2} = \frac{\epsilon_0 \epsilon_r A}{d_0 - x(t)}$$

The circuit model is:

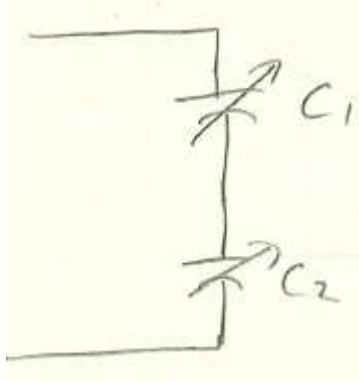

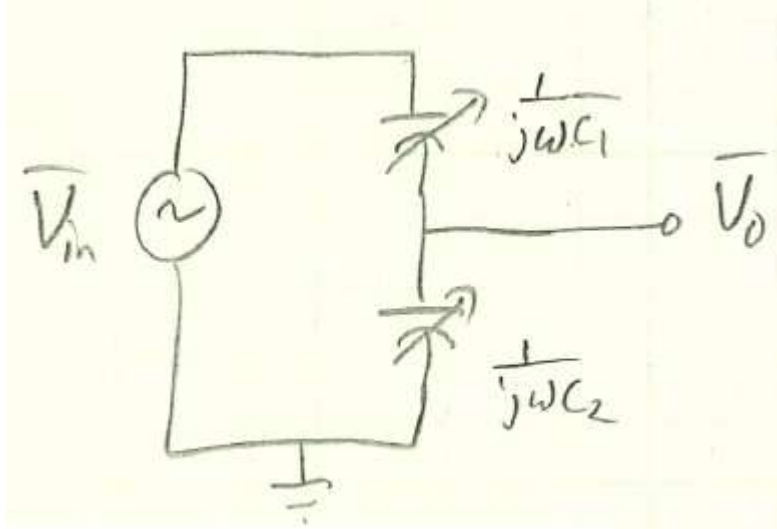Consider the application of an AC voltage, \bar{V}_{in} :



$$\frac{\bar{V}_o}{\bar{V}_{in}} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{\frac{1}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1}{C_2 + C_1} \rightarrow \text{An AC voltage divider}$$

$$\text{Let } \bar{V}_{in} = V_1 \sin(\omega t)$$

$$\text{Therefore: } \bar{V}_o = V_1 \sin(\omega t) \left[\frac{C_1}{C_2 + C_1} \right] \rightarrow \text{select } \omega \gg \omega_{MEMS}$$

$$\begin{aligned} \frac{C_1}{C_2 + C_1} &= \frac{\frac{\epsilon_0 \epsilon_r A}{d_o + x(t)}}{\frac{\epsilon_0 \epsilon_r A}{d_o - x(t)} + \frac{\epsilon_0 \epsilon_r A}{d_o + x(t)}} \\ &= \frac{\frac{1}{d_o + x(t)}}{\frac{1}{d_o - x(t)} + \frac{1}{d_o + x(t)}} \\ &= \frac{d_o - x(t)}{d_o + x(t) + d_o - x(t)} \\ &= \frac{d_o - x(t)}{2d_o} \\ &= 0.5 \left(1 - \frac{x(t)}{d_o} \right) \end{aligned}$$

$$\therefore \bar{V}_o(t) = V_1 \sin(\omega t) \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right]$$


The amplitude of $\bar{V}_o(t)$ is a linear function of $x(t)$.

So, how do we recover the amplitude of $\bar{V}_o(t)$, $V_1 \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right]$?

It is desirable to produce a DC voltage proportional to $V_1 \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right]$.

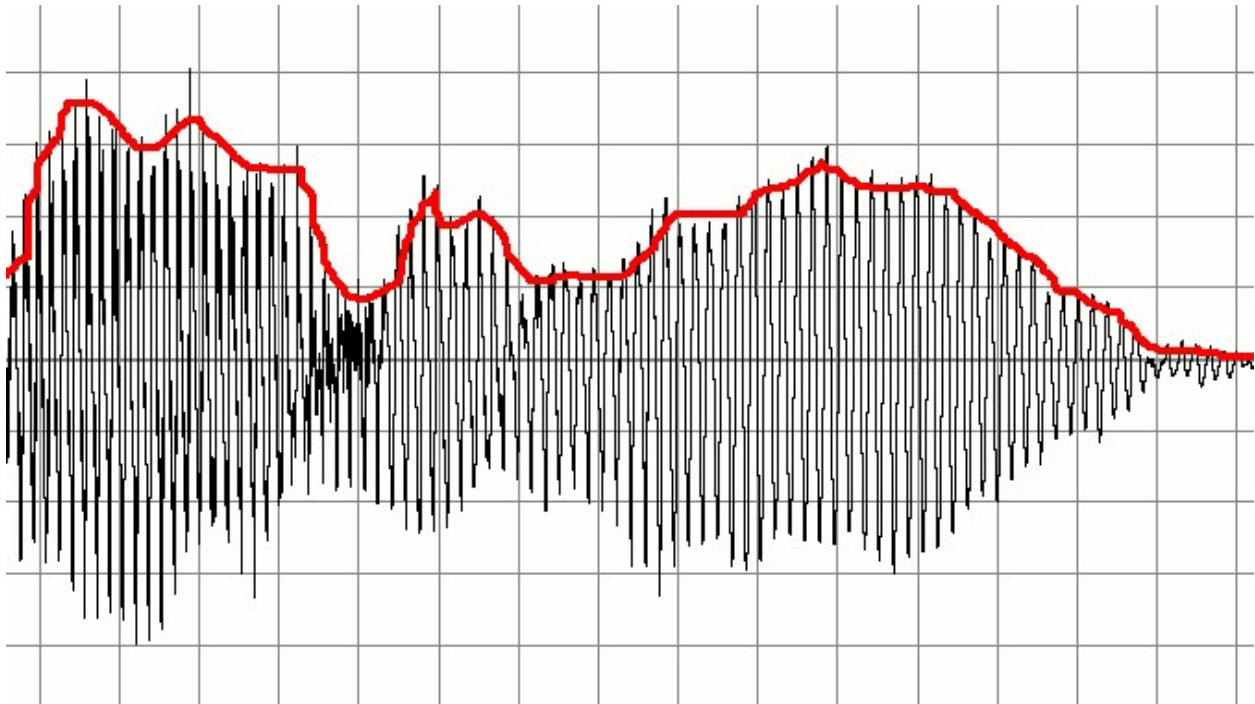a. Envelope Detection


An envelope detector is a diode circuit that recovers the demodulated envelope of an AM modulated signal.




Courtesy: https://en.wikipedia.org/wiki/Envelope_detector#/media/File:C_Envelope_follower.png

The black waveform is the AM signal. The red waveform is the envelope or message we wish to recover.

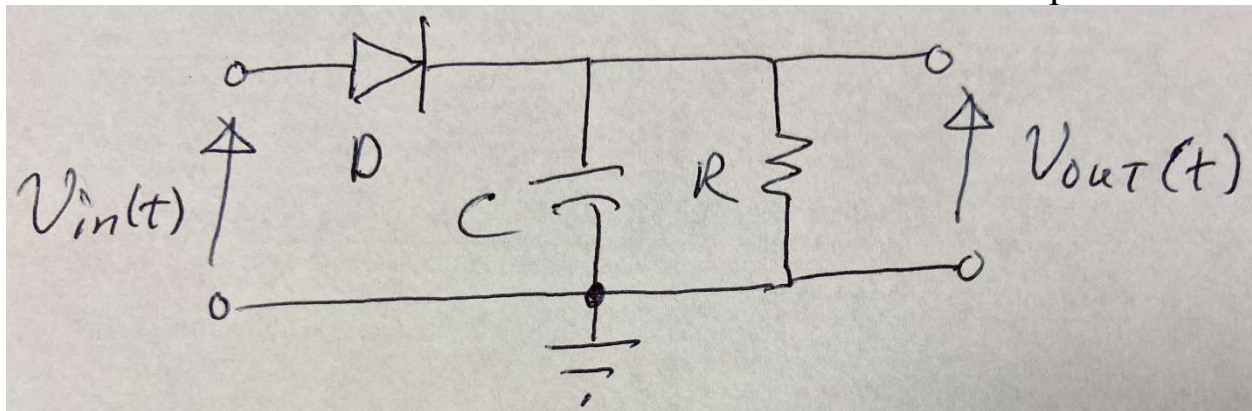A diode rectifier with a RC LPF circuit can be used to accomplish this:



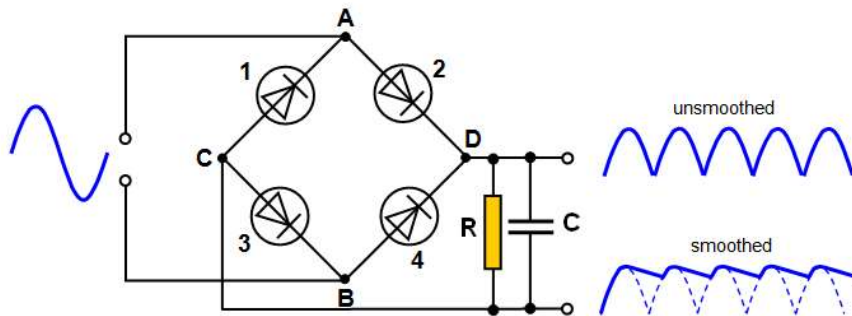More advanced rectifier circuits, such as using a four diode full wave bridge rectifier, or using an op amp based “super diode” could also be used for envelope detectors:



Courtesy: https://www.schoolphysics.co.uk/age16-19/Electronics/Semiconductors/text/Rectification_/index.html


b. Synchronous Demodulator (Lock-in Amplifier)

Consider this:

$$\begin{aligned}
 A\cos(\omega t) \times B\cos(\omega t) &= 0.5AB[\cos(\omega t - \omega t) + \cos(\omega t + \omega t)] \\
 &= 0.5AB[\cos(0) + \cos(2\omega t)] \\
 &= 0.5AB + 0.5AB\cos(2\omega t)
 \end{aligned}$$

\uparrow \uparrow
 DC term AC term at $2\omega t$

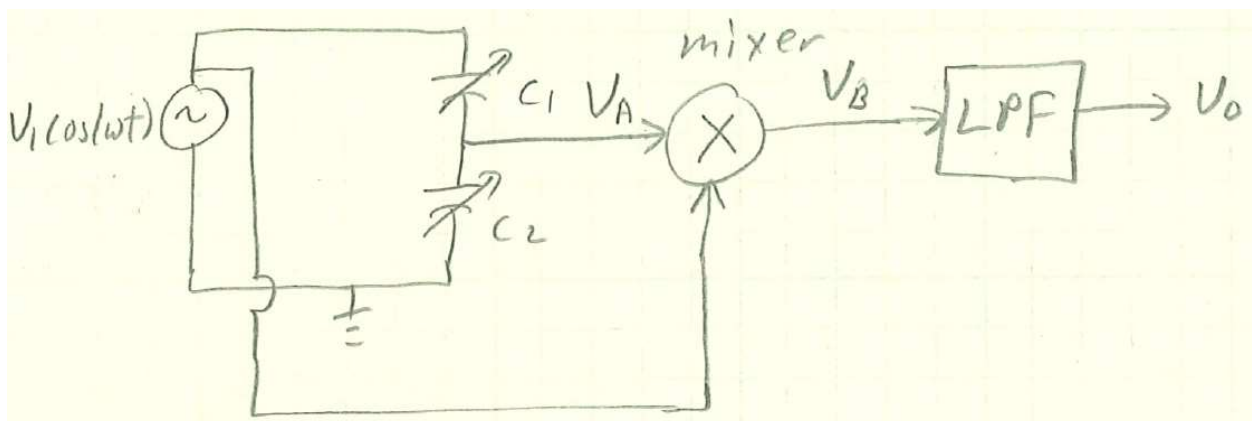So let's connect our differential capacitive sensor into a new circuit:



$V_A = V_1 \cos(\omega t) \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right]$ → same form as with the AC voltage divider

$$V_B = V_A V_1 \cos(\omega t)$$

$$= 0.5 V_1^2 \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right] + 0.5 V_1^2 \cos(2\omega t) \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right]$$

↑
↑
 DC term
 AC term at $2\omega t$

The LPF attenuates the AC term so that:


$$V_o \approx 0.5 V_1^2 \left[0.5 \left(1 - \frac{x(t)}{d_o} \right) \right] = V_c \left(1 - \frac{x(t)}{d_o} \right)$$

where V_c is a constant: $V_c = 0.5 V_1^2 (0.5)$

Now, V_o is a DC voltage that is a linear function of $x(t)$.

5. Capacitor Interface Circuitry: Transimpedance amplifier (TIA)

Consider:

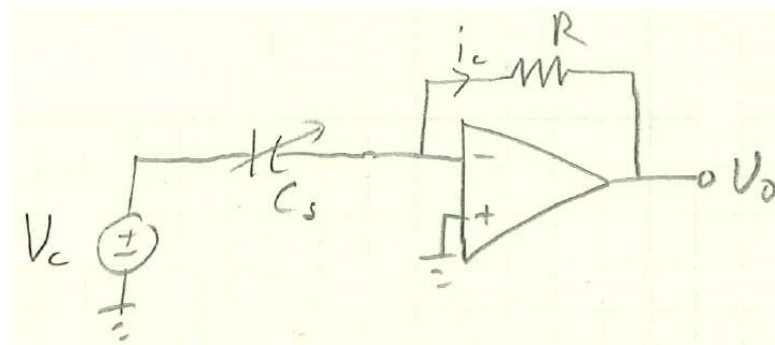

Note: some op amps are not stable with the input tied to a capacitor, and the output will break into high frequency oscillation.

But assuming the op amp configuration is stable: $v_o = -i_c R$

Note: for this inverting amplifier circuit, since the input is a current and the output is a voltage, the gain is a resistance with units of Ω .

For a fixed capacitor: $i_c = C \frac{dv_c}{dt}$. Note: as a differentiator of v_c , the TIA is noisy: it amplifies high frequency noise.

However, the more general case is: $i_c = C \frac{dv_c}{dt} + v_c \frac{dC}{dt} = C \frac{dv_c}{dt} + v_c \frac{\partial C}{\partial x} \frac{dx}{dt}$

a. If v_c is a constant, V_c , then $i_c = V_c \frac{\partial C}{\partial x} \frac{dx}{dt}$

If the capacitor's electrodes are in relative motion, then $\frac{dx}{dt}$ is a velocity term. In steady state, the time varying $C_s(t)$ pumps i_c into the circuit.

b. If $V_c = V_A \sin(\omega t)$ and $\omega \gg \omega_{MEMS}$,


then for short time periods of several V_c cycles, C_s is nearly constant and

$v_c \frac{dC_s}{dt} \approx 0$ (i.e. a very small change during the measurement time)

So: $i_c \approx C_s \frac{dV_c}{dt} = C_s V_A \omega \cos(\omega t)$

And finally: $v_o \approx -C_s R V_A \omega \cos(\omega t)$ for quick measurements of C_s .

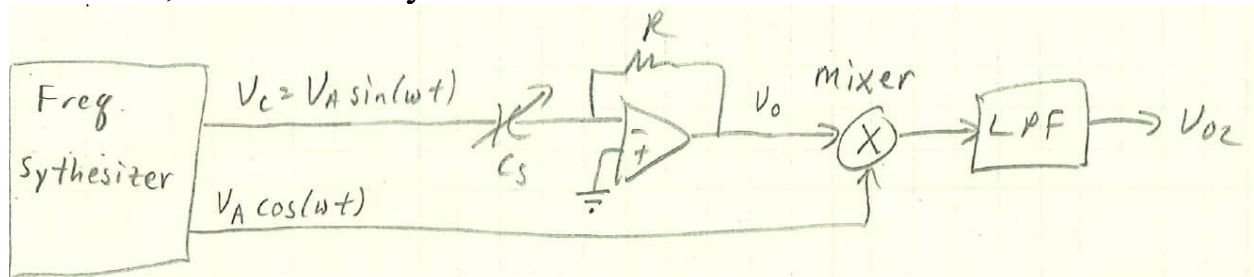However, we can add synchronous demodulation here too:




$$\therefore V_{o2} = LPF[V_o \times V_A \cos(\omega t)] = -0.5C_s R V_A^2 \omega = k C_s$$

where k is a constant: $k = -0.5 R V_A^2 \omega$

So once again, V_{o2} is a DC voltage proportional to C_s , our sensor's capacitance.

Capacitive Fringing Field Sensors

Consider:

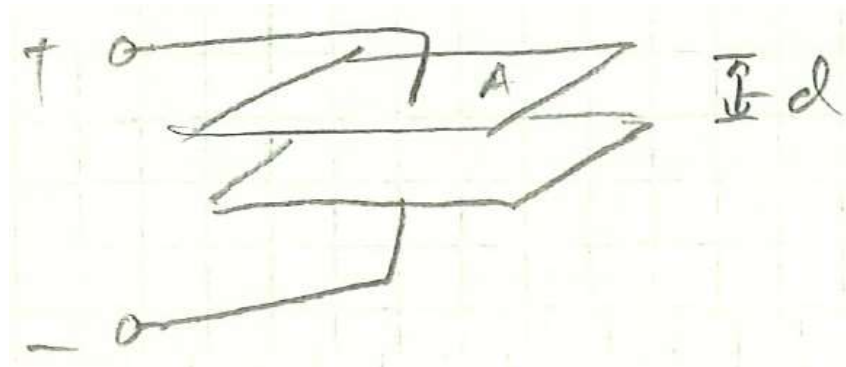


For $A \gg d^2$: $C \approx \frac{\epsilon_0 \epsilon_r A}{d}$, and fringing effects are small,

But $A \approx d^2$ or if $d^2 > A$, $C \neq \frac{\epsilon_0 \epsilon_r A}{d}$.

Actually now, $C > \frac{\epsilon_0 \epsilon_r A}{d}$ due to fringing effects.

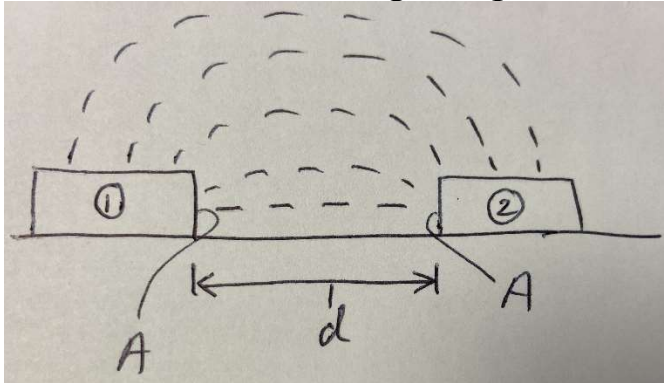Consider the case using two planar electrodes:




1 and 2 are the electrodes, d is the distance between them, and A is the area of each electrode facing each other. The dashed lines represent electric flux lines.

The capacitance between 1 and 2 can be modeled by:

$$C \approx \frac{\epsilon_0 \epsilon_r A \gamma}{d}, \text{ where } \gamma \text{ is a fringing scale factor and } \gamma > 1.$$

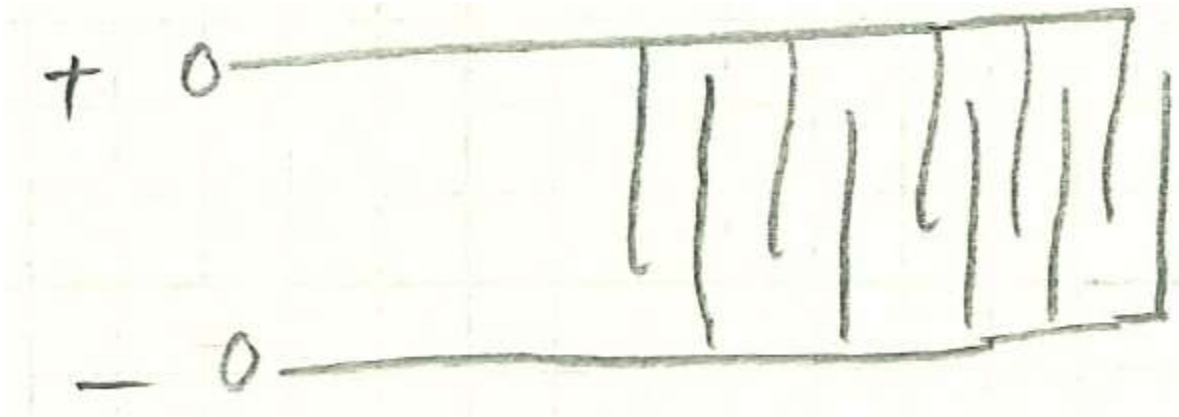Often, the two electrodes are arranged in an interdigitated electrode (IDE) layout on a planar surface, realizing a capacitive fringing field sensor:



Let n = number of interdigitated fingers.

$$C \approx \frac{(n - 1) \epsilon_0 \epsilon_r A \gamma}{d}$$

Sometimes, the IDE is coated with a thin insulating layer, such as polyimide (PCB technology) or silicon dioxide (MEMS technology).


When the electrode width is equal to d , the sensing range above the sensor is approximately $1.25d$ to $1.5d$.

Applications for capacitive fringing field sensors:

1. Detecting the presence of liquid water ($\epsilon_{r|\text{air}} \approx 1$ and $\epsilon_{r|\text{water}} \approx 80$ at room temperature)
2. Measuring the moisture content of many materials
3. Measuring the level of water and other liquids
4. Detecting ice: above ~ 10 KHz, $\epsilon_{r|\text{water}} \gg \epsilon_{r|\text{ice}}$
5. Measuring relative humidity


Meso scale versions, such as in PCB technology, can have relatively large capacitances \rightarrow 100s of pF.

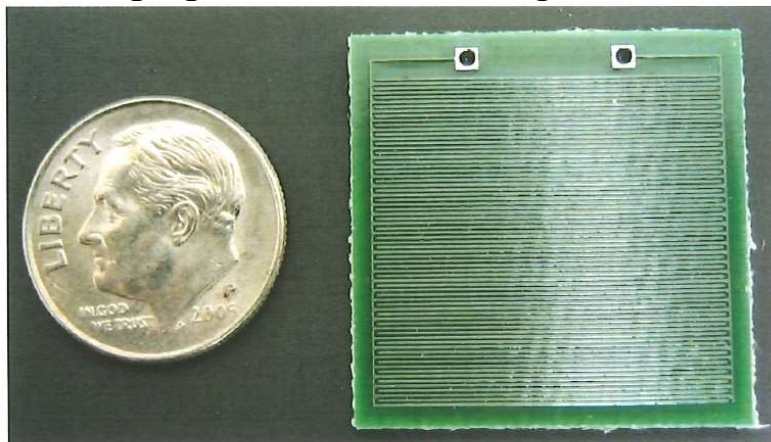PCB Capacitive Fringing Field Sensor Example:




Photo

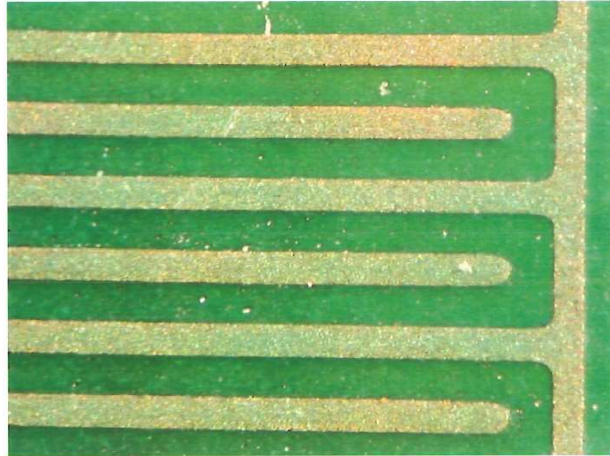Device: 25.4 mm x 25.4 mm
70 interdigitated fingers ($\sim 150\mu\text{m}$ wide)
22.4 mm electrode overlap
63.9pF capacitance in air
321.3pF capacitance when submerged in water



Close up photo of electrode structure

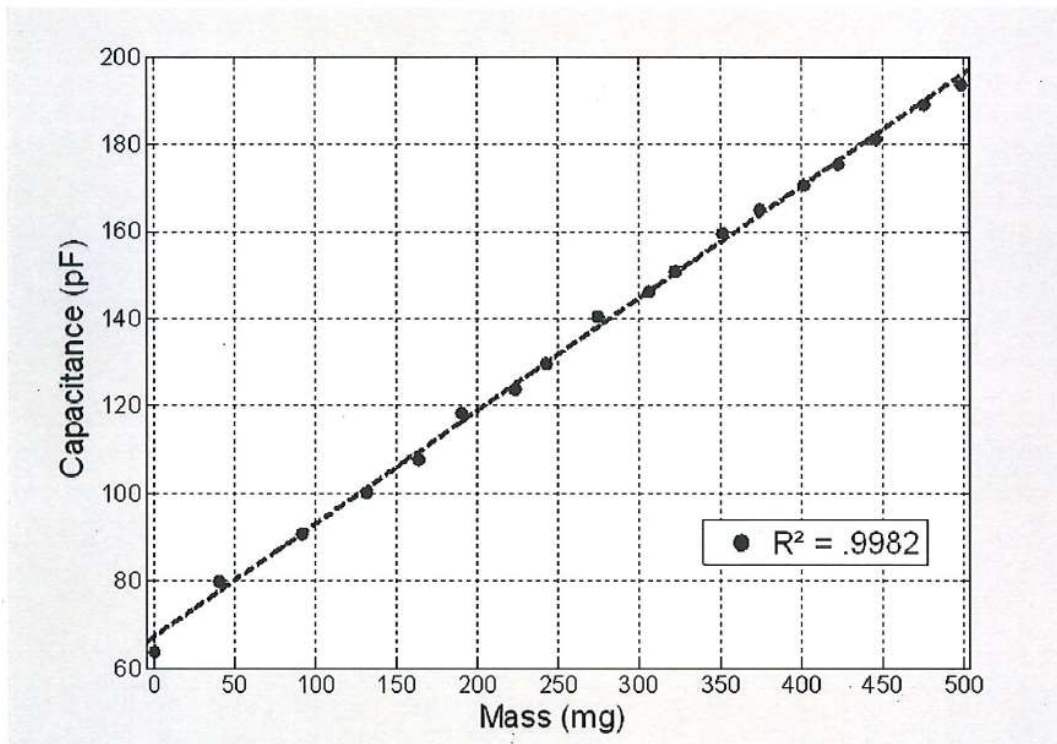

Mass of water drop sensor response

