


Lecture 5 - Modeling for Synthesis

Register Transfer Level (RTL) Design

Register Transfer Language (RTL) Design

- A **system** is viewed as a structure comprising registers, functions and their control signals
- Show dataflow through the system
- Instructions, Data, Addresses
- Functions store and manipulate data

No gates!!!

 

RTL register model

-- Model register to hold one datum of some type

-- Individual bits are not manipulated

```
library ieee; use ieee.std_logic_1164.all;
```

```
entity Reg8 is
```

```
  port (D: in std_logic_vector(7 downto 0);  
        Q: out std_logic_vector(7 downto 0);  
        LD: in std_logic);
```

```
end Reg8;
```

```
architecture behave of Reg8 is
```

```
begin
```

```
  process(LD)
```

```
  begin
```


```
    if (LD'event and LD='1') then
```

```
      Q <= D; -- load data into the register
```

```
    end if;
```

```
  end process;
```

```
end;
```

 

Asynchronous control inputs

```
library ieee; use ieee.std_logic_1164.all;
```

```
entity Reg8 is
```

```
  port (D: in std_logic_vector(7 downto 0);  
        CLK,PRE,CLR: in bit;  
        Q: out std_logic_vector(7 downto 0));
```

```
end Reg8;
```

```
architecture behave of Reg8 is
```

```
begin
```

```
  process(clk,PRE,CLR)
```

```
  begin
```

```
    if (CLR='0') then
```

```
      Q <= "00000000";
```

```
    elsif (PRE='0') then
```

```
      Q <= (others => '1');
```

```
    elsif rising_edge(clk) then
```


```
      Q <= D;
```

```
    end if;
```

```
  end process;
```

```
end;
```

--Async PRE/CLR

 

-- async CLR has precedence

-- force register to all 0s

-- async PRE has precedence if CLR='0'

-- force register to all 1s

-- sync operation only if CLR=PRE='1'

-- load D on clock transition

Synchronous reset/set

--Reset function triggered by clock edge

```
process (clk)
```

```
begin
```

```
  if (clk'event and clk = '1') then
```

```
    if reset = '1' then – reset has precedence over load
```

```
      Q <= "00000000" ;
```

```
    else
```

```
      Q <= D ;
```

```
    end if;
```

```
  end if;
```

```
end process;
```

Register with clock enable

-- “enable” effectively enables/disables clock

```
process (clk)
```

```
begin
```

```
    if rising_edge(clk) then -- detect clock transition
```

```
        if enable = '1' then -- enable load on clock transition
```

```
            Q <= D ;
```

```
        end if;
```

```
    end if;
```

```
end process;
```

Register with parameterized width

-- One model of a given function with variable data size

```
library ieee; use ieee.std_logic_1164.all;
```

```
entity REGN is
```

```
    generic (N: integer := 8);
```

-- N specified when REG used

```
    port ( CLK, RST, PRE, CEN: in std_logic;
```

```
          DATAIN: in std_logic_vector (N-1 downto 0); -- N-bit data in
```

```
          DOUT: out std_logic_vector (N-1 downto 0) -- N-bit data out
```

```
    );
```

```
end entity REGN;
```

```
architecture RTL of REGN is
```

```
begin
```

```
    process (CLK) begin
```

```
        if (CLK'event and CLK = '1') then
```

```
            if (RST = '1') then DOUT <= (others => '0'); --reset to all 0s
```

```
            elsif (PRE = '1') then DOUT <= (others => '1'); --preset to all 1s
```

```
            elsif (CEN = '1') then DOUT <= DATAIN; --load data
```

```
            end if;
```

```
        end if;
```

```
    end process;
```

```
end architecture RTL;
```

Vectors: "100" = ('1','0','0') = ('1', others => '0')

Arbitrarily long: "00...0" = (others => '0')

Instantiating the parameterized register

```
library ieee; use ieee.std_logic_1164.all;
```

```
entity TOP is
```

```
    port (    CLK,X,Y,A,B,C: in std_logic;
            DIN: in  std_logic_vector(5 downto 0);
            Q1: out std_logic_vector(5 downto 0);
            Q2: out std_logic_vector(4 downto 0);
            Q3: out std_logic_vector(3 downto 0)
            );
```

```
end entity TOP;
```

```
architecture HIER of TOP is
```

```
component REGN is
```

```
    generic (N: integer := 8);
    port (    CLK, RST, PRE, CEN: in std_logic;
            DATAIN: in  std_logic_vector (N-1 downto 0);
            DOUT:   out std_logic_vector (N-1 downto 0)
            );
```

```
end component REGN;
```

```
begin
```

```
R1: REGN generic map (6) port map  --6-bit register
      (CLK, A, B, C, DIN, Q1);
```

```
R2: REGN generic map (5) port map  --5-bit register (low 5 bits of DIN)
      (CLK, Y, X, C, DIN(4 downto 0),Q2);
```

```
R3: REGN generic map (4) port map  --4-bit register (low 4 bits of DIN)
      (CLK=>CLK, RST=>A, PRE=>B, CEN=>C, DATAIN=>DIN(3 downto 0), DOUT=>Q3);
```

```
end architecture HIER;
```


2-to-1 mux with parameterized data size

entity muxN is

```
generic (N: integer := 32); -- data size parameter
port ( A,B: in  std_logic_vector(N-1 downto 0);
      Y:  out std_logic_vector(N-1 downto 0);
      Sel: in  std_logic);
```

end muxN;

architecture rtl of muxN is

begin

```
Y <= A when Sel = '0' else B; -- A,B,Y same type
```

end;

-- specify parameter N at instantiation time

M: muxN generic map (16)

```
port map(A=>In1, B=>In2, Y=>Out1);
```

Other types of generic parameters

entity and02 is

```
    generic (Tp : time := 5 ns);    -- gate delay
```

parameter

```
    port (A,B: in std_logic;
          Y:  out std_logic);
```

end and02;

architecture eqn of and02 is

begin

```
    Y <= A and B after Tp;    -- gate with delay Tp
```

end;

.....

```
A_tech1: and02 generic map (2 ns) port map (M,N,P);
```

```
A_tech2: and02 generic map (1 ns) port map (H,K,L);
```

← Gates with different delays.

IEEE Std. 1076.3 Synthesis Libraries

- **Supports arithmetic models**
 - **ieee.numeric_std** (ieee library package)
 - defines UNSIGNED and SIGNED types as arrays of std_logic

```
type SIGNED is array(NATURAL range <>) of STD_LOGIC;  
type UNSIGNED is array(NATURAL range <>) of STD_LOGIC;
```
 - defines arithmetic/relational operators on these types
 - Supports RTL models of functions

- **Lesser-used packages:**
 - **ieee.numeric_bit**
 - same as above except SIGNED/UNSIGNED are arrays of type bit
 - **ieee.std_logic_arith** (*from Synopsis*)
 - Non-standard predecessor of numeric_std/numeric_bit

NUMERIC_STD package contents

- Arithmetic functions: + - * / rem mod
 - Combinations of operand types for which operators are defined:
 - SIGNED + SIGNED return SIGNED
 - SIGNED + INTEGER return SIGNED
 - INTEGER + SIGNED return SIGNED
 - SIGNED + STD_LOGIC return SIGNED
 - PLUS: above combinations with UNSIGNED and NATURAL

- Other operators for SIGNED/UNSIGNED types:
 - Relational: = /= < > <= >=
 - Shift/rotate: sll, srl, sla, sra, rol, ror
 - Maximum(a,b), Minimum(a,b)

- Convert between types:
 - TO_INTEGER(SIGNED), TO_INTEGER(UNSIGNED)
 - TO_SIGNED(INTEGER,#bits), TO_UNSIGNED(NATURAL,#bits)
 - RESIZE(SIGNED or UNSIGNED,#bits) – changes # bits in the vector

Arithmetic with NUMERIC_STD package

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in  UNSIGNED(3 downto 0) ;
          mySum : out UNSIGNED(3 downto 0) ) ;
end Adder4;

architecture Behave_B of Adder4 is
begin
    mySum <= in1 + in2; -- overloaded '+' operator
end Behave_B;
```

UNSIGNED = UNSIGNED + UNSIGNED

Conversion of “closely-related” types

- **STD_LOGIC_VECTOR, SIGNED, UNSIGNED:**

- All arrays of **STD_LOGIC** elements

- Example: How would one interpret “1001” ?

- **STD_LOGIC_VECTOR:** simple pattern of four bits

- **SIGNED:** 4-bit representation of number -7 (**2's complement #**)

- **UNSIGNED:** 4-bit representation of number 9 (**unsigned #**)

- Vectors of same element types can be “converted” (re-typed/re-cast) from one type to another

```
signal A: std_logic_vector(3 downto 0) := “1001”;
```

```
signal B: signed(3 downto 0);
```

```
signal C: unsigned(3 downto 0);
```

```
B <= signed(A);           -- interpret A value “1001” as number -7
```

```
C <= unsigned(A);        -- interpret A value “1001” as number 9
```

```
A <= std_logic_vector(B); -- interpret B as bit pattern “1001”
```

Conversion of “closely-related” types

For arrays of same dimension, *having elements of same type*

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
use IEEE.NUMERIC_STD.all;
```

```
entity Adder4 is
```

```
    port ( in1, in2 : in  STD_LOGIC_VECTOR(3 downto 0) ;
```

```
          mySum : out STD_LOGIC_VECTOR(3 downto 0) ) ;
```

```
end Adder4;
```

```
architecture Behave_B of Adder4 is
```


```
begin
```

```
    mySum <=
```

```
        STD_LOGIC_VECTOR( SIGNED(in1) + SIGNED(in2) );
```

```
end Behave_B;
```

SIGNED result

 

Interpret `STD_LOGIC_VECTOR` as `SIGNED`
Function: `SIGNED = SIGNED + SIGNED`

Interpret `SIGNED` result as `STD_LOGIC_VECTOR`.

Example – binary counter

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.NUMERIC_STD.all;  
ENTITY counter IS  
    port( Q: out std_logic_vector(3 downto 0);  
        ....  
END counter;
```

```
ARCHITECTURE behavior OF counter IS  
    signal Qinternal: unsigned(3 downto 0);  
begin
```

From NUMERIC_STD package



```
    Qinternal <= Qinternal + 1;    -- UNSIGNED = UNSIGNED + NATURAL  
    Q <= std_logic_vector(Qinternal); -- re-type unsigned as std_logic_vector
```


Using a “variable” to describe sequential behavior within a process

```
-- Assume Din and Dout are std_logic_vector
-- and numeric_std package is included
cnt: process(clk)
    variable count: integer; -- internal counter state
begin
    -- valid only within a process
    if clk='1' and clk'event then
        if ld='1' then
            count := to_integer(unsigned(Din)); --update immediately
        elsif cnt='1' then
            count := count + 1; --update immediately
        end if;
    end if;
    Dout <= std_logic_vector(to_unsigned(count,32)); --schedule Dout
end process;
```

Counting to some max_value (not 2^n)

-- full-sized comparator circuit generated to check count = max

process begin

wait until clk'event and clk='1' ;

if (count = max_value) **then**

 count <= 0 ; --roll over from max_value to 0

else

 count <= count + 1 ; --otherwise increment

end if ;

end process ;

Decrementer and comparator

process begin

wait until clk'event and clk='1' ;

if (count = 0) **then**

 count <= max_value ; -- roll over from 0 to max_value

else

 count <= count - 1 ; -- otherwise decrement


end if ;

end process ;

Verilog Modeling Trap

- The order of execution of **procedural statements** in a cyclic behavior may **depend on the order** in which the statements are listed
- Procedural assignments are called **“blocked” assignments** (or blocking assignments)
 - Execute sequentially
 - A procedural assignment must complete execution before the next statement can be executed
 - i.e. the statements that follow a procedural statement are **“blocked”** till the current one completes execution
- Expression substitution is recognized by synthesis tools

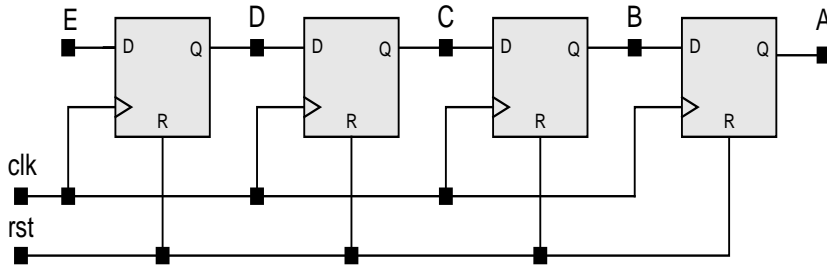Example: Modeling Trap of a Shift Register



```

module shiftreg_PA (E, A, B, C, D, clk, rst);
  output A;
  input E;
  input clk, rst;
  reg A, B, C, D;

  always @ (posedge clk or posedge rst)
  begin
    if (reset) begin
      A = 0; B = 0; C = 0; D = 0; end
    else begin
      A = B;
      B = C;
      C = D;
      D = E;
    end
  end
endmodule

```


```

module shiftreg_PA_rev (E, A, B, C, D,
  clk, rst);
  output A;
  input E;
  input clk, rst;
  reg A, B, C, D;

  always @ (posedge clk or posedge rst)
  begin
    if (reset) begin
      A = 0; B = 0; C = 0; D = 0; end
    else begin
      D = E;
      C = D;
      B = C;
      A = B;
    end
  end
endmodule

```
 
$$\left. \begin{array}{l} D = E; \\ C = D; \\ B = C; \\ A = B; \end{array} \right\} A = E$$



Nonblocking Assignment (\leq) in Cyclic Behavior

- Effectively execute concurrently rather than sequentially by blocked assignments
 - Independent of the order where they are listed
- **Simulator must**
 - **Sample all variables referenced by RHS with nonblocking assignments**
 - **Held them in memory**
 - **Use them to update LHS variables **concurrently****
 - **Before the assignments are evaluated**
 - **Nonblocking makes NO dependency between statements**
- Avoid having multiple behaviors assigning values to be the same variable
 - Otherwise, software race condition makes outcome indeterminate
 - For example, multi-driver case

Blocked (=) v.s. Nonblocking (<=)


- If no data dependency, results of blocked and nonblocking assignments are identical
- Strongly recommend
 - Blocked assignment for combinational logic using level sensitive behavior
 - Nonblocking assignments for edge sensitive behavior

Shift Register Using Nonblocking Assignments

```
module shiftreg_nb (A, E, clk, rst);
    output A;
    input  E;
    input  clk, rst;
    reg    A, B, C, D;

    always @ (posedge clk or posedge rst)
    begin
        if (rst)
            begin A <= 0; B <= 0; C <= 0; D <= 0;
            end
        else
            begin
                A <= B;           //      D <= E;
                B <= C;           //      C <= D;
                C <= D;           //      B <= C;
                D <= E;           //      A <= B;
            end
        end
    end
endmodule
```

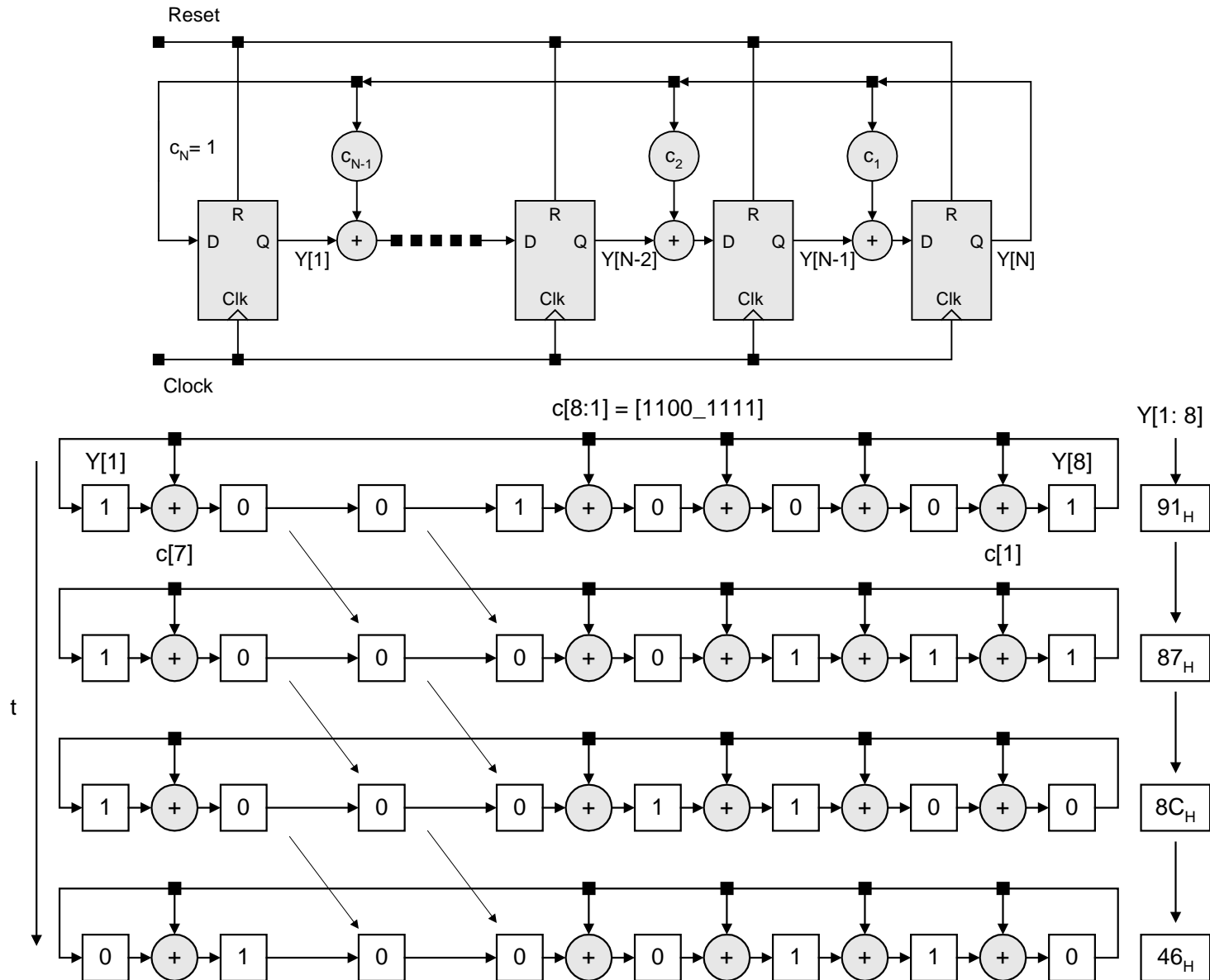
Linear-Feedback Shift Register (Type II LFSR) Dataflow



LFSR --- RTL Dataflow

```
module Auto_LFSR_RTL (Y, Clock, Reset);
  parameter                               Length = 8;
  parameter [1: Length]                   initial_state = 8'b1001_0001; // 91h
  parameter [1: Length]                   Tap_Coefficient = 8'b1111_0011;

  input                                     Clock, Reset;
  output [1: Length]                       Y;
  reg [1: Length]                           Y;

  always @ (posedge Clock)
    if (!Reset) Y <= initial_state;           // Active-low reset to initial state
    else begin
      Y[1] <= Y[8];
      Y[2] <= Tap_Coefficient[7] ? Y[1] ^ Y[8] : Y[1];
      Y[3] <= Tap_Coefficient[6] ? Y[2] ^ Y[8] : Y[2];
      Y[4] <= Tap_Coefficient[5] ? Y[3] ^ Y[8] : Y[3];
      Y[5] <= Tap_Coefficient[4] ? Y[4] ^ Y[8] : Y[4];
      Y[6] <= Tap_Coefficient[3] ? Y[5] ^ Y[8] : Y[5];
      Y[7] <= Tap_Coefficient[2] ? Y[6] ^ Y[8] : Y[6];
      Y[8] <= Tap_Coefficient[1] ? Y[7] ^ Y[8] : Y[7];
    end
endmodule
```

LFSR --- RTL Repetitive Algorithm

```
module Auto_LFSR_ALGO (Y, Clock, Reset);
  parameter                               Length = 8;
  parameter [1: Length]                   initial_state = 8'b1001_0001;
  parameter [1: Length]                   Tap_Coefficient = 8'b1111_0011;
  input                                     Clock, Reset;
  output [1: Length]                       Y;
  integer                                   Cell_ptr;
  reg                                       Y;

  always @ (posedge Clock)
  begin
    if (Reset == 0) Y <= initial_state;    // Arbitrary initial state, 91h
    else
      begin
        for (Cell_ptr = 2; Cell_ptr <= Length; Cell_ptr = Cell_ptr +1)
          if (Tap_Coefficient [Length - Cell_ptr + 1] == 1)
            Y[Cell_ptr] <= Y[Cell_ptr -1]^ Y [Length]; // ^ is xor
          else
            Y[Cell_ptr] <= Y[Cell_ptr -1];
        Y[1] <= Y[Length];
      end
    end
endmodule
```

Verilog Repetitive Statements

- for, repeat, while, forever
 - All activities of all iterations are done in one time step
 - “disable” to terminate a named block
 - Some logic synthesis tools can only synthesize “for” loop
 - i.e., repeat, while, forever are not synthesizable in these tools

Verilog Statement

- Statement can be
 - a single statement or
 - a block statement (i.e. **begin ... end**)
- A named block statement
 - i.e. **begin: <block_name> ... end**

Ones Counter

- Verilog bitwise right-shift operator (\gg), filling with '0'
 - Arithmetic right-shift (\ggg)
- Compare the following two designs

// count_of_1s declares a named block of statements

// Original design

begin: *count_of_1s*

reg [7: 0] temp_reg;

count = 0;

temp_reg = reg_a; *// load a data word*

while (temp_reg)

begin

if (temp_reg[0])

 count = count + 1;

 temp_reg = temp_reg \gg 1;

end

end

// Alternative

begin: *count_of_1s*

reg [7: 0] temp_reg;

count = 0;

temp_reg = reg_a; *// load a data word*

while (temp_reg)

begin

 count = count + temp_reg[0];

 temp_reg = temp_reg \ggg 1;

end

end

Find_First_One

- Find the location of the first 1 in a 16-bit word
 - The word is assumed to contain at least one 1

```
module find_first_one (index_value, A_word, trigger);
  output      [3: 0]    index_value;
  input       [15: 0]   A_word;
  input                               trigger;
  reg         [3: 0]    index_value;


  always @ (trigger)
    begin: search_for_1
      index_value = 0;
      for (index_value = 0; index_value <= 15; index_value = index_value + 1)
        if (A_word[index_value] == 1)
          disable search_for_1;
    end
endmodule
```

Multicycle Operations -- 4-cycle Adder


- Some digital machines have repetitive operations distributed over multiple clock cycles
 - Can be modeled in Verilog by a synchronous cyclic behavior that has as many nested edge-sensitive event control expressions as needed to complete the operations
 - May not be synthesizable
- Example: 4-cycle adder
 - To form the sum of four successive samples of a datapath
 - Store the samples in registers then use multiple adders
 - Or, one adder to accumulate the sum sequentially
 - One FSM to control the 4-cycle operation and only one adder
 - The resulting synthesized implementation
 - To ensure proper re-initialization, “disable” is in each clock cycle
 - Regardless when the “reset” is asserted

4-cycle Adder

```
module add_4cycle (sum, data, clk, reset);  
  output      [5: 0]  sum;  
  input       [3: 0]  data;  
  input       clk, reset;  
  reg         sum;  
  always @ (posedge clk) begin: add_loop  
    if (reset) disable add_loop; else sum <= data;  
    @ (posedge clk) if (reset) disable add_loop; else sum <= sum + data;  
    @ (posedge clk) if (reset) disable add_loop; else sum <= sum + data;  
  end  
endmodule
```

 

Class Test 1

 

Algorithmic State Machine (ASM) Charts

- State Transition Graphs (STGs)
 - Indicate the transitions that result from inputs applied to the state machine in a particular state
 - Do not directly display the evolution of states under the application of input data
- ASM Charts
 - Abstraction of functionality of a sequential machine
 - Reveal the sequential steps of a machine's activity
 - Focus on activities rather than content of storage elements
 - Example: the counter to be introduced shortly
 - Three states: idle, incrementing and decrementing
 - Independent of counter word width
 - ASM chart elements
 - **state box**
 - **decision box**
 - **conditional box**
 - Clock governs transitions between states
 - Linked ASM charts describe complex machines
 - ASM charts represent both Mealy and Moore machines

ASM Chart Elements


- State box
 - Each state box represents the state of the machine between synchronizing clock events
- Decision box
- Conditional box




State Box



 Conditional Output or Register Operation Box





Decision Box

 

Asyn/Synchronous Reset in ASM

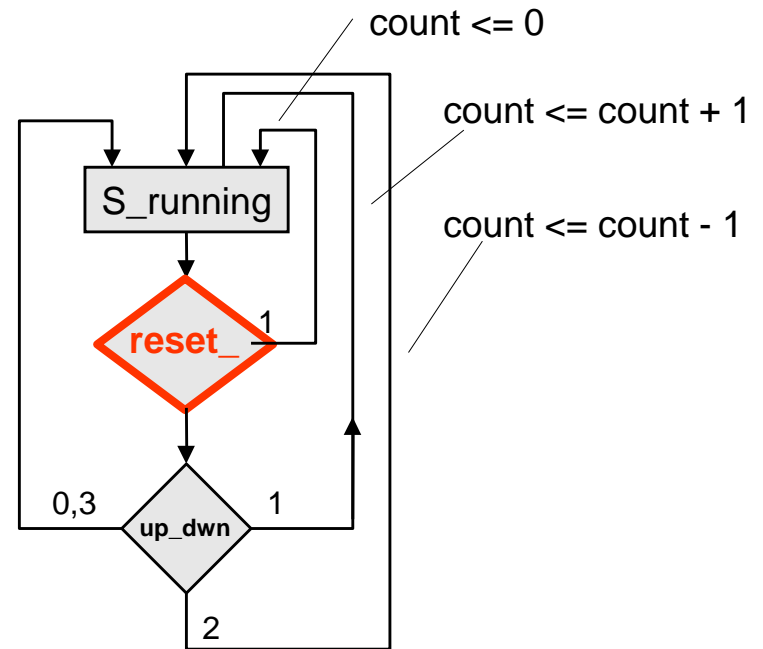 - Asynchronous reset: a RESET input to the reset state box
- Synchronous reset: one decision box of RESET input




ASM Chart (cont.)

- Only paths leading to a change in states are shown in ASM
- If a variable not appear in a decision box on a path leaving a state, then the path is independent of the value of the variable

ASM Chart Example: Tail Light Controller

A Mealy Machine with Synchronous Reset

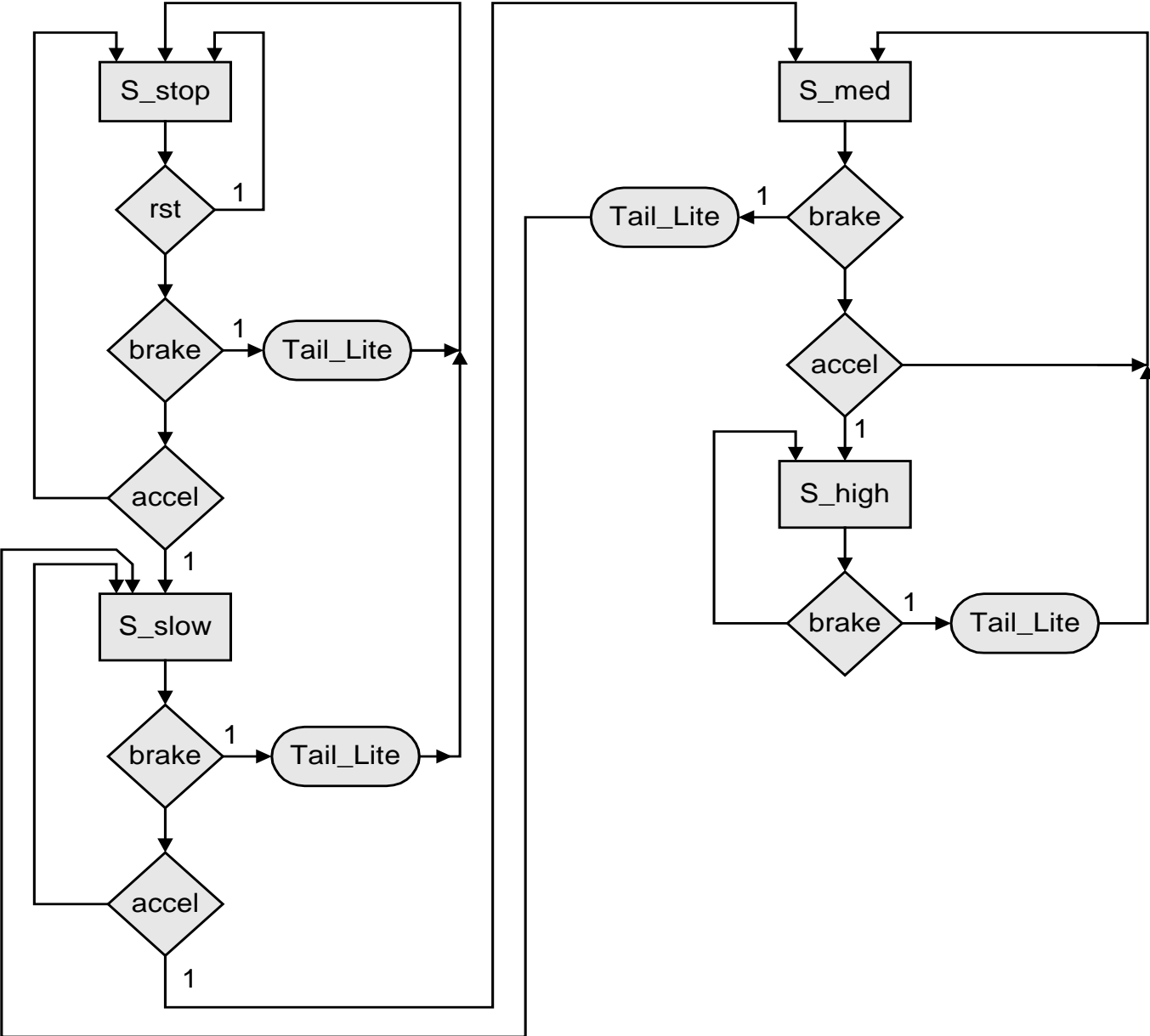


ASM and Datapath (ASMD) Charts

- To form an ASMD: modify ASM (i.e. controller) by annotating each of its paths to indicate the concurrent register operations (i.e. datapath operations) when the controller makes a transition along the path
 - Not in conditional boxes
 - Not in state boxes
 - Because the datapath registers are not part of the controller
 - Fact: output generated by the controller controls the datapath register
- Clarify a design of a sequential machine by separating the design of its datapath from the design of the controller
- ASMD chart maintains a clear relationship between a datapath and its controller
 - Outputs generated by the controller control the datapath register
 - Outputs generated by datapath report the status of datapath back to the controller

2:1 Decimator Using 2-stage Pipeline


- Used to move data from a high clock rate datapath to a lower data rate datapath
 - Can also used to convert data from a parallel format to a serial format
- ASMD of the 2:1 decimator
 - A Mealy machine with synchronous reset to S_idle
 - An incomplete ASMD
 - Because no conditional outputs
 - i.e the output of the controller to control how datapath works
 - Such as adding an output for load-register
 - E.g. “Ld” state represents load to R0 since $R0 \leftarrow \{P1, P0\}$ on the path leaving the state when Ld=1
 - Note that **datapath register operations made with a nonblocking assignment are concurrent**
 - Hence no race between $R0 \leftarrow \{P1, P0\}$ and $\{P1, P0\} \leftarrow \{0, 0\}$

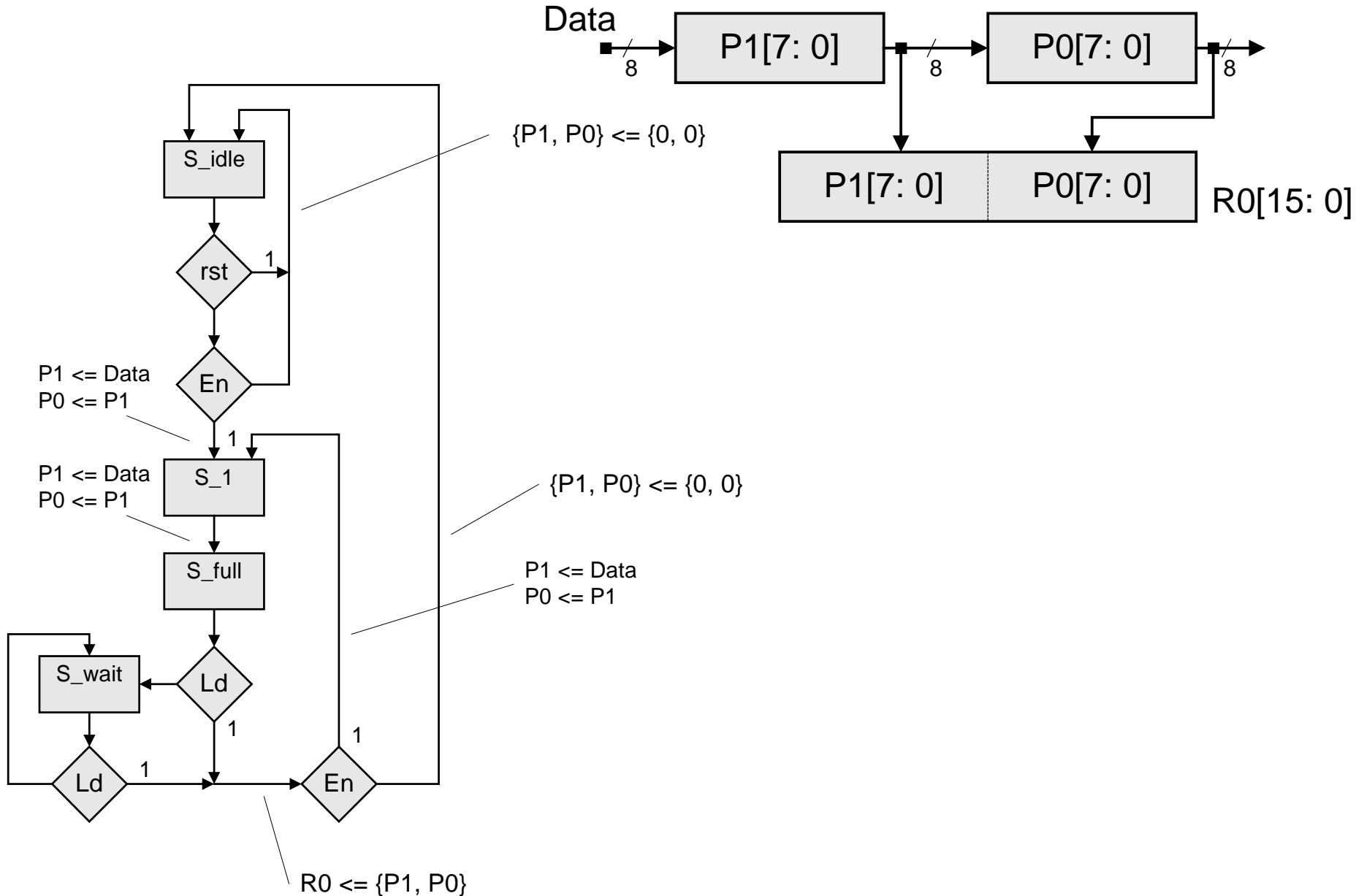2:1 Decimator Using 2-stage Pipeline (cont.)



Synthesis of Sequence Recognizer


 
- Example: detect 3 consecutive 1s
 - Assert D_out when a given pattern of consecutive bits has been received in its serial input stream, D_in
 - Apply data on the rising edge of the clock if the state transitions are to occur on the falling edge of the clock, and visa-versa
 - Recall the general rule for exercising FSM



Conventions to Describe Sequence Recognizers

- The output of a Mealy machine is valid immediately before the active edge of the clock controlling the machine
 - Data must be stable prior to active edge for at least the setup time
- Successive values inputs are received in successive clock cycles.
- A *non-resetting* machine continues to assert its output if the input bit pattern is overlapping
- A *resetting* machine asserts for one cycle after detecting the input sequence, and then de-asserts for one cycle before detecting the next sequence of bits

Mealy and Moore ASMs (3 Consecutive 1s)

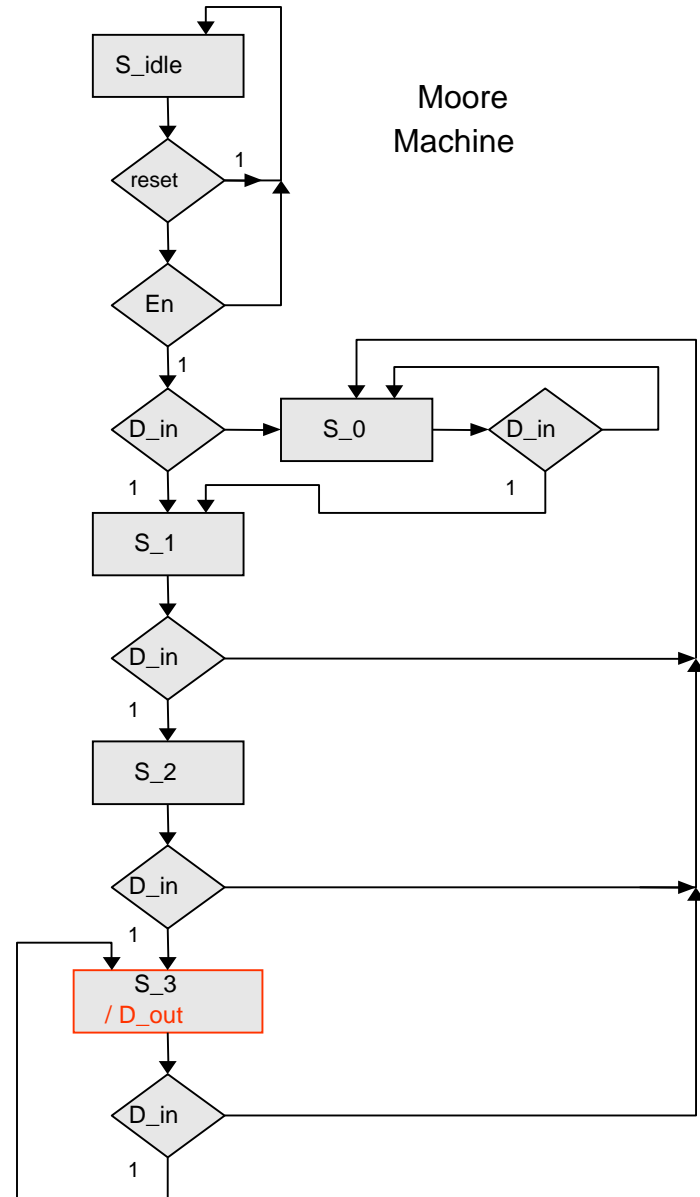 

Mealy and Moore for 3 Consecutive 1s (cont.)


- Both are non-resetting
 - How to modify them into resetting sequence recognizers?
- Moore has one more state than Mealy
- The Mealy machine anticipates D_{in} and asserts D_{out} before the third clock
- The Moore machine does not anticipate D_{in}
 - That is, the Moore machine asserts D_{out} in the state reached after the third active edge of the clock

Sequence Recognizer for 3 Consecutive 1s (cont.)

```

module Seq_Rec_3_1s_Mealy
    (D_out, D_in, En, clk, reset);
output    D_out;
input     D_in, En;
input     clk, reset;
// Binary coding for states
parameter S_idle =    0;
parameter S_0 =      1;
parameter S_1 =      2;
parameter S_2 =      3;
reg[1: 0] state, next_state;

```

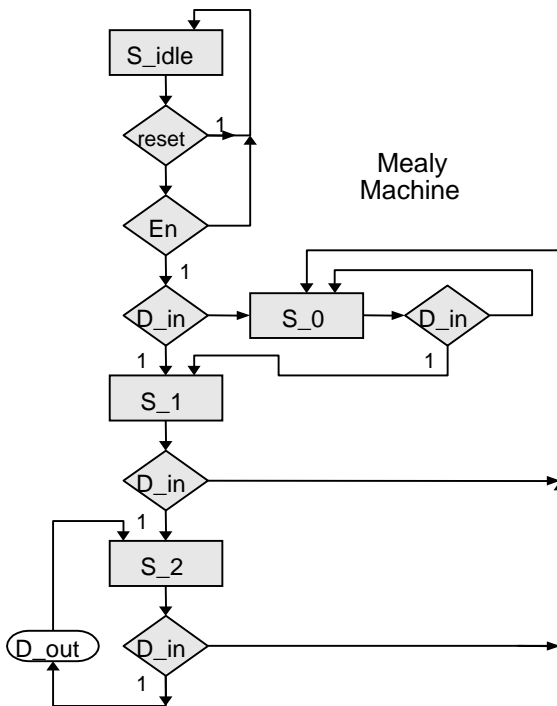

```

always @ (negedge clk)
    if (reset == 1) state <= S_idle; else state <= next_state;

always @ (state or D_in) begin
    case (state) // Partially decoded
        S_idle: if ((En == 1) && (D_in == 1)) next_state = S_1;
                else if ((En == 1) && (D_in == 0)) next_state = S_0;
                else next_state = S_idle;
        S_0: if (D_in == 0) next_state = S_0;
            else if (D_in == 1) next_state = S_1;
            else next_state = S_idle;
        S_1: if (D_in == 0) next_state = S_0;
            else if (D_in == 1) next_state = S_2;
            else next_state = S_idle;
        S_2: if (D_in == 0) next_state = S_0;
            else if (D_in == 1) next_state = S_2;
            else next_state = S_idle;
        default: next_state = S_idle;
    endcase
end
assign D_out = ((state == S_2) && (D_in == 1)); // Mealy output
endmodule


```

Sequence Recognizer for 3 Consecutive 1s (cont.)

```

module Seq_Rec_3_1s_Moore
    (D_out, D_in, En, clk, reset);
output  D_out;
input   D_in, En;
input   clk, reset;
// Binary coding for states
parameter S_idle = 0;
parameter S_0 = 1;
parameter S_1 = 2;
parameter S_2 = 3;
parameter S_3 = 4;
reg[2:0] state, next_state;

```

 

```

always @ (negedge clk)
    if (reset == 1) state <= S_idle; else state <= next_state;

always @ (state or D_in) begin
    case (state)
        S_idle: if ((En == 1) && (D_in == 1))      next_state = S_1; else
                if ((En == 1) && (D_in == 0))      next_state = S_0;
                else                                next_state = S_idle;
        S_0:    if (D_in == 0)                      next_state = S_0; else
                if (D_in == 1)                      next_state = S_1;
                else                                next_state = S_idle;
        S_1:    if (D_in == 0)                      next_state = S_0; else
                if (D_in == 1)                      next_state = S_2;
                else                                next_state = S_idle;
        S_2, S_3: if (D_in == 0)                   next_state = S_0; else
                if (D_in == 1)                   next_state = S_3;
                else                                next_state = S_idle;
        default:
        endcase
    end
    assign D_out = (state == S_3); // Moore output
endmodule



```


Alternative Design for Sequence Recognizer

- Alternative approach: Shift input bits through a register and detect contents
 - Consider sequence recognizer as a datapath unit
 - Such as a shift register
 - Then compare the content of shift register with the expected pattern
- Note: an explicit state machine implementation of the alternative design for a sequence recognizer is not necessarily the most efficient implementation

Alternative Design for Sequence Recognizer (cont.)

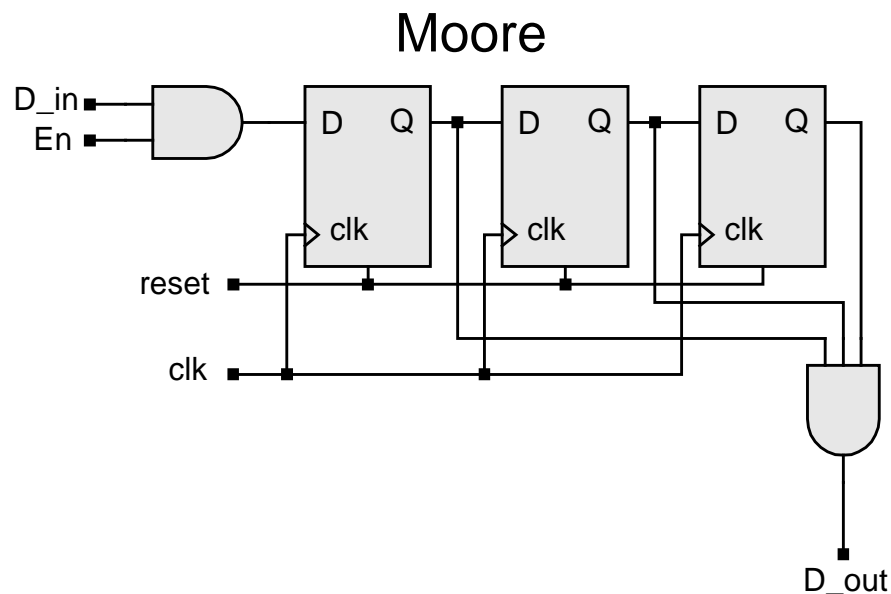 - The Mealy/Moore machines below are gated the datapath with En
 - *What happens if $En=0$?*
 - Register content will be lost
- Mealy has one less FF than Moore



Alternative Design for Sequence Recognizer (cont.)

```
module Seq_Rec_3_1s_Mealy_Shft_Reg (D_out, D_in, En, clk, reset);  
  output          D_out;  
  input           D_in, En;  
  input           clk, reset;  
  parameter      Empty = 2'b00;  
  reg    [1: 0]   Data;  
  always @ (negedge clk)  
    if (reset == 1) Data <= Empty; else if (En == 1) Data <= {D_in, Data[1]};  
  assign D_out = ((Data == 2'b11) && (D_in == 1 )); // Mealy output depends on primary input  
endmodule
```

```
module Seq_Rec_3_1s_Moore_Shft_Reg (D_out, D_in, En, clk, reset);  
  output          D_out;  
  input           D_in, En;  
  input           clk, reset;  
  parameter      Empty = 3'b000;  
  reg    [2: 0]   Data;  
  always @ (negedge clk)  
    if (reset == 1) Data <= Empty; else if (En == 1) Data <= {D_in, Data[2:1]};  
  assign D_out = (Data == 3'b111); // Moore output depends on state only  
endmodule
```

Design of a Datapath Controller

1. Understand the problem

- Especially the register operations that must execute on **a given datapath architecture**

2. Define ASM

- A state machine controlled by primary inputs and status of datapath register (i.e. the feedback linkage from datapath to controller)

3. Create ASMD

- Annotating ASM with datapath operations associated with state transitions (i.e. path) of the controller
- Register operation of ASMD written in register transfer notations with **NONBLOCKING assignments**
 - since they are executed concurrently in the datapath

4. Controller outputs to datapath

- **For Moore machines:** Annotate state of the controller with unconditional output signals (i.e. outputs of a state)
- **For Mealy machines:** Include conditional boxes for controller output signals to control datapath

5. Feedback linkage from datapath to controller

- If there are signals reports status of datapath back to the controller, then use decision box

6. Integration

- Integrate the verified datapath module and the verified controller module with one parent module to verify the overall functionality


Counters and Registers

- Storage elements of counters and registers usually have the same synchronizing and control signals
 - One exception: ripple counter
 - Connects the output of a stage to the clock input of an adjacent stage
- Counters with asynchronous reset
- Ring counter
- Up/down/load counter
- Shift register
- Parallel load register
- Universal shift register
- Register file


Counters

- The ASM/ASMD have no indication of the bit-width of the counter
- Three states: S_idle, S_incr and S_decr
 - May be further simplified to a single state, S_running
- 2-bit input up_down to count up(1), count down(2) and hold the count (0 and 3)
- Active low asynchronous reset

Counters(3 states) with Async Reset_

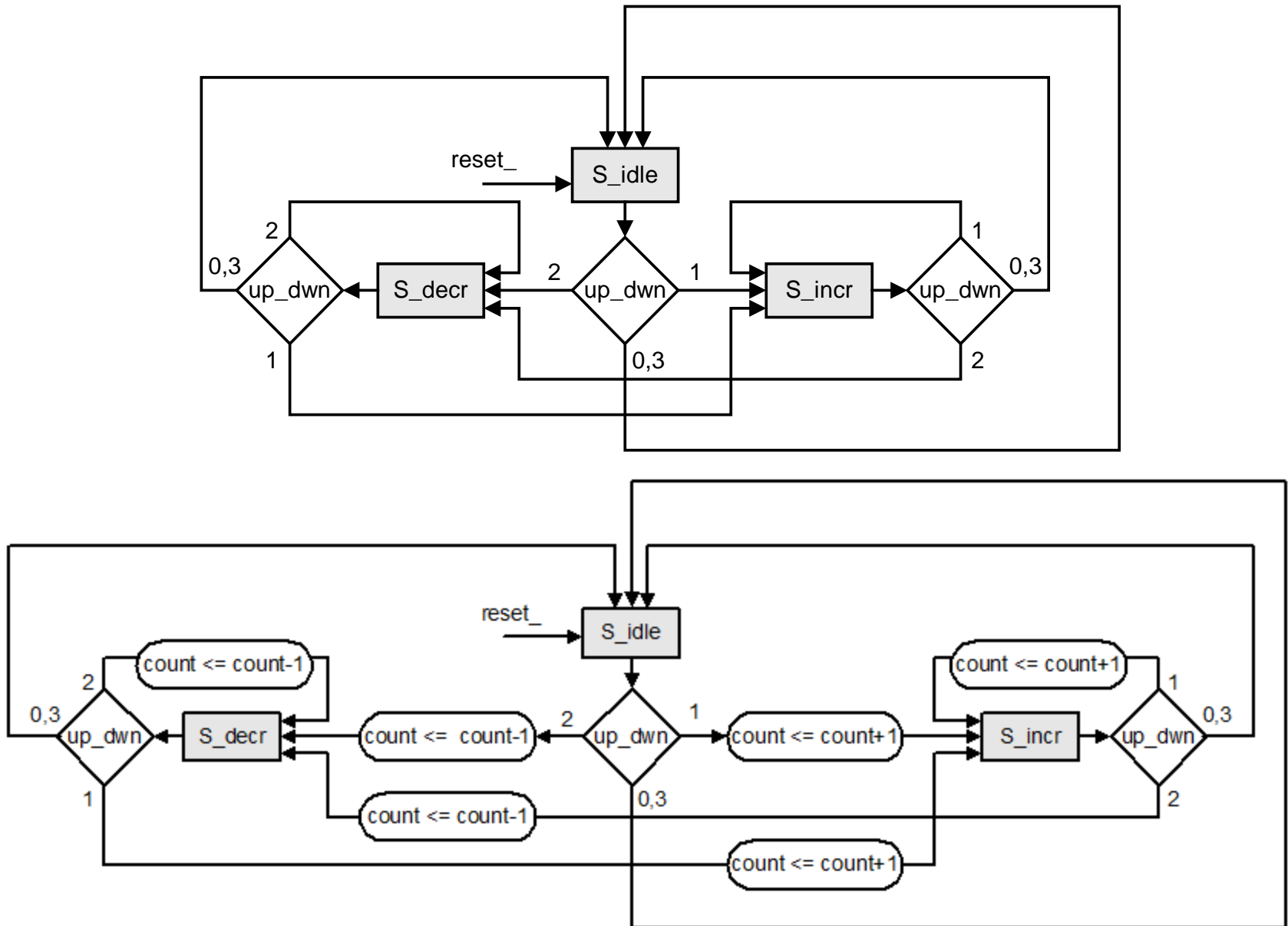

Counters (cont.)


 


Counters (3 states) with Async Reset_ (cont.)

- It is an implicit state machine
 - No explicit states (S_idle, S_incr, S_decr) used in the design
 - Implemented using if-then-else within edge-sensitive behavior


```
module Up_Down_Implicit1 (count, up_dwn, clock, reset_);  
  output [2: 0]    count;  
  input  [1: 0]    up_dwn;  
  input          clock, reset_  
  
  reg [2: 0] count;  
  
  always @ (negedge clock or negedge reset_)  
    if (reset_ == 0) count <= 3'b0; else  
      if (up_dwn == 2'b00 || up_dwn == 2'b11) count <= count; else  
        if (up_dwn == 2'b01) count <= count + 1; else  
          if (up_dwn == 2'b10) count <= count - 1;  
  
endmodule
```

  Simplified Counter ASMDs with Async/Sync Reset_



Ring Counter

 - Ring counter asserts a single bit that circulates through the counter in a synchronous manner



Ring Counter (cont.)

- Activity of the machine is the same in every clock cycle
- This implementation is an implicit state machine


```
module ring_counter (count, enable, clock, reset);
  output          [7: 0]    count;
  input           enable, reset, clock;
  reg             [7: 0]    count;

  always @ (posedge reset or posedge clock)
    if (reset == 1'b1) count <= 8'b0000_0001; else
      if (enable == 1'b1) count <= {count[6: 0], count[7]}; // Concatenation operator
endmodule
```

```
VHDL:: count <= count[6: 0] & count[7];
```

Up/Down/Load Counter

```
module up_down_counter (Count, Data_in, load, count_up, counter_on, clk, reset);  
  output          [2: 0]    Count;  
  input           load, count_up, counter_on, clk, reset,;  
  input          [2: 0]    Data_in;  
  reg            [2: 0]    Count;  
  
  always @ (posedge reset or posedge clk)  
    if (reset == 1'b1) Count <= 3'b0; else  
      if (load == 1'b1) Count <= Data_in; else  
        if (counter_on == 1'b1) begin  
          if (count_up == 1'b1) Count <= Count +1;  
          else Count <= Count -1;  
        end  
  endmodule
```

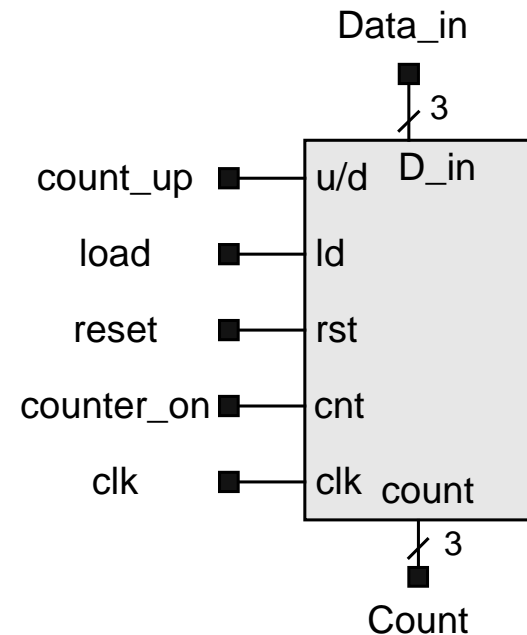

Shift Register

- Remember the “model trap”
 - Must use **nonblocking** assignments in this design

```
module Shift_reg4 (Data_out, Data_in, clock, reset);
```

```
  output          Data_out;
```

```
  input           Data_in, clock, reset;
```

```
  reg    [3: 0]   Data_reg;
```

```
  assign Data_out = Data_reg[0];
```

```
  always @ (negedge reset or posedge clock)
```


```
  begin
```

```
    if (reset == 1'b0) Data_reg <= 4'b0;
```

```
    else Data_reg <= {Data_in, Data_reg[3:1]}; //shift right
```

```
  end
```


```
endmodule
```

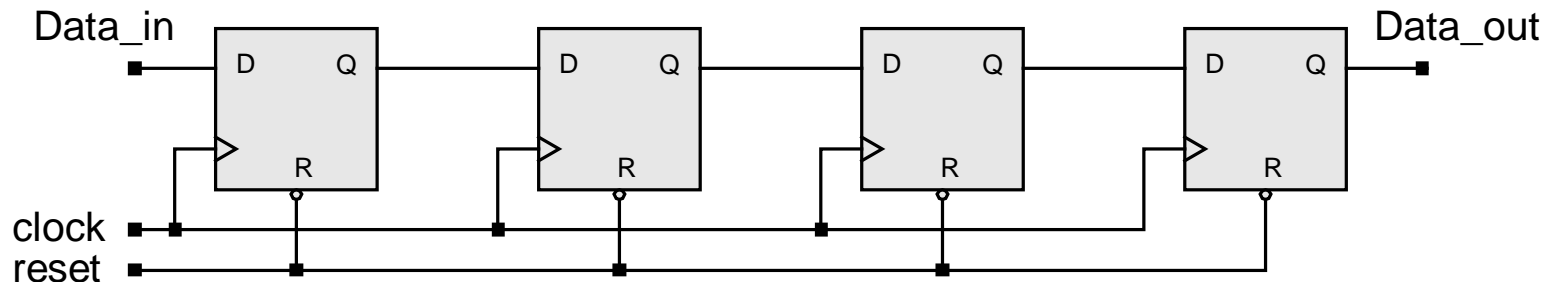

Parallel Load Register

- MUX is synthesized from “else if (load==1'b1)”
 - How about “else” i.e. (load==1'b0)?
 - If not specified, retain the previous value

```
module Par_load_reg4 (Data_out, Data_in, load, clock, reset);  
  input  [3: 0]  Data_in;  
  input        load, clock, reset;  
  output [3: 0]  Data_out;          // Port size  
  reg        Data_out;             // Data type  
  always @ (posedge reset or posedge clock)  
  begin  
    if (reset == 1'b1)  
      Data_out <= 4'b0;  
    else if (load == 1'b1)  
      Data_out <= Data_in;  
  end  
endmodule
```

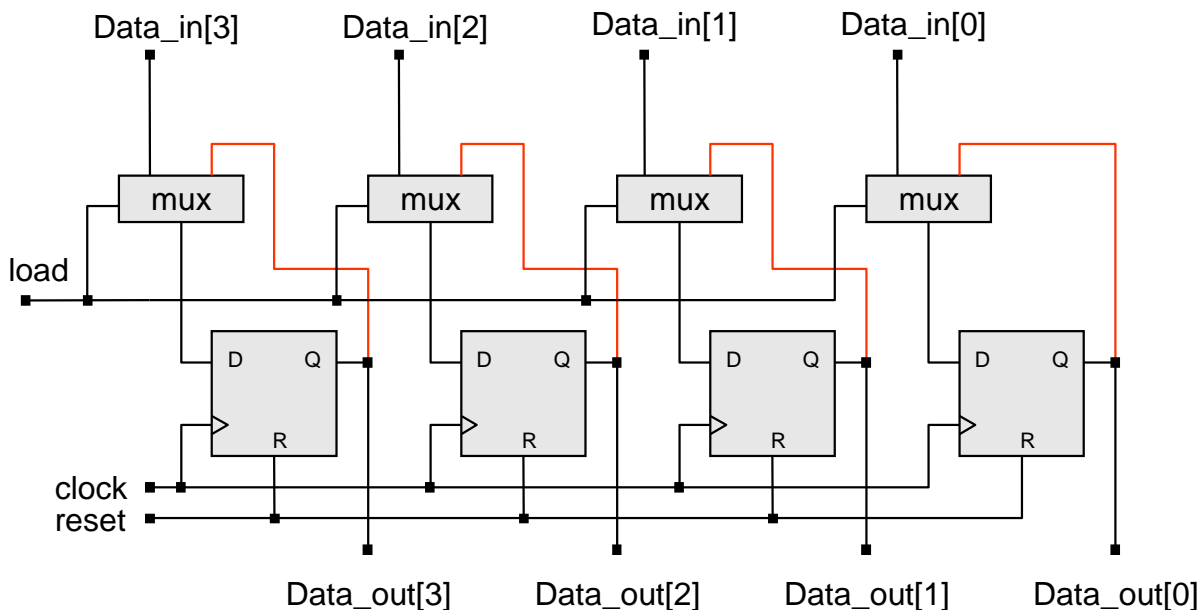

Shift Registers

- Shift register with parallel load
 - later
- Arithmetic shift register
 - For signed number operation
 - MSB is preserved
 - Shift-left: multiply by 2
 - Shift-right: divide by 2

Universal Shift Register

```
module Universal_Shift_Reg
```

```
(Data_Out, MSB_Out, LSB_Out, Data_In, MSB_In, LSB_In, s1, s0, clk, rst);
```

```
output [3: 0] Data_Out;
```

```
output MSB_Out, LSB_Out;
```

```
input [3: 0] Data_In;
```

```
input MSB_In, LSB_In;
```

```
input reg s1, s0, clk, rst;
```

```
reg Data_Out;
```

```
assign MSB_Out = Data_Out[3];
```

```
assign LSB_Out = Data_Out[0];
```

```
always @ (posedge clk) begin
```

```
if (rst) Data_Out <= 0;
```

```
else case ({s1, s0})
```

```
0: Data_Out <= Data_Out;
```

```
// Hold
```

```
1: Data_Out <= {MSB_In, Data_Out[3:1]};
```

```
// Serial shift from MSB
```

```
2: Data_Out <= {Data_Out[2: 0], LSB_In};
```

```
// Serial shift from LSB
```


```
3: Data_Out <= Data_In;
```

```
// Parallel Load
```


```
endcase
```

```
end
```

```
endmodule
```

 

Register File

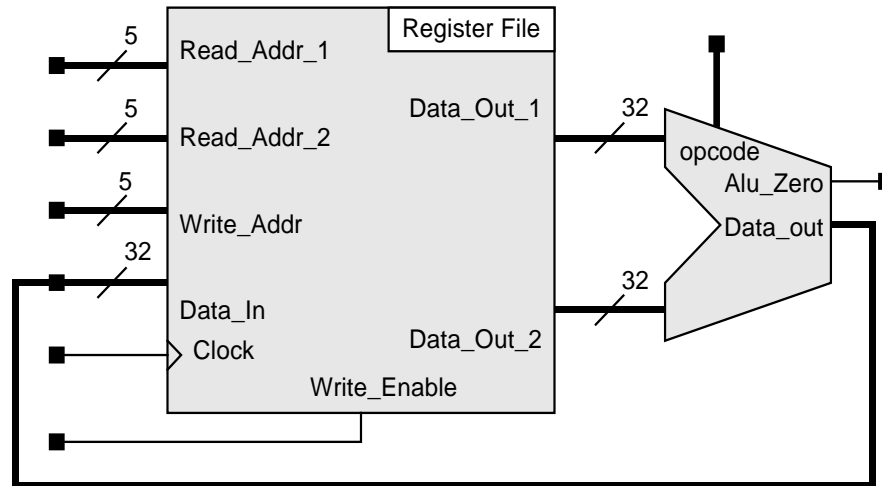

```
module Register_File (Data_Out_1,Data_Out_2,Data_in,  
                    Read_Addr_1,Read_Addr_2,Write_Addr,Write_Enable,Clock);  
  
    output [31: 0]    Data_Out_1, Data_Out_2;  
    input  [31: 0]    Data_in;  
    input  [4: 0]     Read_Addr_1, Read_Addr_2, Write_Addr;  
    input  Write_Enable, Clock;  
    reg    [31: 0]    Reg_File [31: 0];    // 32bit x32 word memory declaration  
  
    assign Data_Out_1 = Reg_File[Read_Addr_1];  
    assign Data_Out_2 = Reg_File[Read_Addr_2];  
    always @ (posedge Clock) begin  
        if (Write_Enable) Reg_File [Write_Addr] <= Data_in;  
    end  
endmodule
```

“Concept of Memory” in Verilog

- Memory
 - Declaration an array of words
 - E.g. `reg [31:0] data_out; // one 32-bit word`
`reg [31:0] Reg_file [31:0]; // 32x32 bit word memory`
- Verilog does not support 2-dimensional array
 - However, a word in a Verilog memory can be addressed directly
 - E.g., `Reg_file [12]`
 - A cell bit in a word can also be addressed indirectly by first loading the word into a buffer register then addressing the bit of the word
 - E.g. `Data_out = Reg_file [12];`
`Data_out [1:0]`
- Decoder are synthesized automatically by synthesis tool in `Reg_file[]` to decode the address which locates a specific register