

# RFIC Design and Testing for Wireless Communications

**A PragaTI (TI India Technical University) Course**  
**July 18, 21, 22, 2008**

## **Lecture 9: Frequency synthesizer design II (VCO)**

**By**

**Vishwani D. Agrawal**  
**Fa Foster Dai**

**200 Broun Hall, Auburn University**  
**Auburn, AL 36849-5201, USA**

# RFIC Design and Testing for Wireless Communications

## Topics

### Monday, July 21, 2008


9:00 – 10:30	Introduction – Semiconductor history, RF characteristics
11:00 – 12:30	Basic Concepts – Linearity, noise figure, dynamic range
2:00 – 3:30	RF front-end design – LNA, mixer
4:00 – 5:30	Frequency synthesizer design I (PLL)

### Tuesday, July 22, 2008

9:00 – 10:30	Frequency synthesizer design II (VCO)
11:00 – 12:30	RFIC design for wireless communications
2:00 – 3:30	Analog and mixed signal testing


# Phase Noise Specification of Oscillators

Example of oscillator periodic waveforms

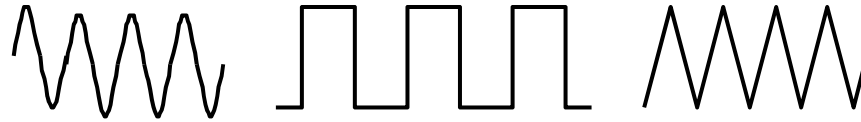

- **Phase noise.** We desire accurate periodicity with all signal power concentrated in one discrete oscillator frequency  $\rightarrow$  an impulse function in frequency domain. However, all real oscillators have less than perfect spectral purity and thus they develop “skirts”. Power in the skirts is evidence of phase noise, Phase noise is any noise that changes the frequency or phase of the oscillator waveform. Phase noise is given by:

$$PN = \frac{P_o}{N_o}$$

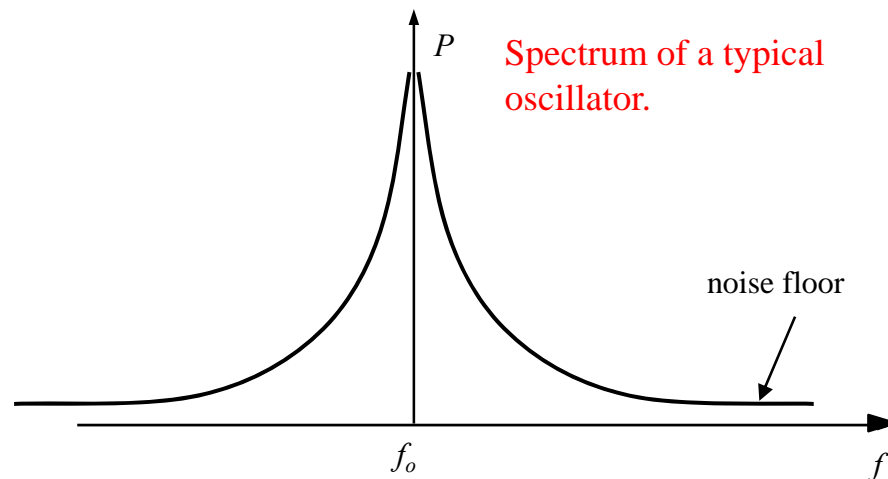


- Where  $P_o$  is the power in the tone at the frequency of oscillation and  $N_o$  is the noise power spectral density at some specified offset from the carrier. Phase noise is usually specified in  **$\text{dBc/Hz}$** , meaning noise a 1-Hz bandwidth measured in decibels with respect to the carrier.
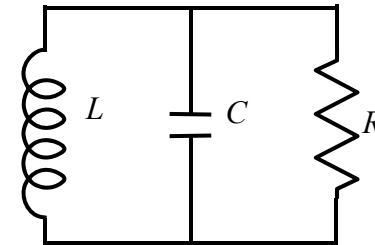
## LC Resonator – Core of Oscillators

- If  $i(t) = I_{pulse} \delta(t)$  is applied to a parallel resonator, the time domain response of the system can be found as:

$$v_{out} = \frac{\sqrt{2}I_{pulse}e^{\frac{-t}{2RC}}}{C} \cos\left(\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}} \cdot t\right)$$




- Oscillation frequency

$$\omega_{osc} = \sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$$


- In most oscillators,  $|R| \gg \sqrt{L/C}$

$$\omega_{osc} = \sqrt{\frac{1}{LC}}$$

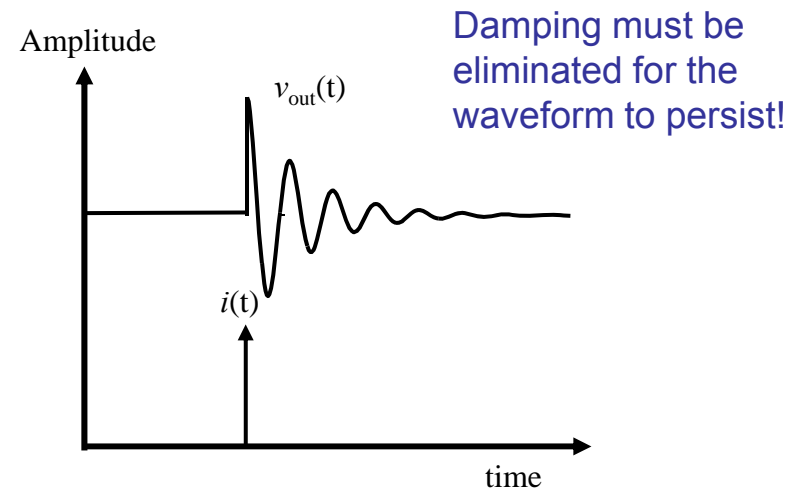


Damped LC resonator with current step applied.
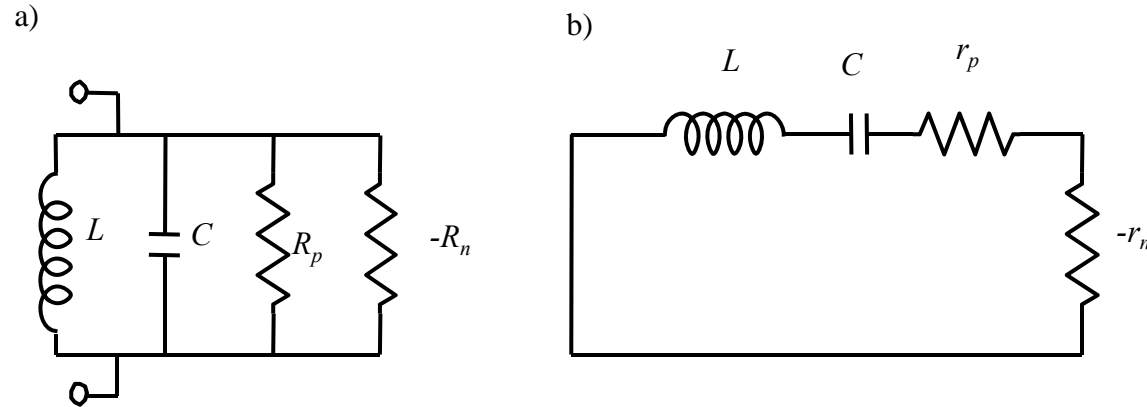
## Adding Negative Resistance Trough Feedback to Resonator



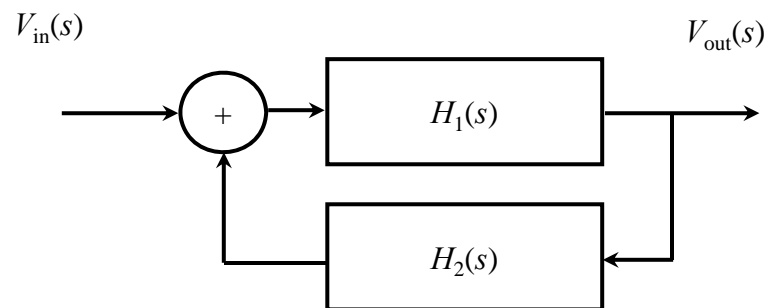The addition of negative resistance to the circuit to overcome losses in a) a parallel resonator or b) a series resonator.



Linear model of an oscillator as a feedback control system.

## Barkhausen Criterion

- Closed loop gain

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{H_1(s)}{1 - H_1(s)H_2(s)}$$

- Condition for oscillation: denominator approaches zero. → To find the closed-loop poles

$$1 - H_1(s)H_2(s) = 0$$

- For sustained oscillation at constant amplitude, the pole must be on the  $j\omega$  axis. For the open-loop analysis

$$H_1(j\omega)H_2(j\omega) = 1$$


positive feedback  
with gain larger  
than or equal to 1.

- Barkhausen criterion, which states that for sustained oscillation at constant amplitude, the gain around the loop is 1 and the phase around the loop is 0 or some multiple of  $2\pi$ .**

$$|H_1(j\omega)||H_2(j\omega)| = 1$$

$$\angle H_1(j\omega)H_2(j\omega) = 2n\pi$$


## VCO Output Spectral Purity

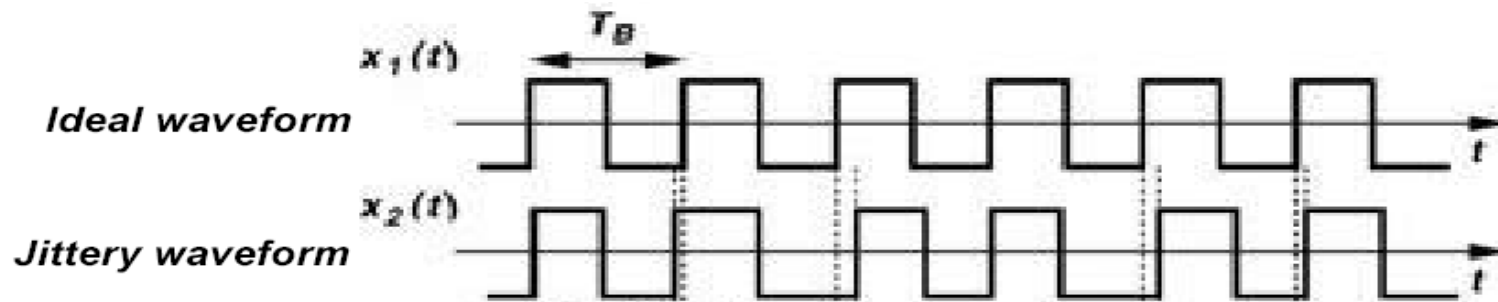

Noise in one sideband in a 1Hz bandwidth:


$$L_{\text{total}}(\Delta\omega) = \frac{\text{noise power in 1Hz BW at } \omega_0 + \Delta\omega}{\text{Carrier power}}$$

Units: dBc/Hz

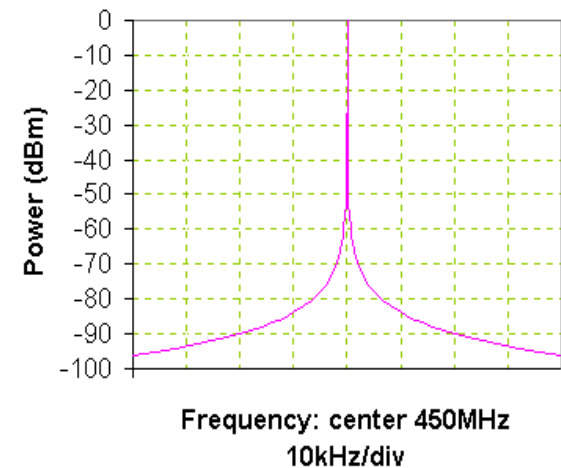


VCO Output Spectrum
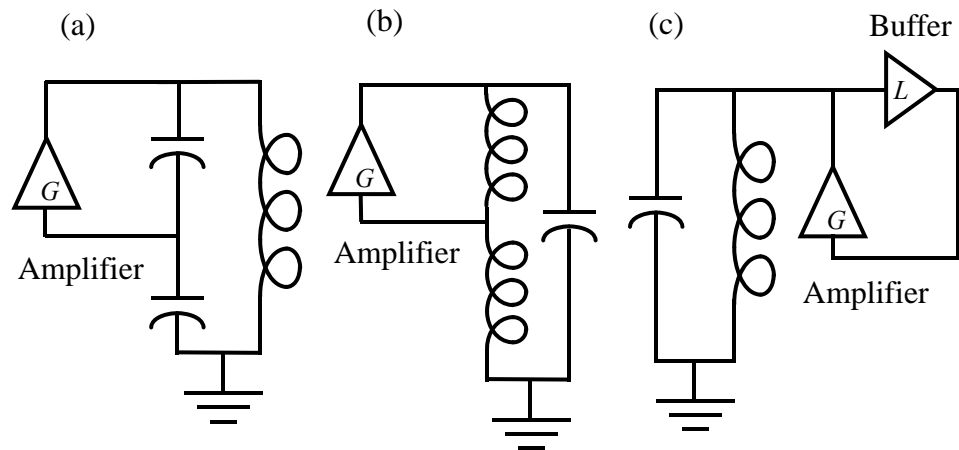
## Popular Implementation of Feedback to Resonator



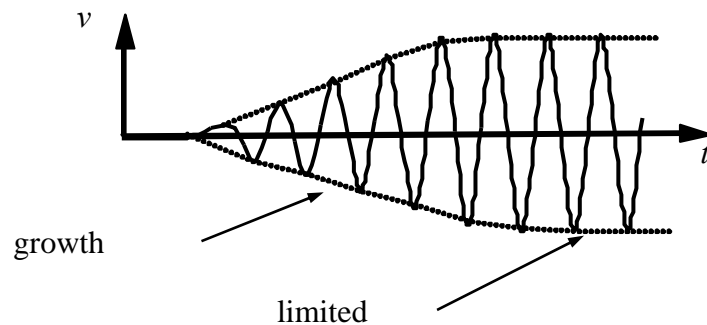Resonators with feedback. (a) Colpitts Oscillator.  
(b) Hartley Oscillator (not suitable for IC). (c)  $-G_m$  oscillator.




Waveform of an LC resonator with losses compensated. The oscillation grows until a practical constraint limits the amplitude.


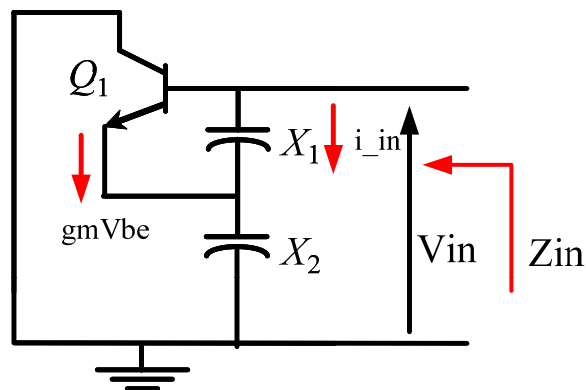
# Negative Resistance of Colpitts Amplifier

$$v_{in} = i_{in}(jX_1 + jX_2) + g_m v_{be}(jX_2)$$

Negative Impedance, if  $X_1$  and  $X_2$  are the same type



$$Z_{in} = \frac{v_{in}}{i_{in}} = -g_m X_1 X_2 + j(X_1 + X_2)$$

$$Z_{in} = -\frac{g_m}{\omega^2 C_1 C_2} + \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$

To start the oscillation,


$$\begin{aligned} -g_m X_1 X_2 &> R_L \\ g_m &> R_L \omega^2 C_1 C_2 \end{aligned}$$

Load reactance needs to equal  $-j(X_1 + X_2) \rightarrow$  add an inductor

Oscillation frequency

$$f_{osc} = \frac{1}{2\pi} \left[ \frac{1}{L_3} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \right]^{1/2}$$

## Negative Resistance of –Gm Oscillator

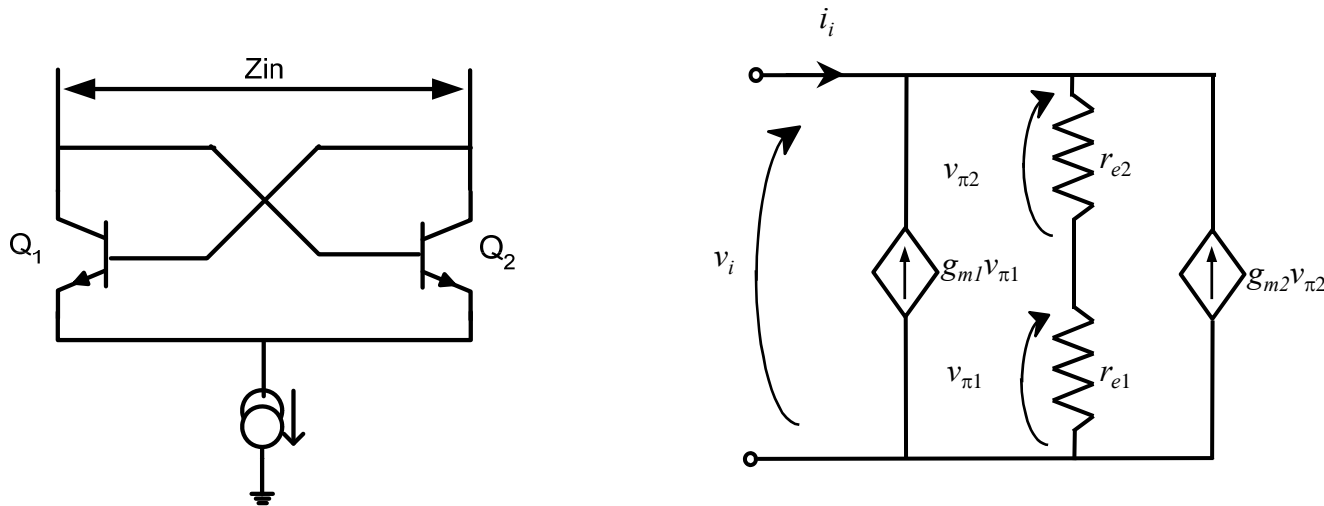

$$i_i = \frac{v_i}{r_{e1} + r_{e2}} = -g_{m1}v_{\pi1} - g_{m2}v_{\pi2}$$

- Both transistors are biased identically,  $Z_i = \frac{-2}{g_m}$

- Condition for oscillation is that  $g_m > \frac{2}{R_p}$

where  $R_p$  is the equivalent parallel resistance of the resonator.

# VCO Mathematical Model

Output frequency of an ideal VCO:

$$\omega_{out} = \omega_{FR} + K_{vco} V_c$$

Sinusoidal output:  $y(t) = A \cos( \omega_{FR} t + K_{vco} \int_{-\infty}^t V_C )$

Open loop Q :


$$Q = \frac{\omega_0}{2} \left| \frac{d\phi}{d\omega} \right|$$

$\omega_0$  is the center frequency


$\phi$  is the phase of open loop transfer function
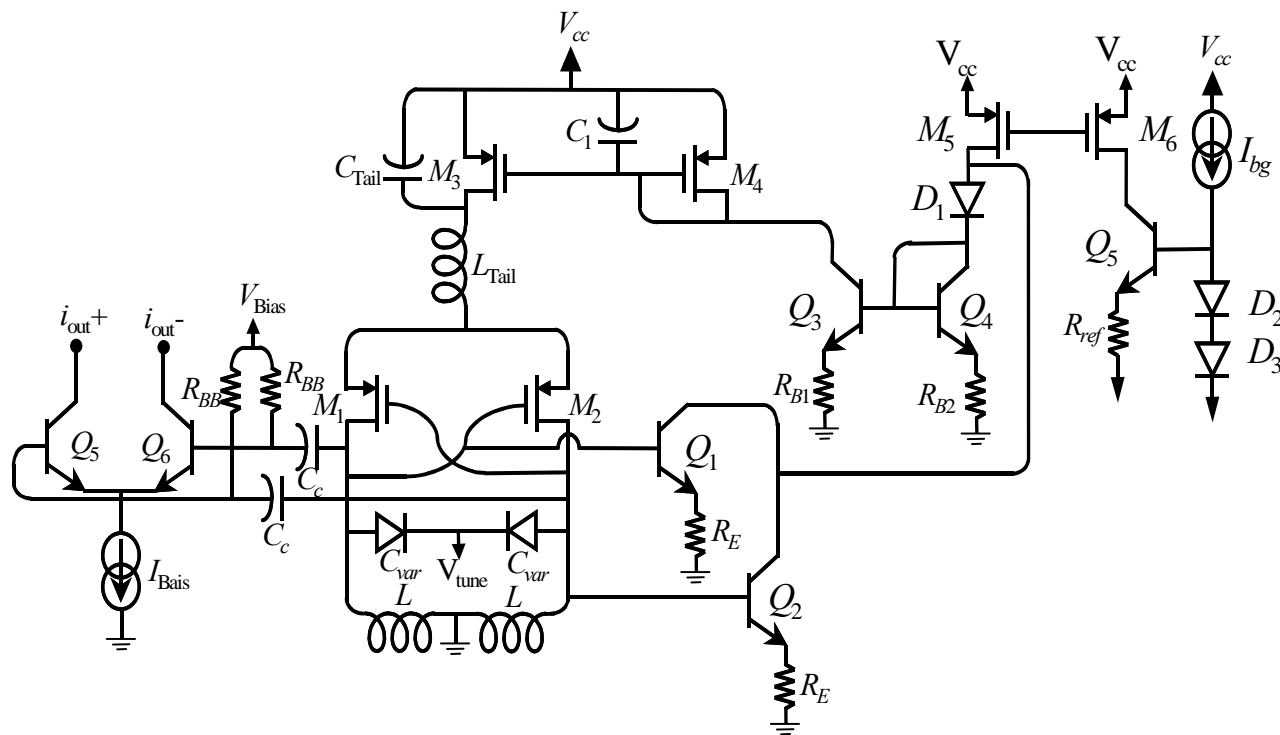
# PMOS VCO with Automatic Amplitude Control

- Large  $V_{\text{tune}}$  range (almost from 0V ~  $V_{\text{cc}}$  V).
- Tank can be connected to ground rather than DC  $\rightarrow$  lower phase noise and diodes can be connected in the proper polarity without additional biasing.
- PMOS transistors can be operated into saturation without affecting the VCO noise performance  $\rightarrow$  higher output swing than bipolar VCO.
- High phase noise below 100kHz offset (due to high flicker noise)  $\rightarrow$  can be tolerated by wider loop bandwidth ( $>100\text{kHz}$ ).


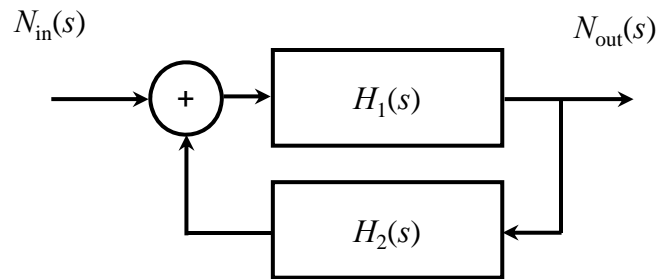
## Linear or Addictive Phase Noise -- Leeson's Formula



### Oscillator Phase Noise $\Phi_n(t)$

$$V_{osc} = A \cos[\omega_0 t + \phi_n(t)]$$

- Noise close loop transfer function

$$\frac{N_{out}(s)}{N_{in}(s)} = \frac{H_1(s)}{1 - H(s)}$$

- Open loop transfer function  
 $H(s) = H_1(s)H_2(s)$

$$H(j\omega) \approx H(j\omega_0) + \Delta\omega \frac{dH}{d\omega}$$

- Oscillation conditions  $H(j\omega_0) = 1 \longrightarrow H_1(j\omega_0) = H_1$

- Noise power

$$\left| \frac{N_{out}(s)}{N_{in}(s)} \right|^2 = \frac{|H_1|^2}{(\Delta\omega)^2 \left| \frac{dH}{d\omega} \right|^2}$$

# Oscillator Phase Noise – Leeson's Equation

$$H(\omega) = |H|e^{j\phi}$$

$$\frac{dH}{d\omega} = \frac{d|H|}{d\omega} e^{j\phi} + |H| j e^{j\phi} \frac{d\phi}{d\omega}$$

ignorable

dominant

$$\left| \frac{dH}{d\omega} \right|^2 = \left| \frac{d|H|}{d\omega} \right|^2 + |H|^2 \left| \frac{d\phi}{d\omega} \right|^2$$

Orthogonal

- At resonance, the phase changes much faster than magnitude, and  $|H|=1$  near resonance. → ignore amplitude noise and AM to PM conversion as well.

$$\left| \frac{dH}{d\omega} \right|^2 = \left| \frac{d\phi}{d\omega} \right|^2$$



$$\left| \frac{N_{out}(s)}{N_{in}(s)} \right|^2 = \frac{|H_1|^2}{(\Delta\omega)^2 \left| \frac{d\phi}{d\omega} \right|^2}$$

$$Q = \frac{\omega_0}{2} \left| \frac{d\phi}{d\omega} \right|$$



$$\left| \frac{N_{out}(s)}{N_{in}(s)} \right|^2 = \frac{|H_1|^2 \omega_0^2}{4Q^2 (\Delta\omega)^2}$$

# Oscillator Phase Noise – Leeson's Equation

- If feedback path is unity, then  $H_1=H$ , and since  $|H|=1$  near resonance

$$\left| \frac{N_{out}(s)}{N_{in}(s)} \right|^2 = \frac{\omega_0^2}{4Q^2(\Delta\omega)^2}$$

- Phase noise is quoted as an absolute noise referred to the carrier power

$$PN = \frac{|N_{out}(s)|^2}{2P_s} = \left( \frac{|H_1|\omega_0}{(2Q\Delta\omega)} \right)^2 \left( \frac{|N_{in}(s)|}{2P_s} \right)$$


- $P_s$  is the signal power at active device input.
- If the transistor and bias were noiseless, then the only noise present would be due to the resonator losses. The transistors and the bias will add noise to the minimum noise of

$$|N_{in}(s)|^2 = kT$$

# Oscillator Phase Noise – Leeson's Equation
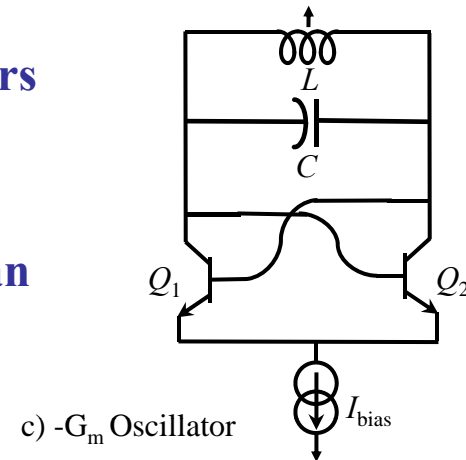
## Active Device noise:

- If  $\rho$  is the fraction of cycle for which the transistors are completely switched,  $i_{nt}$  is the noise current injected into the oscillator from the bias during this time.
- During transitions (1-  $\rho$ ), the transistors act like an amplifier, and collector shot noise  $i_{cn}$  usually dominates.



$R_p$  is the equivalent parallel resistance of the tank.

$$|N_{in}(s)|^2 = kT + \frac{i_{nt}^2 R_p}{2} \rho + i_{cn}^2 R_p (1 - \rho)$$

Resonator loss  
(source)

Bias noise

Transistor shot noise

$$F = 1 + \frac{i_{nt}^2 R_p}{2kT} \rho + \frac{i_{cn}^2 R_p (1 - \rho)}{kT}$$

$$PN = \left( \frac{|H_1| \omega_0}{(2Q\Delta\omega)} \right)^2 \left( \frac{FkT}{2P_s} \right)$$




# Oscillator Phase Noise – Leeson's Equation


- It has been assumed that **flicker noise** is insignificant at the frequencies of interest. This may not be the case for CMOS designs. If  $\omega_c$  represents the flicker noise corner where flicker noise and thermal noise are equal, phase noise is given by

$$PN = \left( \frac{|H_1|\omega_0}{(2Q\Delta\omega)} \right)^2 \left( \frac{FkT}{2P_s} \right) \left( 1 + \frac{\omega_c}{\Delta\omega} \right)$$

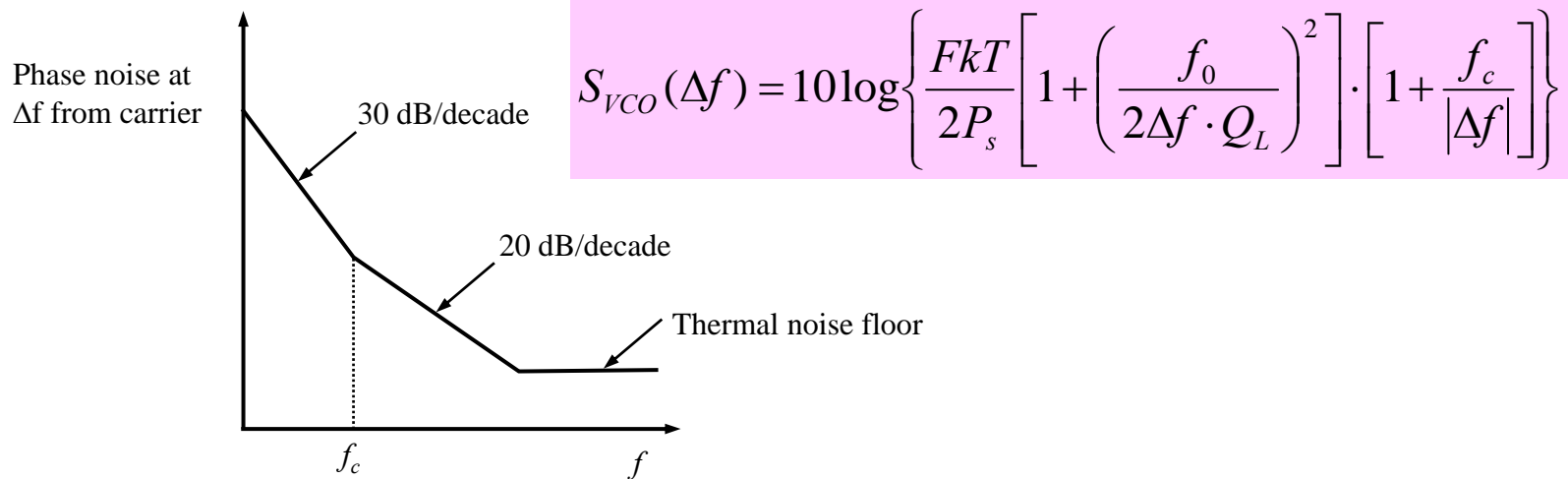
- Assuming unity feedback, oscillator output spectrum density




## Simulated PLL Phase Noise Sources

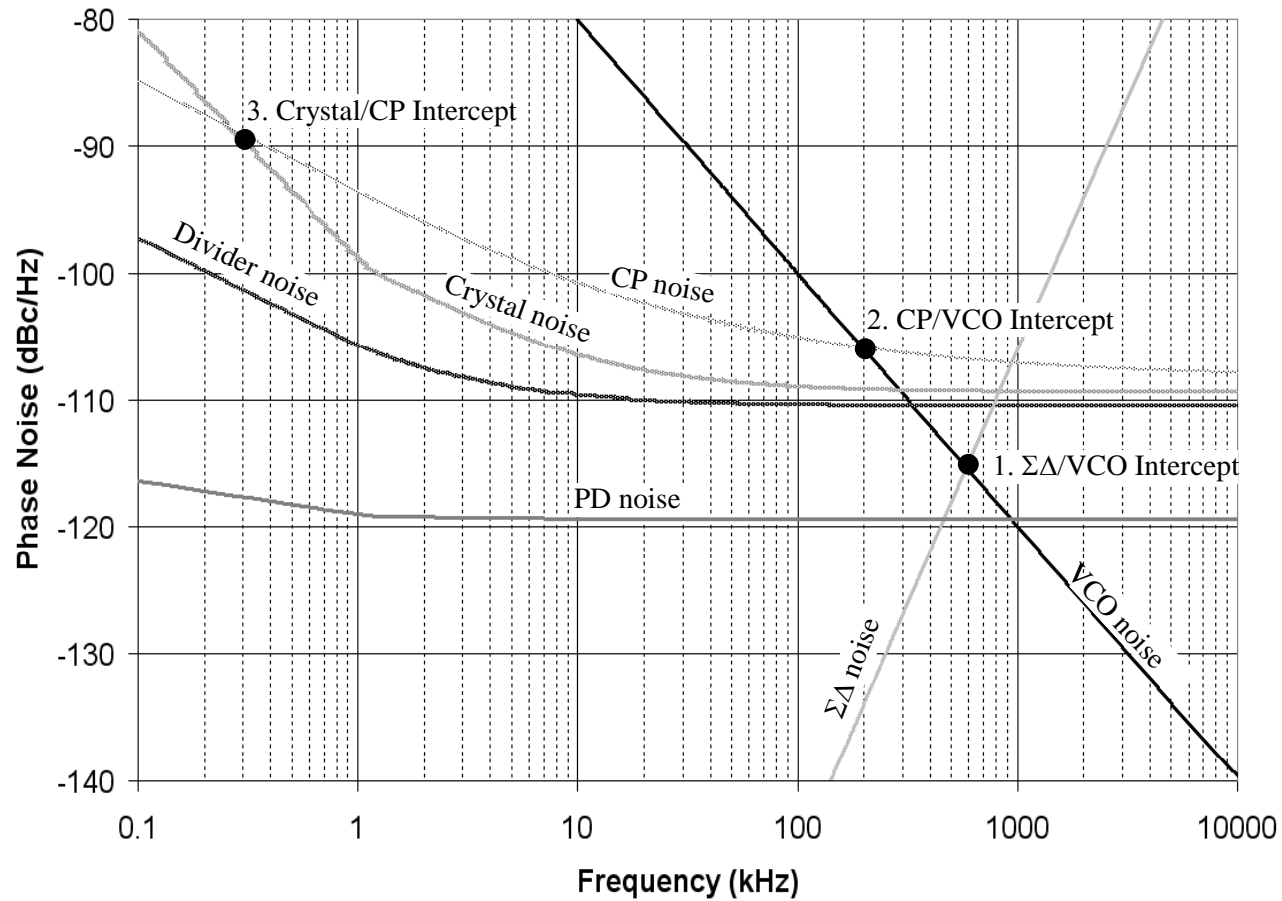
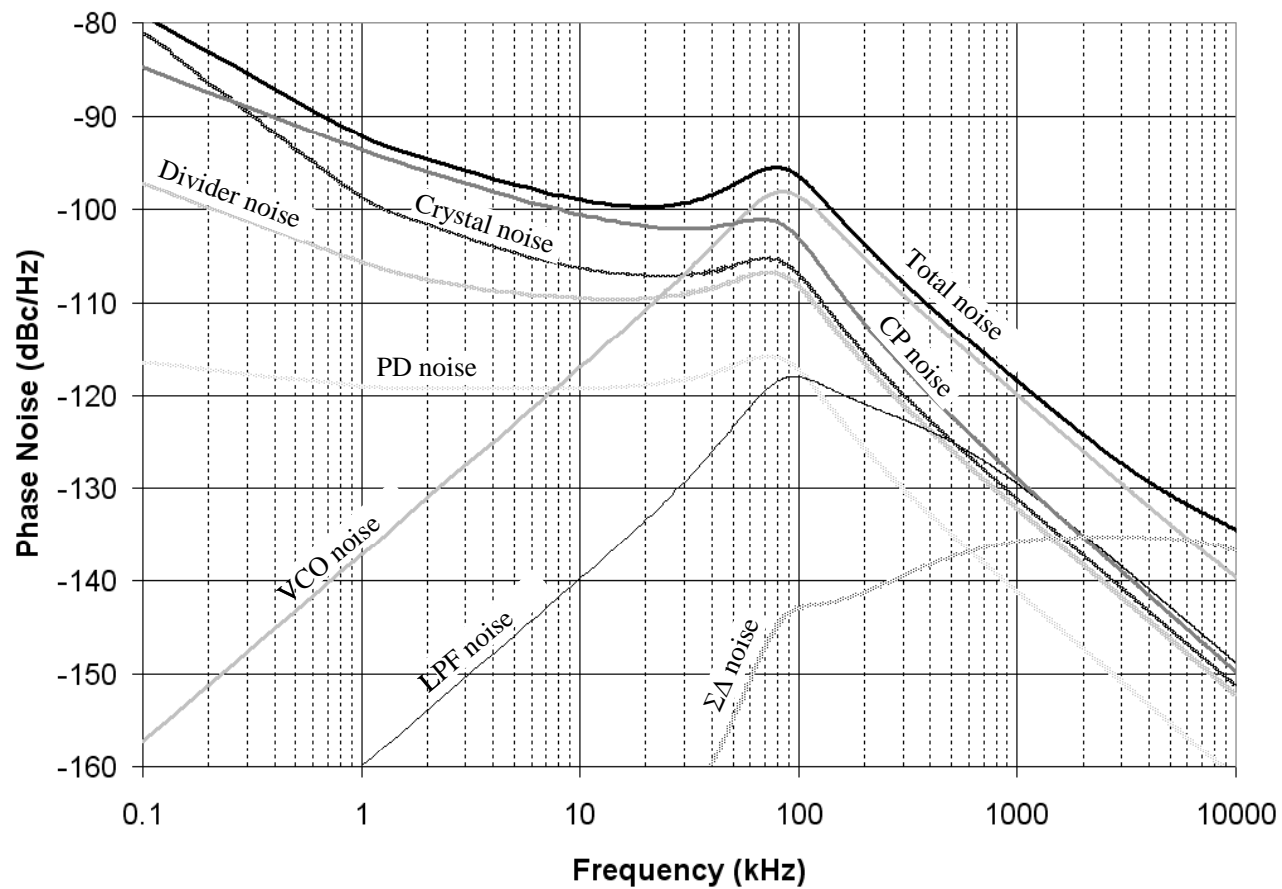
## Simulated PLL Phase Noise With Loop Effect


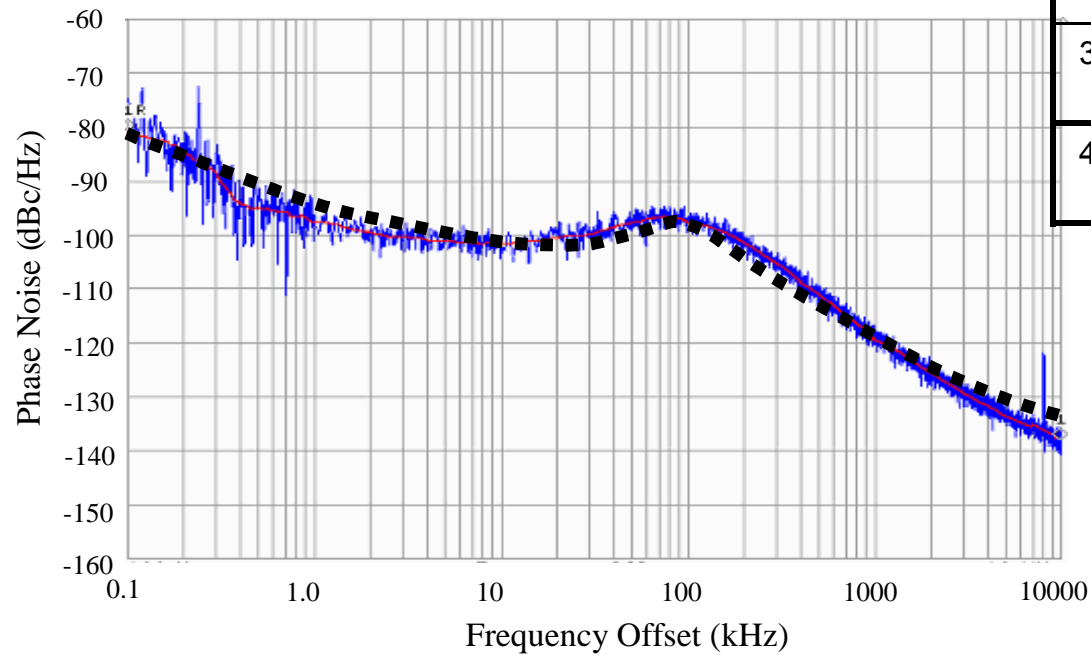
## Comparison of measured and simulated phase noise



Frequency Band	Simulated Phase Noise	Measured Phase Noise
3.2-3.3GHz	0.44°rms	0.50°rms
4.1-4.3GHz	0.50°rms	0.535°rms

Parameter	Value
$C_1$	3nF
$C_2$	600pF
$R$	600Ω