



AUBURN  
UNIVERSITY

# Optional MECH 3140 Lecture: Driving Motors and Op-Amps

David Bevly




# How to supply a negative voltage?

- Turns out that motors must be able to be driven in reverse
  - This is done by supplying a “negative” voltage
  - In reality this is done by reversing the polarity of the terminals across the motor
  - In control systems we can’t do this manually
    - Controller needs to be able to supply positive and negative voltages to the motor (i.e. turn the motor in either direction given a single supply)
  - This is done using what is called an H-bridge
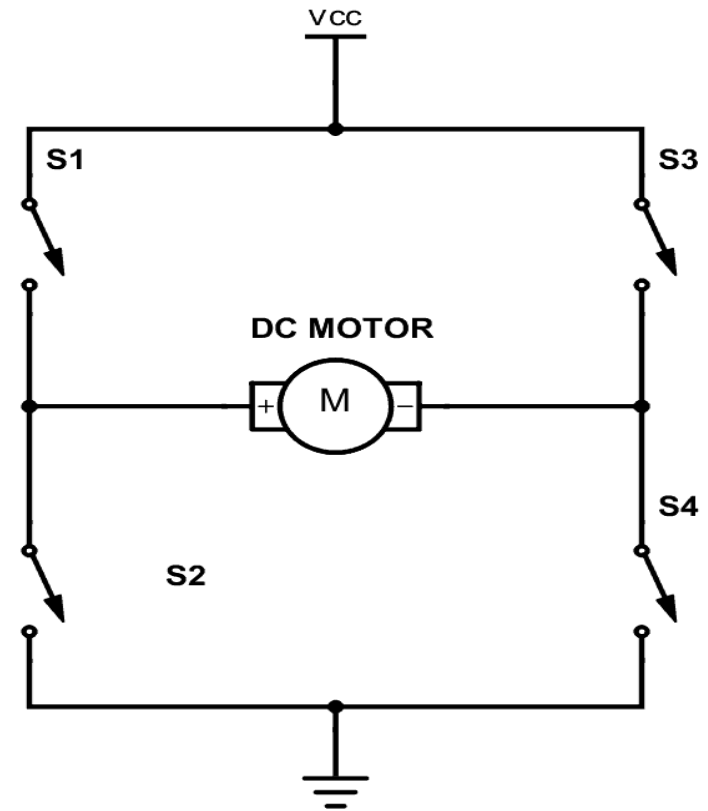
# H-bridges

- An H-bridge allows for automatically being able to swap the polarity across the motor
  - It gets its name since it looks like an H
  - The direction of the motor is set using the 4 “switches” (S1,S2,S3,S4)





<https://www.build-electronic-circuits.com/h-bridge/>

# H-Bridges

- To run “positive” voltage, close switch S1 and S4 (and open S2 and S3)


<https://www.build-electronic-circuits.com/h-bridge/>

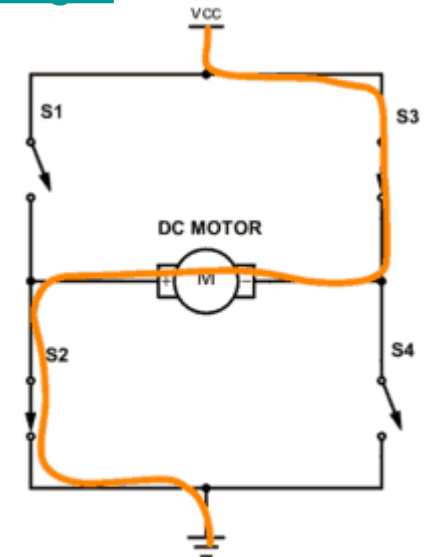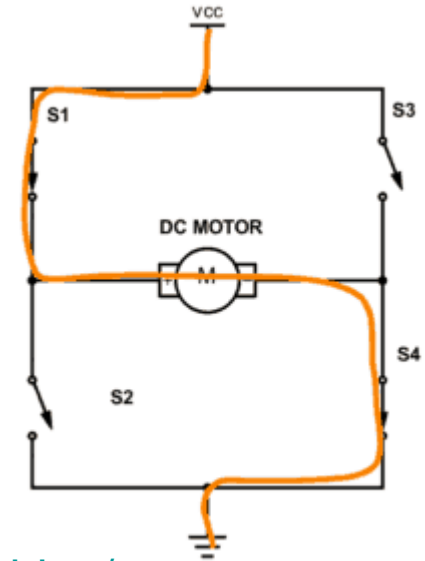- To run “negative” voltage close switch S2 and S3 (and open S1 and S4)


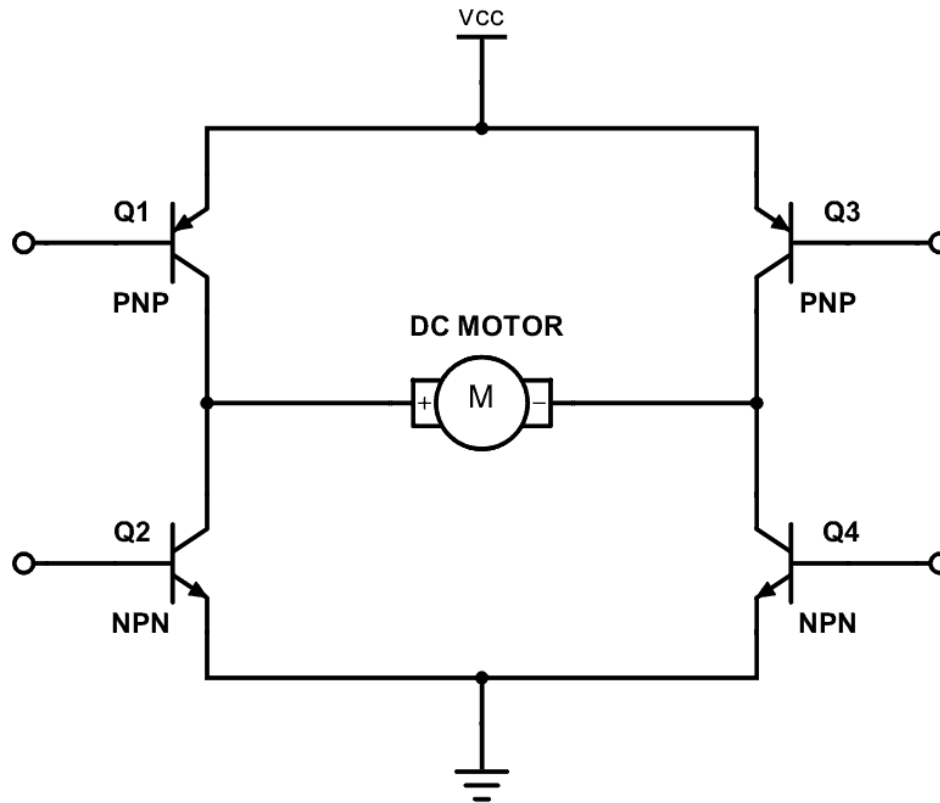
# H-Bridges

- The “switches” are controlled by transistors
  - Transistors are the EE version of valves




# How to Set Motor Voltage?

- If you have a 12 volt supply, how do you provide 6 volts?
  - You don't use a voltage divider (i.e. two resistors)
    - This is wasting energy
    - It's the mechanical equivalent of controlling your cars speed by using full throttle and partial brakes

# How to Control Motor Voltage?


- Provide the motor with a 12 volts supply
- Then turn the motor on for part of the time and off for part of the time
  - So you send 12 volts for part of the time and 0 volts part of the time
  - This is called Pulse Width Modulation (PWM)
  - Why doesn't the motor speed up and slow down?
    - Think frequency response!

# Motor $V_s=6$ Volts

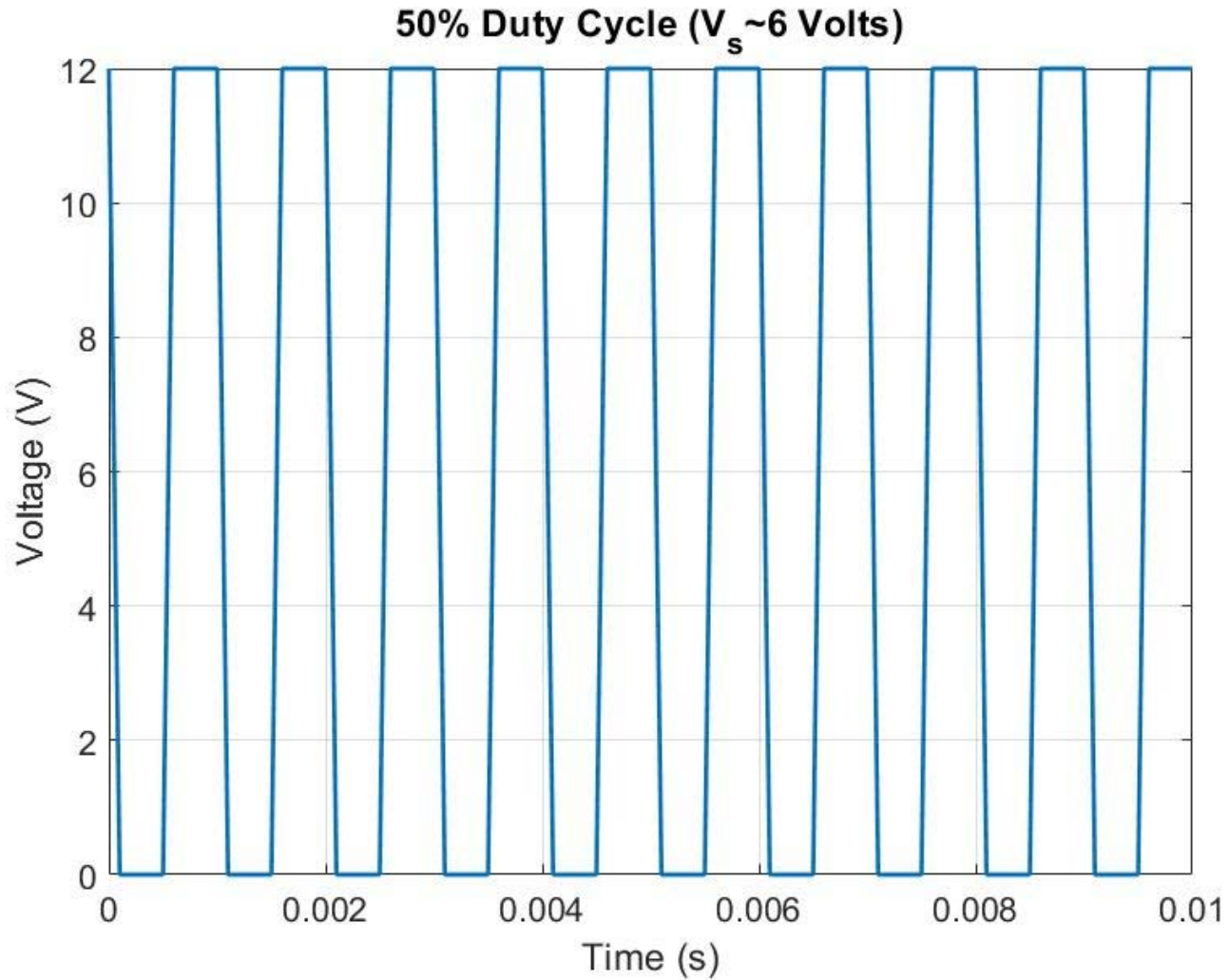




# Motor $V_s=10.8$ Volts

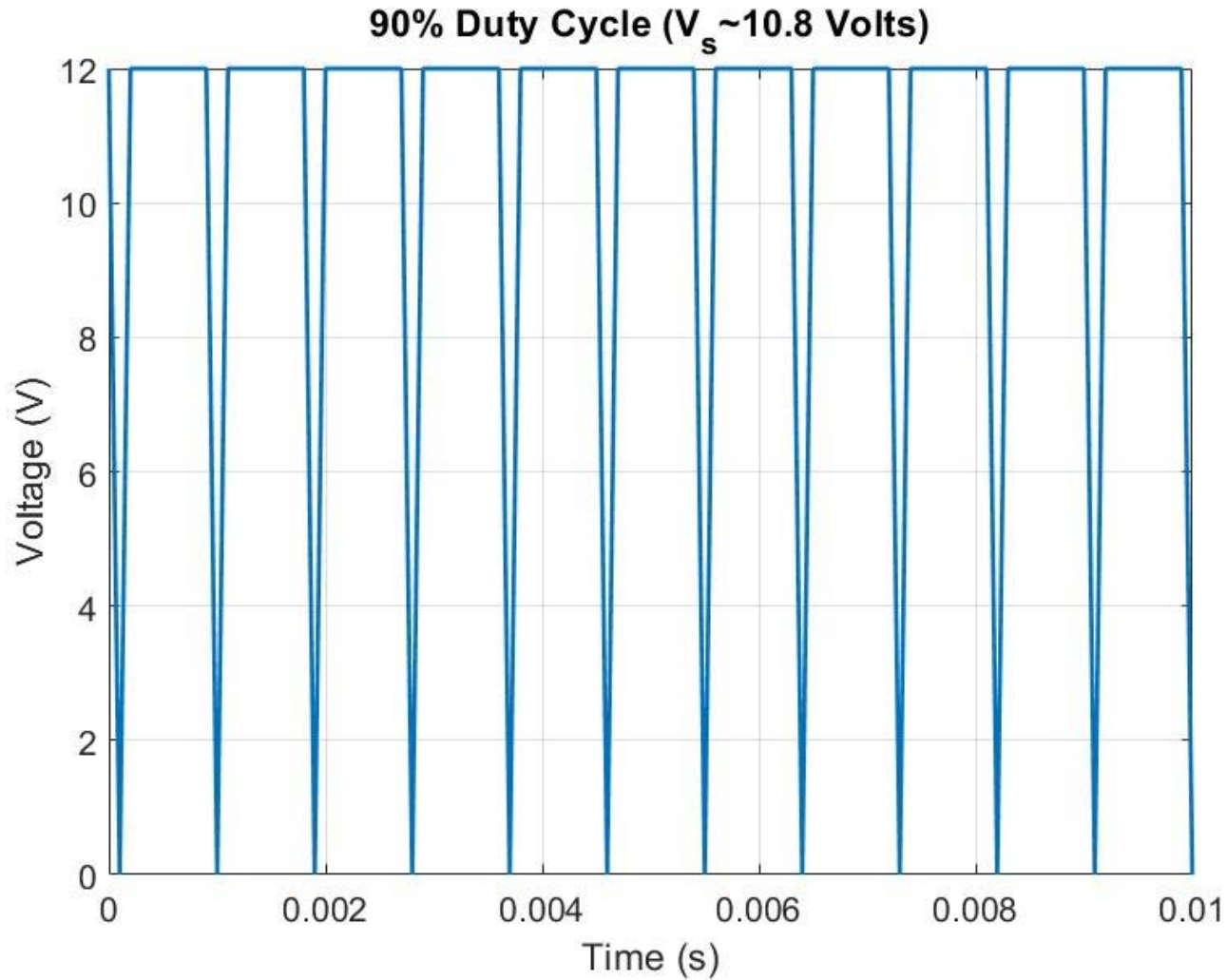

# Motor $V_s=1.2$ Volts

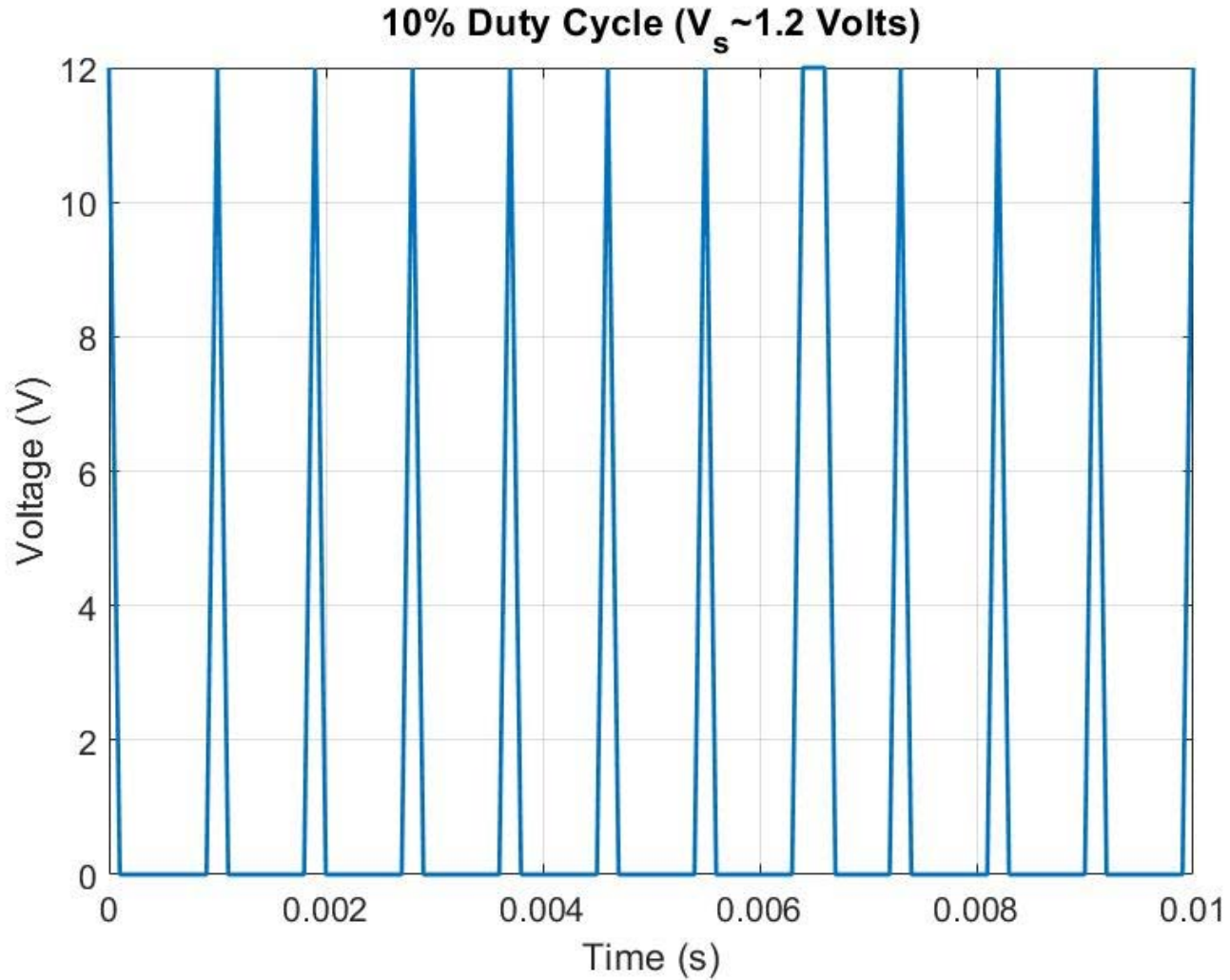

# How to Set Motor Voltage?


- PWM actually works with the H-bridge
  - Turn on and off the PNP transistors with the PWM signal
    - 12 volts supply is always connected
    - PWM signal dictates the effective percentage of the voltage to the motor
    - Direction is dictated by which PNP transistors you PWM on and off.
  - Most motor driver h-bridges actually have a supply line, ground, the two motor terminal connections, 1 direction line/bit, 1 PWM line
    - Such as the LMD18200 from Texas Instruments

# LMD18200



AIN-094

## Key Features (Continued)

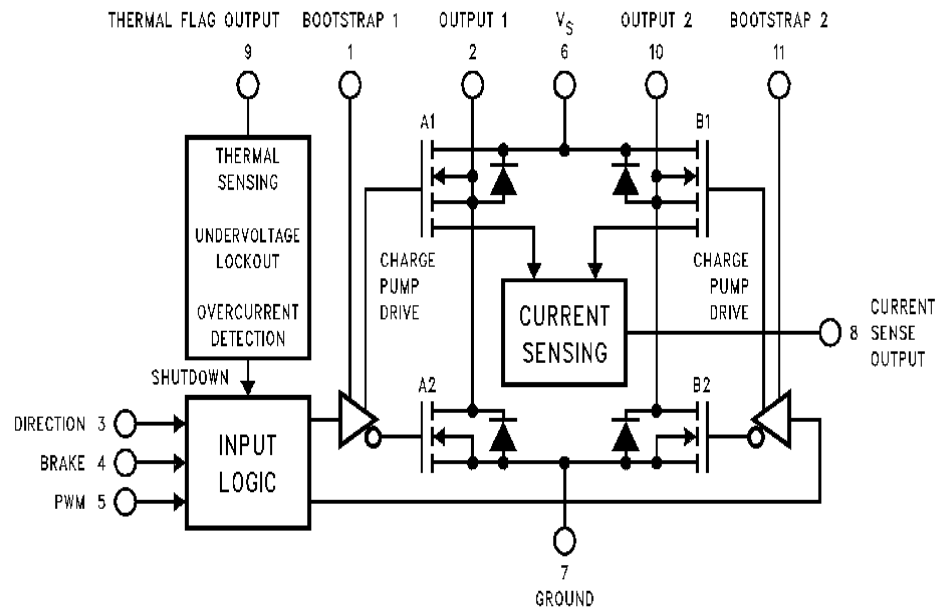


01085902

FIGURE 2. Block Diagram of the LMD18200
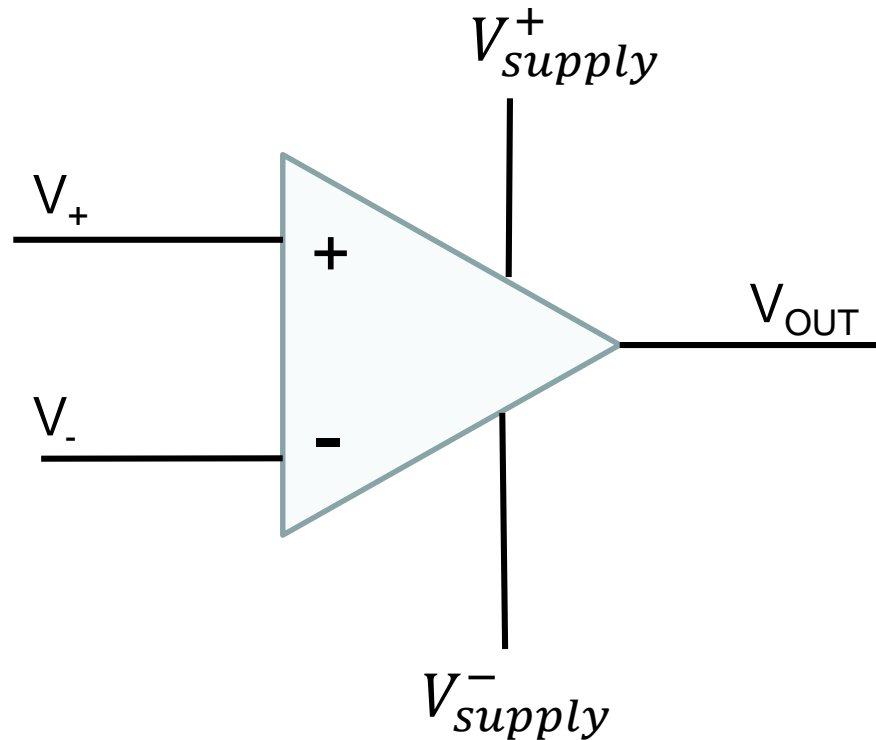
# Operational Amplifiers (Op-Amps)

- Op-amps are extremely useful for practical applications related to mechanical systems



# Op-Amp Golden Rules

- Op-Amps operate under 2 Golden Rules

$$1) I_+ = I_- = 0 \quad \& \quad 2) V_+ = V_-$$

- These dictate the operation/model/equation for the op-amp set up

- A third principle (but not a golden rule):

$$V_{supply}^+ < V_{out} < V_{supply}^-$$


- These are idealized principles

- An op-amp specification sheet will give how close to these the actual op-amp gets

- The closer the op-amp gets to these idealize principles, the more expensive the op-amp

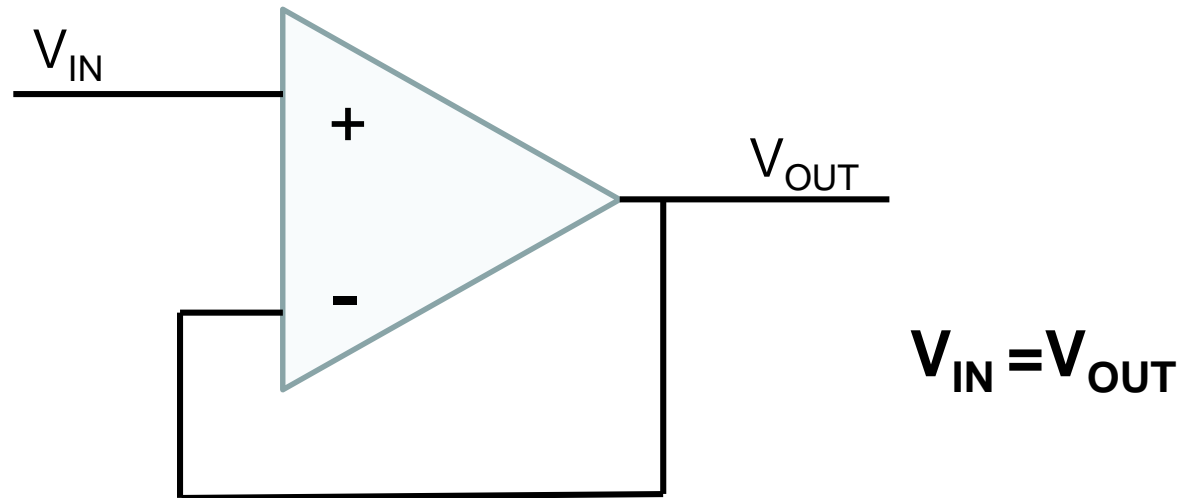
# Buffer/Follower Configuration

- What would be the point of this op-amp configuration
  - Isolates a sensor measurement
    - Since the Op-Amp doesn't draw any current (i.e. one of the golden rules)


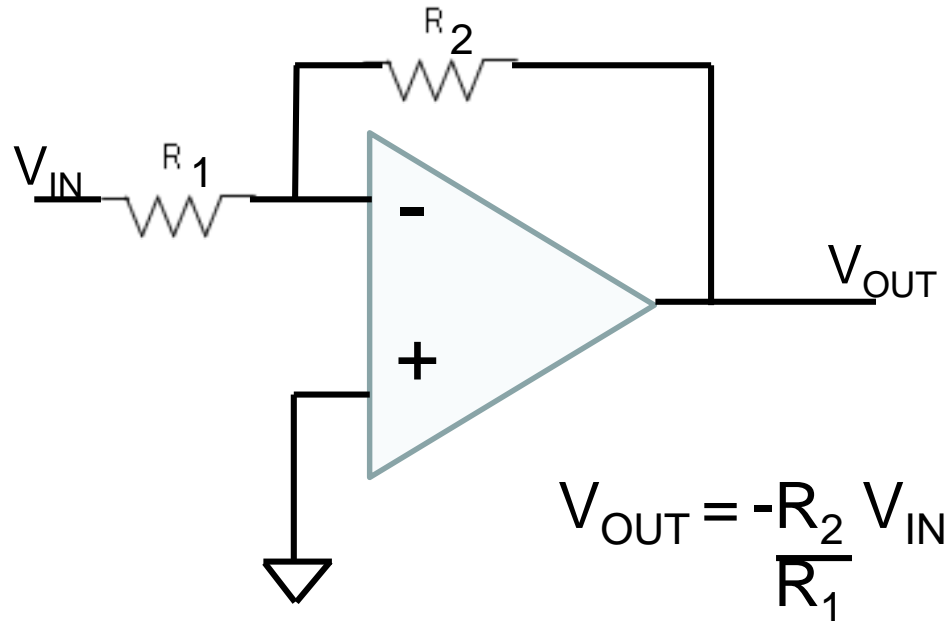
# Inverse Amplifier Configuration


- What would be the point of this op-amp configuration
  - Amplify a signal
    - Utilize the full range of a data acquisition system
    - Scale the sensor measurement to full range





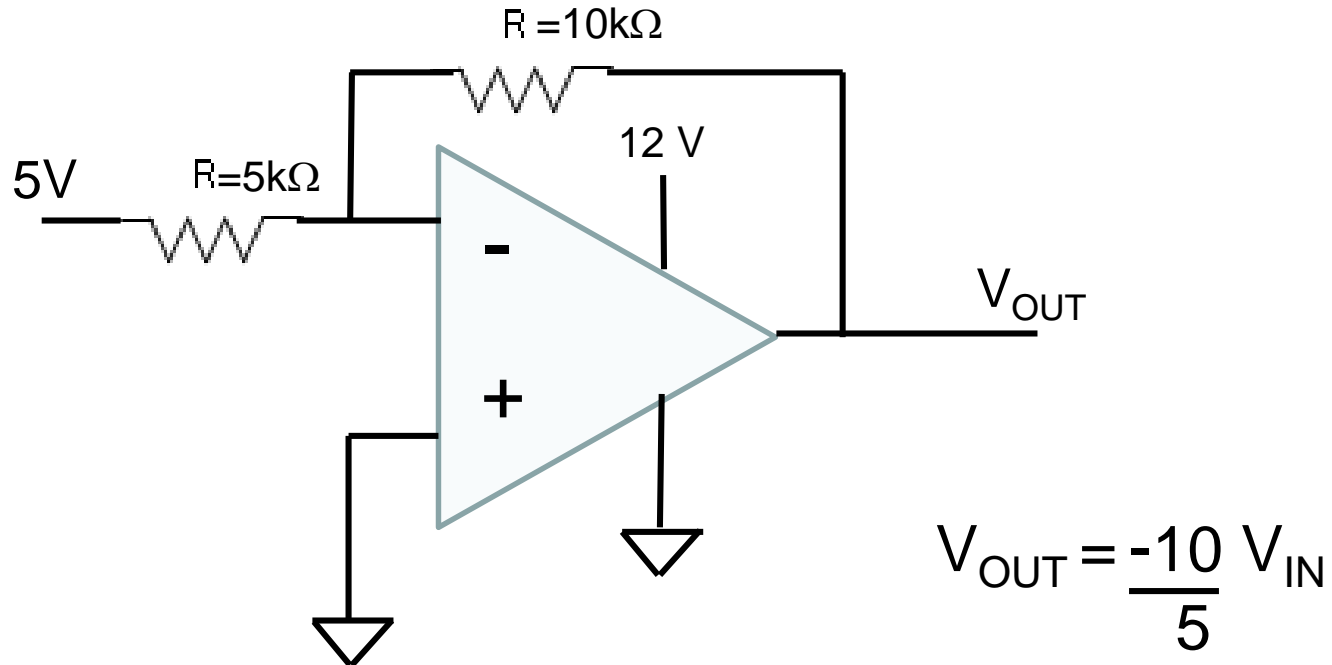
# Inverse Amplifier Configuration

- What will the output of this Op-amp be?


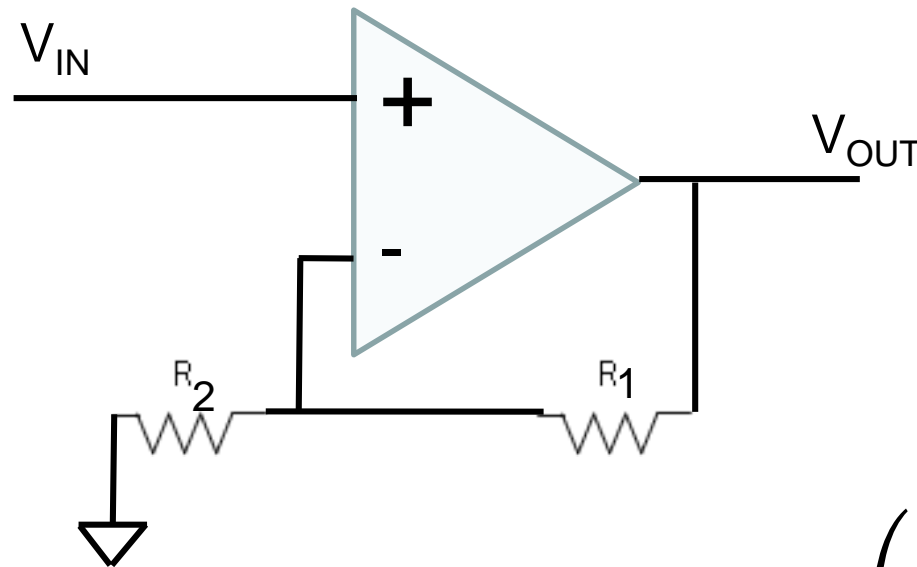
# Non-Inverting Amplifier Configuration



- Can also set up the amplifier in a “non-inverting” configuration to amplify a signal




$$V_{out} = \left( 1 + \frac{R_1}{R_2} \right) V_{in}$$
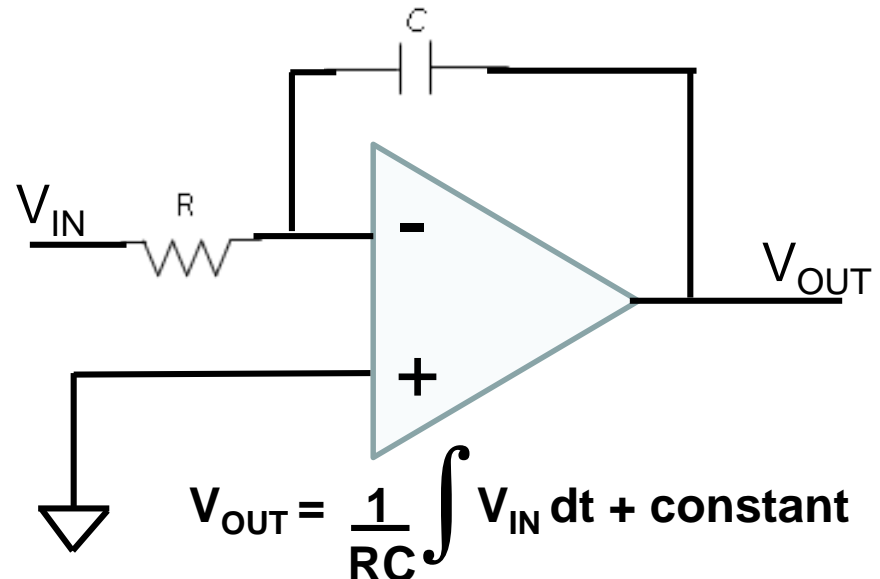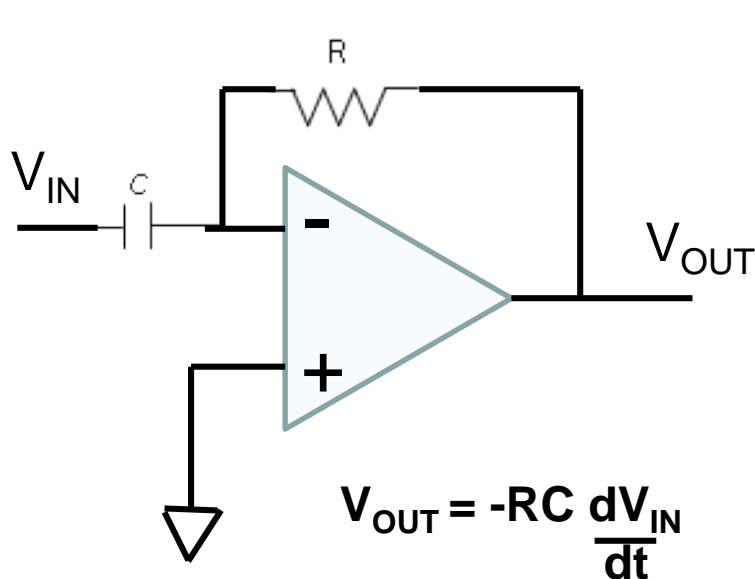
# Differentiation & Integration Configs.


- What are these used for?
  - Integrate or differentiate a signal
    - Used for I or D control
    - This is how PID controllers were primarily built
      - Not used as much now due to microcontrollers and computers
      - But some electronics are too “fast” for computer, so they must still be done in analog



# TI LM6144 Quad Op-AMP

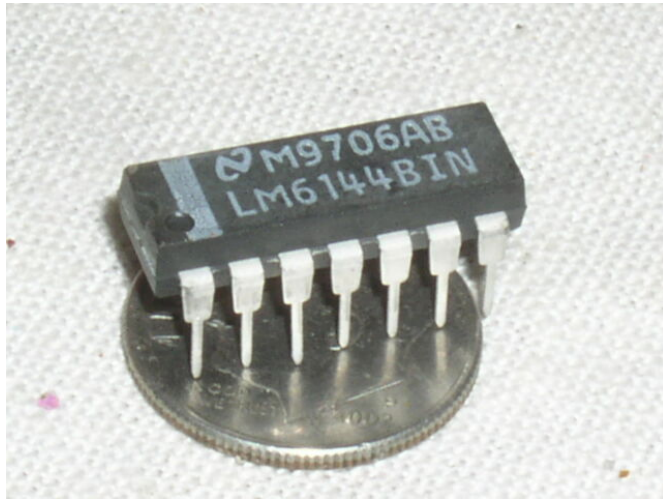

14-Pin DIP/SO

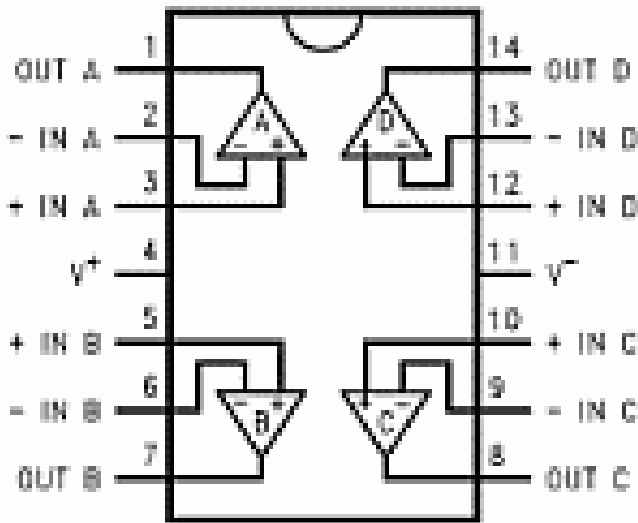

DS90C01-2

Top View

At  $V_S = 5V$ . Typ Unless Noted.

- Rail-to-rail Input CMVR  $-0.25V$  to  $5.25V$
- Rail-to-Rail Output Swing  $0.005V$  to  $4.995V$
- Wide Gain-Bandwidth:  $17MHz$  at  $50kHz$  (typ)
- Slew Rate:
  - Small Signal,  $5V/\mu s$
  - Large Signal,  $30V/\mu s$
- Low Supply Current  $650\mu A/Amplifier$
- Wide Supply Range  $1.8V$  to  $24V$
- CMRR  $107dB$
- Gain  $108dB$  with  $R_L = 10k$
- PSRR  $87dB$