

Linear Feedback Shift Registers (LFSRs)

- Efficient design for Test Pattern Generators & Output Response Analyzers (also used in CRC)


- FFs plus a few XOR gates
 - fewer gates
 - higher clock frequency
- better than counter

- Two types of LFSRs

- External Feedback
- Internal Feedback
 - higher clock frequency

- Characteristic polynomial

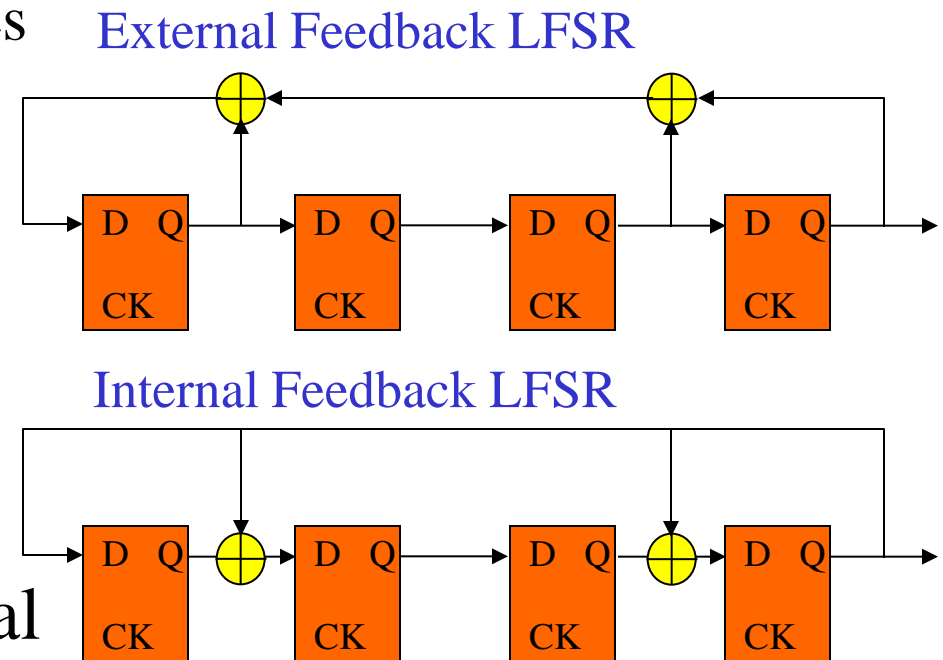
- defined by XOR positions
- $P(x) = x^4 + x^3 + x + 1$ in both examples



LFSRs (cont)

Characteristic polynomial of LFSR

- $n = \#$ of FFs = degree of polynomial
- XOR feedback connection to FF $i \Leftrightarrow$ coefficient of x^i
 - coefficient = 0 if no connection
 - coefficient = 1 if connection
 - coefficients always included in characteristic polynomial:
 - x^n (degree of polynomial & primary feedback)
 - $x^0 = 1$ (principle input to shift register)
- Note: state of the LFSR \Leftrightarrow polynomial of degree $n-1$
- Example: $P(x) = x^3 + x + 1$

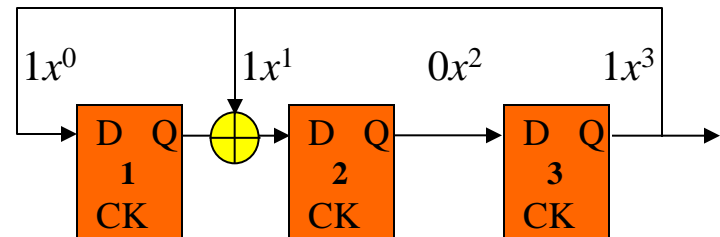


LSFRs (cont)

- An LFSR generates periodic sequence
 - must start in a non-zero state,
- The maximum-length of an LFSR sequence is $2^n - 1$
 - does not generate all 0s pattern (gets stuck in that state)
- The characteristic polynomial of an LFSR generating a maximum-length sequence is a ***primitive polynomial***
- A maximum-length sequence is ***pseudo-random***:
 - number of 1s = number of 0s + 1
 - same number of runs of consecutive 0s and 1s
 - 1/2 of the runs have length 1
 - 1/4 of the runs have length 2
 - ... (as long as fractions result in integral numbers of runs)

LFSRs (cont)

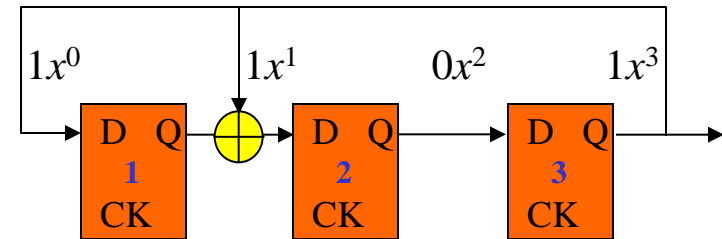- Example: Characteristic polynomial is $P(x) = x^3 + x + 1$
- Beginning at all 1s state

- 7 clock cycles to repeat
- maximal length = $2^n - 1$
- polynomial is primitive



- Properties:

- four 1s and three 0s
- 4 runs:

- 2 runs of length 1 (one 0 & one 1)
- 1 run of length 2 (0s)
- 1 run of length 3 (1s)

1	1	1	1
1	0	1	2
1	0	0	3
0	1	0	4
0	0	1	5
1	1	0	6
0	1	1	7
1	1	1	

- Note: external & internal LFSRs with same primitive polynomial do not generate same sequence (only same length)

LFSRs (cont)

- Reciprocal polynomial, $P^*(x)$
 - $P^*(x) = x^n P(1/x)$
 - example: $P(x) = x^3 + x + 1$
 - then: $P^*(x) = x^3 (x^{-3} + x^{-1} + 1) = 1 + x^2 + x^3 = x^3 + x^2 + 1$
 - if $P(x)$ is primitive, $P^*(x)$ is also primitive
 - same for non-primitive polynomials
- Polynomial arithmetic
 - modulo-2 ($x^n + x^n = x^n - x^n = 0$)

Addition/Subtraction

$$\begin{array}{r}
 (x^5 + x^2 + 1) + (x^4 + x^2) \\
 x^5 \qquad \qquad x^2 \qquad 1 \\
 + \quad x^4 \qquad x^2 \\
 \hline
 x^5 \quad x^4 \qquad \qquad 1 \\
 = x^5 + x^4 + 1
 \end{array}$$

Multiplication

$$\begin{array}{r}
 (x^2 + x + 1) \times (x^2 + 1) \\
 \qquad \qquad \qquad x^2 + x + 1 \\
 \qquad \qquad \times \quad x^2 + 1 \\
 \hline
 \qquad \qquad \qquad x^2 + x + 1 \\
 x^4 + x^3 + x^2 \\
 \hline
 = x^4 + x^3 + x + 1
 \end{array}$$


Division

$$\begin{array}{r}
 \qquad \qquad \qquad x^2 + x + 1 \\
 x^2 + 1 \overline{) x^4 + x^3 + x + 1} \\
 \underline{x^4 \quad + x^2} \\
 \qquad \qquad x^3 + x^2 + x + 1 \\
 \underline{x^3 \qquad \quad + x} \\
 \qquad \qquad \qquad x^2 + 1 \\
 \underline{x^2 + 1} \\
 \qquad \qquad \qquad \qquad \qquad 0
 \end{array}$$

LFSRs (cont)


- Non-primitive polynomials produce sequences $< 2^n - 1$
 - Typically primitive polys desired for TPGs & ORAs
- Example of non-primitive polynomial
 - $P(x) = x^3 + x^2 + x + 1$

External Feedback LFSR

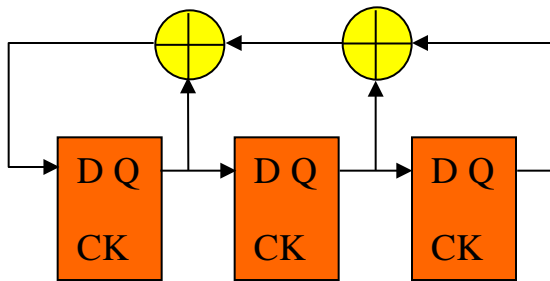

$\begin{array}{c} 0\ 0\ 0 \\ \hline 0\ 0\ 0 \end{array}$	$\begin{array}{c} 1\ 1\ 1 \\ \hline 1\ 1\ 1 \end{array}$	$\begin{array}{c} 1\ 0\ 0 \\ 1\ 1\ 0 \\ 0\ 1\ 1 \\ \hline 0\ 0\ 1 \\ 1\ 0\ 0 \end{array}$	$\begin{array}{c} 0\ 1\ 0 \\ \hline 1\ 0\ 1 \\ 0\ 1\ 0 \end{array}$
--	--	---	---

Internal Feedback LFSR

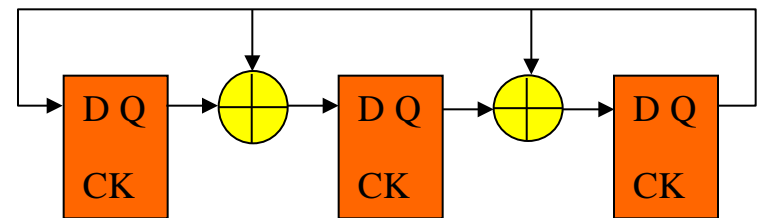

$\begin{array}{c} 0\ 0\ 0 \\ \hline 0\ 0\ 0 \end{array}$	$\begin{array}{c} 1\ 1\ 1 \\ 1\ 0\ 0 \\ 0\ 1\ 0 \\ \hline 0\ 0\ 1 \\ 1\ 1\ 1 \end{array}$	$\begin{array}{c} 1\ 1\ 0 \\ \hline 0\ 1\ 1 \\ 1\ 1\ 0 \end{array}$	$\begin{array}{c} 1\ 0\ 1 \\ \hline 1\ 0\ 1 \end{array}$
--	---	---	--

LFSRs (cont)

- Primitive polynomials with minimum # of XORs

Degree (n)	Polynomial
2,3,4,6,7,15,22	$x^n + x + 1$
5,11,21,29	$x^n + x^2 + 1$
8,19	$x^n + x^6 + x^5 + x + 1$
9	$x^n + x^4 + 1$
10,17,20,25,28	$x^n + x^3 + 1$
12	$x^n + x^7 + x^4 + x^3 + 1$
13,24	$x^n + x^4 + x^3 + x + 1$
14	$x^n + x^{12} + x^{11} + x + 1$
16	$x^n + x^5 + x^3 + x^2 + 1$
18	$x^n + x^7 + 1$
23	$x^n + x^5 + 1$
26,27	$x^n + x^8 + x^7 + x + 1$
30	$x^n + x^{16} + x^{15} + x + 1$

HDL descriptions

-- VHDL model

entity LFSR is

port (CLK,PR: in bit;

Q: buffer bit_vector(4 downto 1));

end entity LFSR;

architecture RTL of LFSR is

begin

process (CLK)

begin

if (CLK'event and CLK = '1') then

if (PR = '1') then

Q <= "1111";

else

for K in 2 to 4 loop

Q(K) <= Q(K-1);

end loop;


end if;

Q(1) <= Q(4) xor Q(3);

end if;

end process;

end architecture RTL;

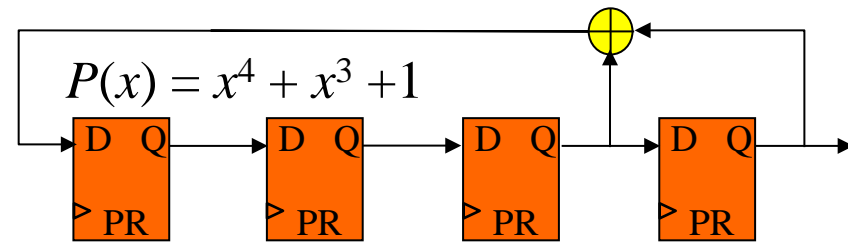

// Verilog model

module LFSR (CLK, PR, Q);

input CLK, PR;

output [4:1] Q;

/* end of "entity" portion and

beginning of "architecture" portion */

reg Q;

integer K;

always @ (posedge CLK) begin

if (PR == 1)

Q = 4'b1111;

else begin

for (K=2 ; K < 5 ; K=K+1) begin

Q[K] = Q[K-1];

end

Q[1] = Q[4] ^ Q[3];

end

end

endmodule