

# VHDL 3 – Sequential Logic Circuits

Reference: Roth/John Text: Chapter 2

# VHDL “Process” Construct

---

- ▶ Allows conventional programming language structures to describe circuit **behavior** – especially sequential behavior
  - ▶ Process statements are executed *in sequence*
  - ▶ Process statements are executed once at start of simulation
  - ▶ Process is suspended at “end process” until an event occurs on a signal in the “sensitivity list”

```
[label:] process (sensitivity list)
    declarations
begin
    sequential statements
end process;
```



# Modeling combinational logic as a process

---

-- All signals referenced in process must be in the sensitivity list.

```
entity And_Good is
```

```
    port (a, b: in std_logic; c: out std_logic);
```

```
end And_Good;
```

```
architecture Synthesis_Good of And_Good is
```

```
begin
```

```
    process (a,b)    -- gate sensitive to events on signals a and/or b
```

```
    begin
```

```
        c <= a and b; -- c updated (after delay on a or b “events”
```

```
    end process;
```

```
end;
```

-- Above process is equivalent to simple signal assignment statement:

```
--     c <= a and b;
```

---



# Bad example of combinational logic

---

-- This example produces unexpected results.

```
entity And_Bad is
```

```
    port (a, b: in std_logic; c: out std_logic);
```

```
end And_Bad;
```

```
architecture Synthesis_Bad of And_Bad is
```

```
begin
```

```
    process (a)          -- sensitivity list should be (a, b)
```

```
    begin
```

```
        c <= a and b; -- will not react to changes in b
```

```
    end process;
```

```
end Synthesis_Bad;
```

-- synthesis may generate a flip flop, triggered by signal a




# Modeling sequential behavior

---
 
## -- Edge-triggered flip flop/register

```
entity DFF is
  port (D,CLK: in bit;
        Q: out bit);
end DFF;
architecture behave of DFF is
begin
  process(clk)  -- “process sensitivity list”
  begin
    if (clk'event and clk='1') then  -- rising edge of clk
      Q <= D;                          -- optional “after x” for delay
      QB <= not D;
    end if;
  end process;
end;
```



- ▶ *clk'event* is an “attribute” of signal *clk* (*signals have several attributes*)
  - ▶ *clk'event* = TRUE if an event has occurred on *clk* at the current simulation time  
FALSE if no event on *clk* at the current simulation time
  - ▶ *clk'stable* is a complementary attribute (TRUE of no event at this time)



# Edge-triggered flip-flop

---

- Special functions in package `std_logic_1164` for `std_logic` types
  - `rising_edge(clk)` = TRUE for 0->1, L->H and several other “rising-edge” conditions
  - `falling_edge(clk)` = TRUE for 1->0, H->L and several other “falling-edge” conditions

## Example:

```
signal clk: std_logic;
begin
  process (clk)                                -- trigger process on clk event
  begin
    if rising_edge(clk) then                   -- detect rising edge of clk
      Q  <= D ;                                -- Q and QB change on rising edge
      QB <= not D;
    end if;
  end process;
```



# Common error in processes

---

- Process statements are evaluated only at time instant  $T$ , at which an event occurs on a signal in the sensitivity list
  - Statements in the process use signal values that exist at time  $T$ .
  - Signal assignment statements “schedule” future events.

## Example:

```
process (clk)                                -- trigger process on clk event
begin
    if rising_edge(clk) then                 -- detect rising edge of clk
        Q <= D ;                             -- Q and QB change  $\delta$  time after rising edge
        QB <= not Q;                         -- Timing error here!!
    end if;                                  -- Desired QB appears one clock period late!
end process;                                 -- Should be: QB <= not D;
```

As written above, if clk edge occurs at time  $T$ :

Q will change at time  $T+\delta$ , to  $D(T)$

QB will change at time  $T+\delta$ , to “not  $Q(T)$ ” – using  $Q(T)$  rather than new  $Q(T+\delta)$


---


 
# Alternative to sensitivity list

---

```
process -- no "sensitivity list"
begin
    wait on clk; -- suspend process until event on clk
    if (clk='1') then
        Q <= D after 1 ns;
    end if;
end process;
```




- ▶ **BUT - sensitivity list is preferred for sequential circuits!**
- ▶ Other “wait” formats: `wait until (clk'event and clk='1')`  
`wait for 20 ns;`
- ▶ This format does not allow for asynchronous controls
- ▶ Cannot have both sensitivity list and wait statement
- ▶ **Process executes endlessly if neither sensitivity list nor wait statement provided!**




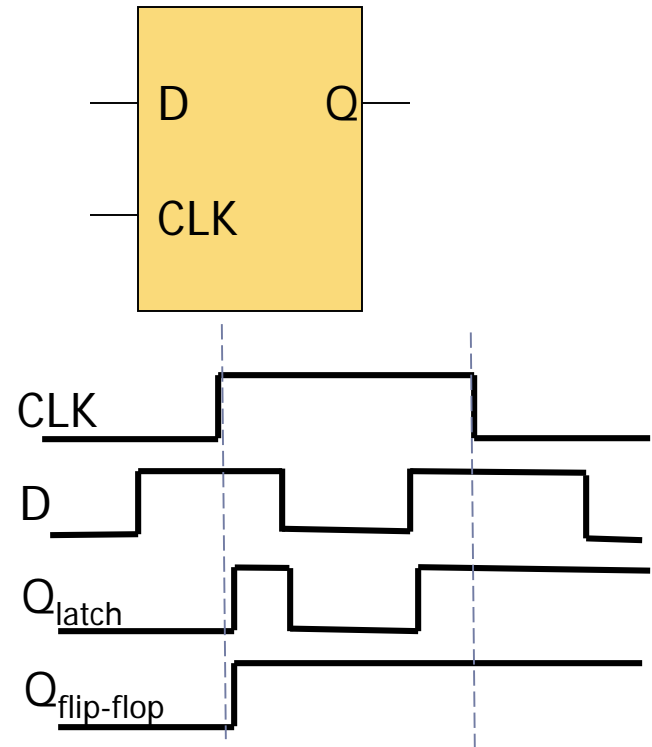
# Level-Sensitive D latch vs. D flip-flop

```
entity Dlatch is
  port (D,CLK: in bit;
        Q: out bit);
end Dlatch;
architecture behave of Dlatch is
begin
  process(D, clk)
  begin
    if (clk='1') then
      Q <= D after 1 ns;
    end if;
  end process;
end;
```



Q<sub>latch</sub> can change when CLK becomes '1' and/or when D changes while CLK='1' (rather than changing only at a clock edge)

# RTL “register” model (not gate-level)

---

entity Reg8 is

```
port (D: in std_logic_vector(0 to 7);  
      Q: out std_logic_vector(0 to 7);  
      LD: in std_logic);
```

end Reg8;

architecture behave of Reg8 is

begin

```
process(LD)
```

```
begin
```


```
    if rising_edge(LD) then
```

```
        Q <= D;
```

```
    end if;
```

```
end process;
```

```
end;
```

 

**D and Q can be any abstract data type**

---



# RTL “register” with clock enable

--Connect all system registers to a common clock

--Select specific registers to be loaded

entity RegCE is

```
port (D: in std_logic_vector(0 to 7);  
      Q: out std_logic_vector(0 to 7);  
      EN: in std_logic;      --clock enable  
      CLK: in std_logic);
```

end RegCE;

architecture behave of RegCE is

begin

```
process(CLK)
```

```
begin
```

```
    if rising_edge(CLK) then
```

```
        if EN = '1' then
```


```
            Q <= D;      --load only if EN=1 at the clock transition
```

```
        end if;
```

```
    end if;
```

```
end process;
```

```
end;
```

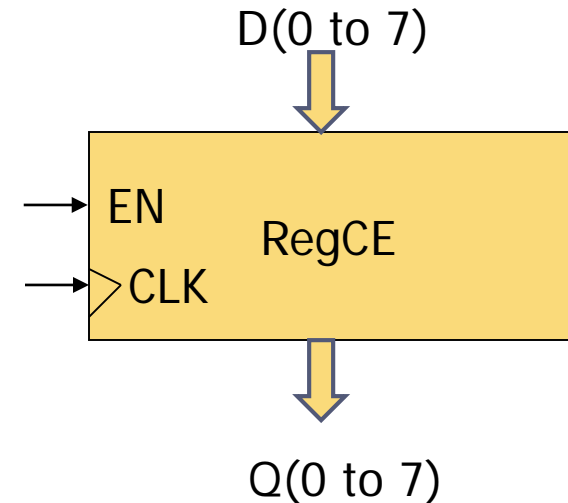

# Synchronous vs asynchronous inputs

---

- **Synchronous** inputs are synchronized to the clock.
- **Asynchronous** inputs are not, and cause immediate change.
  - Asynchronous inputs normally have precedence over sync. inputs

```
process (clock, asynchronous_signals )
```

```
begin
```

```
    if (boolean_expression) then
```

```
        asynchronous signal_assignments
```

```
    elsif (boolean_expression) then
```

```
        asynchronous signal assignments
```

```
    elsif (clock'event and clock = constant) then
```

```
        synchronous signal_assignments
```

```
    end if ;
```

```
end process;
```

---



# Synchronous vs. Asynchronous Flip-Flop Inputs

entity DFF is

```
port (D,CLK: in std_logic;   --D is a sync input
      PRE,CLR: in std_logic; --PRE/CLR are async inputs
      Q: out std_logic);
```

end DFF;

architecture behave of DFF is

begin

```
process(clk,PRE,CLR)
```

```
begin
```

```
if (CLR='0') then
```

```
Q <= '0';
```

```
elsif (PRE='0') then
```

```
Q <= '1';
```


```
elsif rising_edge(clk) then
```

```
Q <= D;
```

```
end if;
```

```
end process;
```

```
end;
```

 

-- async CLR has precedence

-- then async PRE has precedence

-- sync operation only if CLR=PRE='1'

*What happens if CLR = PRE = 0 ??*

# Sequential Constructs: *if-then-else*

---

## General format:

```
if (condition) then
    do stuff
elsif (condition) then
    do more stuff
else
    do other stuff
end if;
```

## Example:

```
if (S = "00") then
    Z <= A;
elsif (S = "11") then
    Z <= B;
else
    Z <= C;
end if;
```

*elsif* and *else* clauses are optional, BUT incompletely specified *if-then-else* (no *else*) implies memory element



# Sequential Constructs: *case-when*

---

## General format:

```
case expression is
  when value =>
    do stuff
  when value =>
    do more stuff
  when others =>
    do other stuff
end case;
```

## Example:

```
case S is
  when "00" =>
    Z <= A;
  when "11" =>
    Z <= B;
  when others =>
    Z <= C;
end case;
```



# Sequential Constructs: *for loop*

---

## General format:

```
[label:] for identifier in range loop  
    do a bunch of junk  
end loop [label];
```

## Example:

```
init: for k in N-1 downto 0 loop  
    Q(k) <= '0';  
end loop init;
```

Note: variable k is “implied” in the for-loop and does not need to be declared





# Sequential Constructs: *while* loop

---

## General format:

```
[label:] while condition loop  
    do some stuff  
end loop [label];
```

## Example:

```
init: while (k > 0) loop  
    Q(k) <= '0'  
    k := k - 1;  
end loop init;
```

Note: Variable *k* must be declared as a process “variable”,  
between *sensitivity list* and *begin*, with format:  
*variable k: integer := N-1;*

---



# Modeling Finite State Machines (FSMs)


---

- ▶ “Manual” FSM design & synthesis process:
  1. Design state diagram (behavior)
  2. Derive state table
  3. Reduce state table
  4. Choose a state assignment
  5. Derive output equations
  6. Derive flip-flop excitation equations
- ▶ Steps 2-6 can be automated, given a state diagram
  - ▶ Model states as enumerated type
  - ▶ Model output function (Mealy or Moore model)
  - ▶ Model state transitions (functions of current state and inputs)
  - ▶ Consider how initial state will be forced



# FSM structure

---

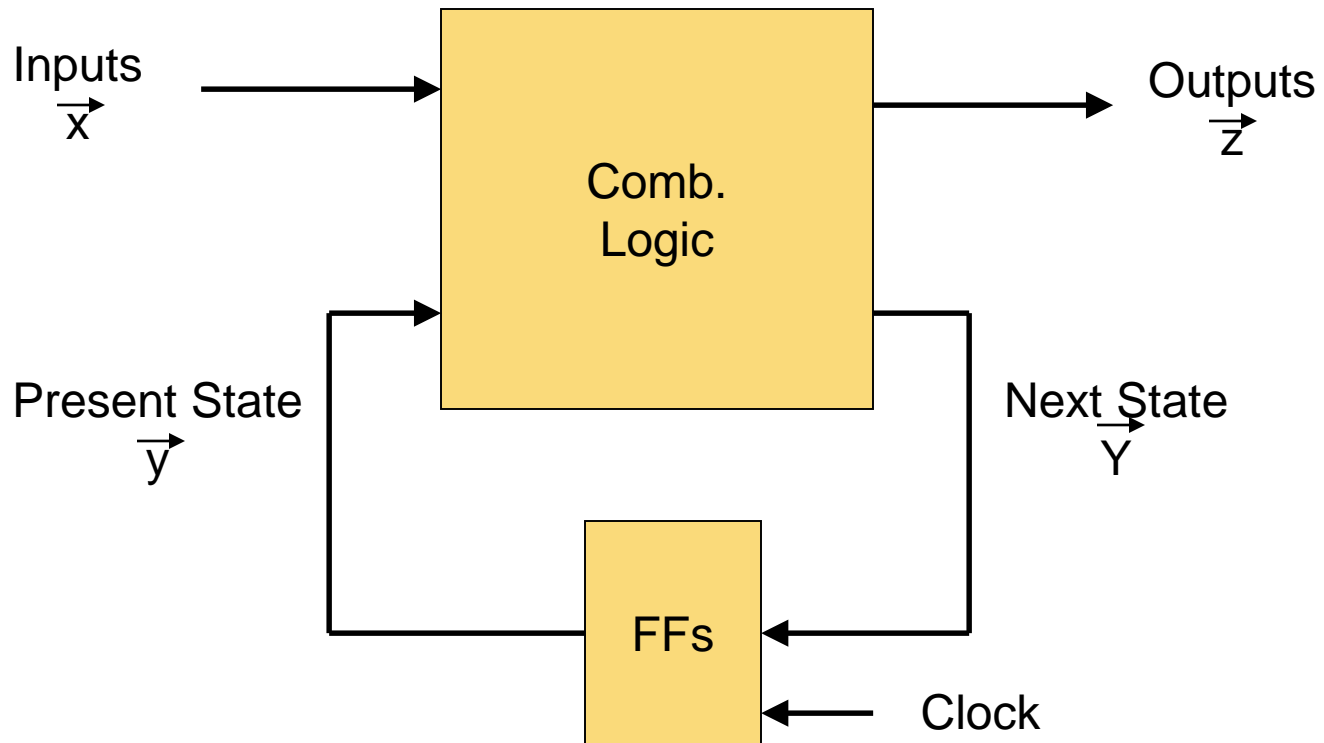


Mealy Outputs  $z = f(x,y)$ , Moore Outputs  $z = f(y)$

Next State  $Y = f(x,y)$

---



# FSM example – Mealy model

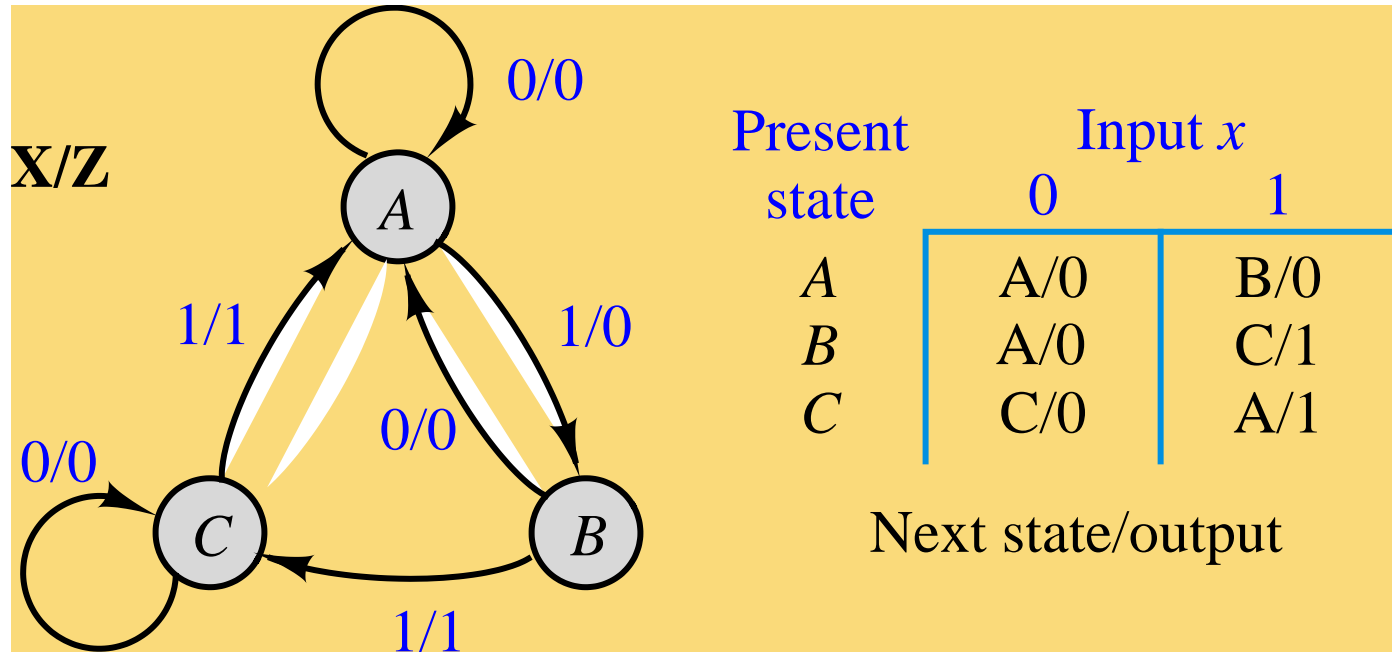

entity seqckt is

```
port ( x: in  std_logic;      -- FSM input
       z: out std_logic;      -- FSM output
       clk: in std_logic );   -- clock
end seqckt;
```

# FSM example - behavioral model

---

architecture behave of seqckt is

type states is (A,B,C); -- symbolic state names (enumerate)

signal state: states; --state variable

begin

-- Output function (combinational logic)

z <= '1' when ((state = B) and (x = '1')) --all conditions  
                  or ((state = C) and (x = '1')) --for which z=1.  
          else '0'; --otherwise z=0


-- State transitions on next slide

---



# FSM example – state transitions

```
process (clk) – trigger state change on clock transition
begin
  if rising_edge(clk) then -- change state on rising clock edge
    case state is -- change state according to x
      when A => if (x = '0') then
                  state <= A;
                else -- if (x = '1')
                  state <= B;
                end if;
      when B => if (x='0') then
                  state <= A;
                else -- if (x = '1')
                  state <= C;
                end if;
      when C => if (x='0') then
                  state <= C;
                else -- if (x = '1')
                  state <= A;
                end if;
    end case;
  end if;
end process;
```



# FSM example – alternative model

---

architecture behave of seqckt is

```
type states is (A,B,C); -- symbolic state names (enumerate)
```

```
signal curr_state,next_state: states;
```

```
begin
```

```
-- Model the memory elements of the FSM
```

```
process (clk)
```

```
begin
```

```
    if (clk'event and clk='1') then
```

```
        pres_state <= next_state;
```

```
    end if;
```

```
end process;
```

(continue on next slide)

---



# FSM example (alternate model, continued)

---

-- Model next-state and output functions of the FSM

-- as combinational logic

process (x, pres\_state) -- function inputs

begin

    case pres\_state is -- describe each state

        when A => if (x = '0') then

            z <= '0';

            next\_state <= A;

        else -- if (x = '1')

            z <= '0';

            next\_state <= B;

        end if;

---

(continue on next slide for pres\_state = B and C)





# FSM example (alternate model, continued)

---

```
when B => if (x='0') then
    z <= '0';
    next_state <= A;
else
    z <= '1';
    next_state <= C;
end if;
```

```
when C => if (x='0') then
    z <= '0';
    next_state <= C;
else
    z <= '1';
    next_state <= A;
end if;
```

```
end case;
end process;
```

---



# Alternative form for output and next state functions (combinational logic)

---

## -- Next state function (combinational logic)

```
next_state <= A when ((curr_state = A) and (x = '0'))
                    or ((curr_state = B) and (x = '0'))
                    or ((curr_state = C) and (x = '1')) else
B when ((curr_state = I) and (x = '1')) else
C;
```


## -- Output function (combinational logic)

```
z <= '1' when ((curr_state = B) and (x = '1'))      --all conditions
              or ((curr_state = C) and (x = '1'))    --for which z=1.
              else '0';                               --otherwise z=0
```



# Moore model FSM

---

 

*Input Ordering:*  
EN TDI  $\dashrightarrow$  11

*Output Ordering:*  
RST SHIFT  $\dashrightarrow$  00

entity FSM is  
port (CLK, EN, TDI: in bit;  
RST, SHIFT: out bit);  
end entity FSM;



architecture RTL of FSM is

```
type STATES is (Reset, BIST, Result, NOP); -- abstract state names
signal CS: STATES;                          -- current state
begin
SYNC: process (CLK) begin -- change states on falling edge of CLK
  if (CLK'event and CLK='0') then
    if (EN = '1') then -- change only if EN = 1
      if (CS = Reset) then
        if (TDI='0') then CS <= BIST; end if; --EN,TDI = 10
      elsif (CS = BIST) then
        if (TDI='1') then CS <= Result; end if; --EN,TDI = 11
      elsif (CS = Result) then
        if (TDI='1') then CS <= NOP; end if; --EN,TDI = 11
      elsif (CS = NOP) then
        if (TDI='0') then CS <= BIST; --EN,TDI = 10
        else CS <= Reset; --EN,TDI = 11
        end if;
      end if;
    end if;
  end if; end if; end process SYNC;
```

(Outputs on next slide)



# Moore model outputs

---

-- Outputs = functions of the state

```
COMB: process (CS) begin
    if (CS = Reset) then
        RST <= '1';
        SHIFT <= '0';
    elsif (CS = Result) then
        RST <= '0';
        SHIFT <= '1';
    else
        RST <= '0';
        SHIFT <= '0';
    end if;
end process COMB;

end architecture RTL;
```

-- more compact form

```
RST <= '1' when CS = Reset else '0';

SHIFT <= '1' when CS = Result else '0';

end architecture RTL;
```

Note that Moore model outputs  
are independent of current inputs.

