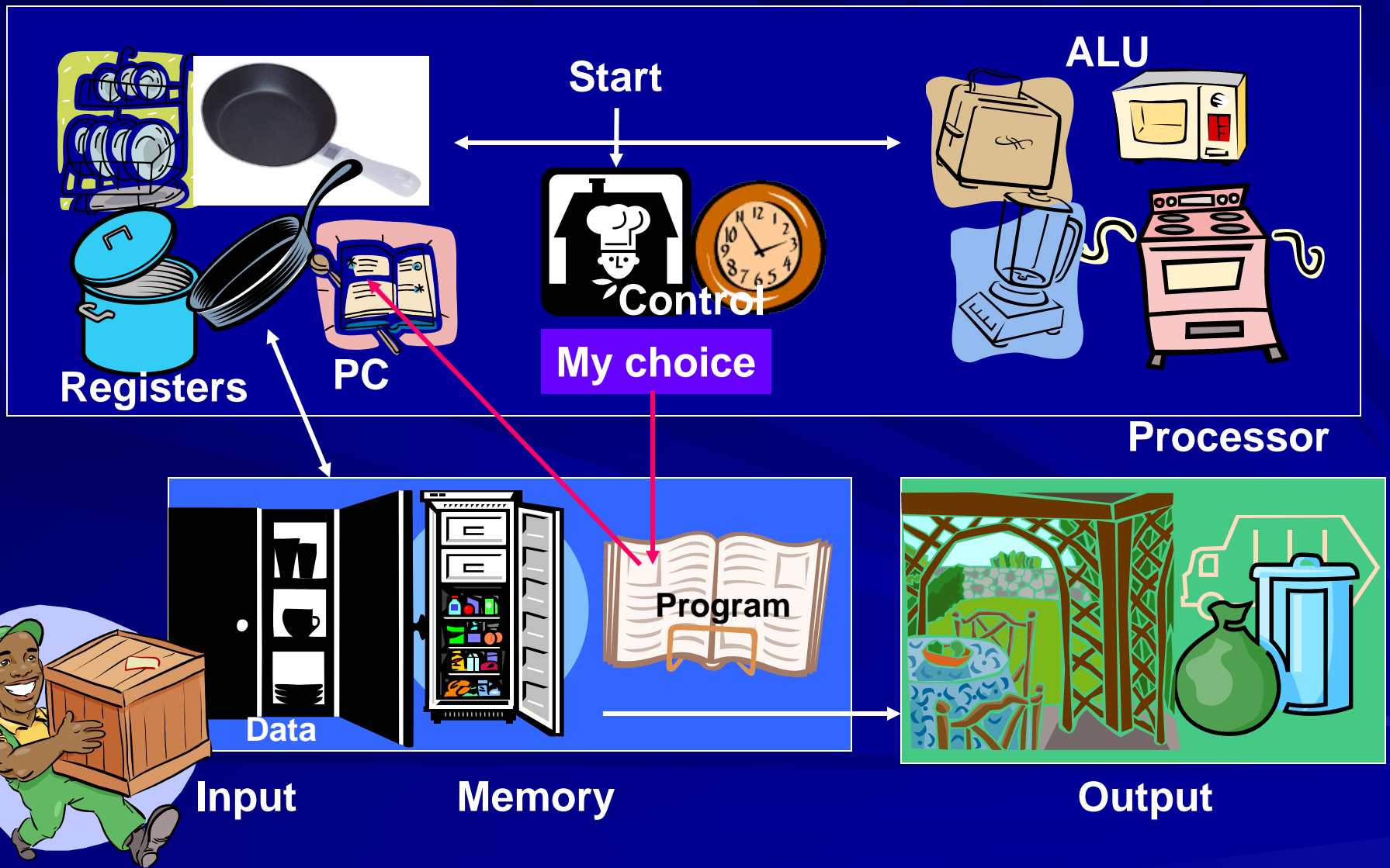


ELEC 5200-001/6200-001  
Computer Architecture and Design  
Fall 2013  
**Datapath and Control**  
**(Chapter 4)**

**Vishwani D. Agrawal & Victor P. Nelson**  
Department of Electrical and Computer Engineering  
Auburn University, Auburn, AL 36849


# Von Neumann Kitchen




# Where Does It All Begin?

- In a register called *program counter (PC)*.
- PC contains the memory address of the next instruction to be executed.
- In the beginning, PC contains the address of the memory location where the program begins.

# Where is the Program?

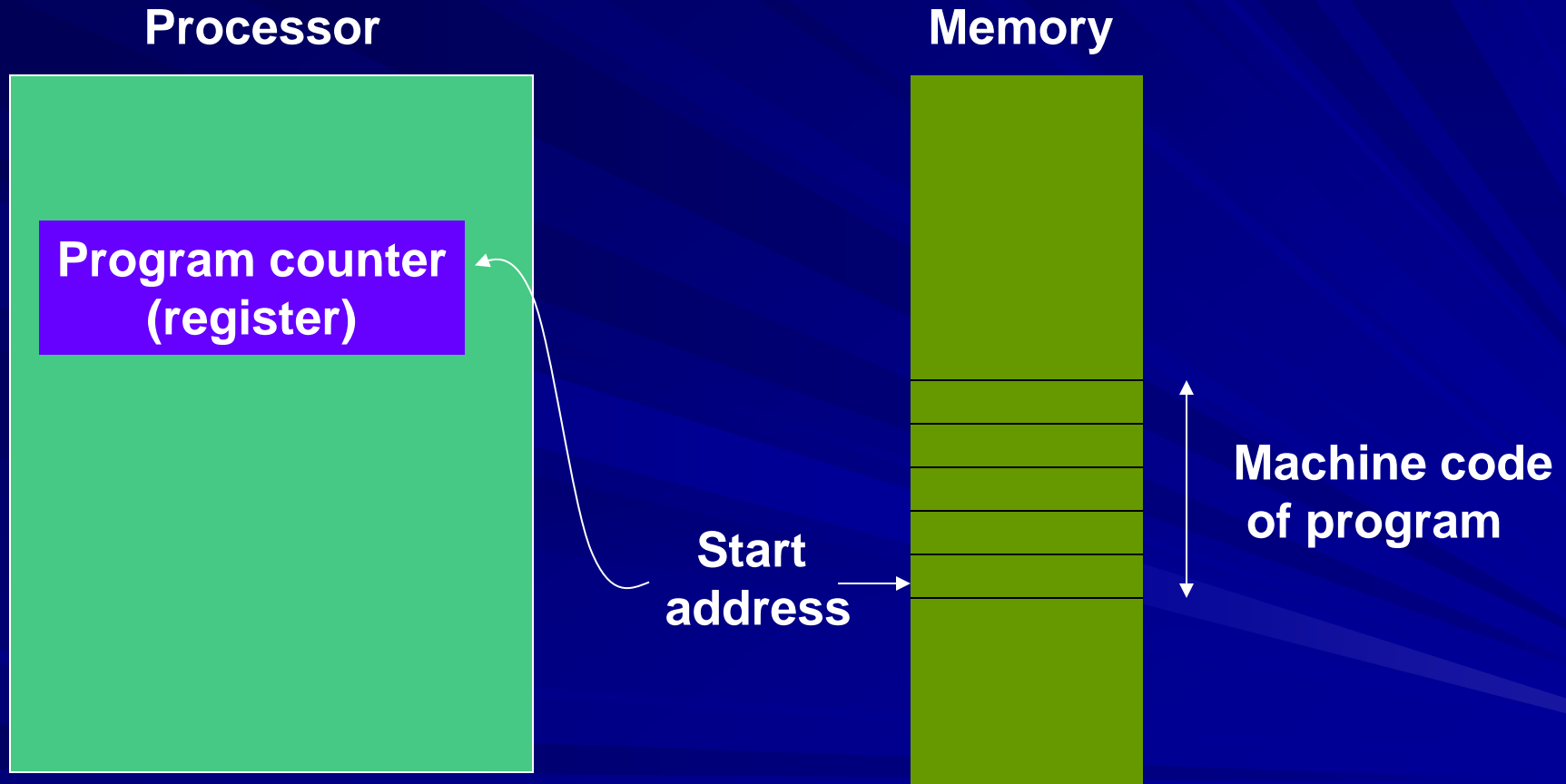


# How Does It Run?

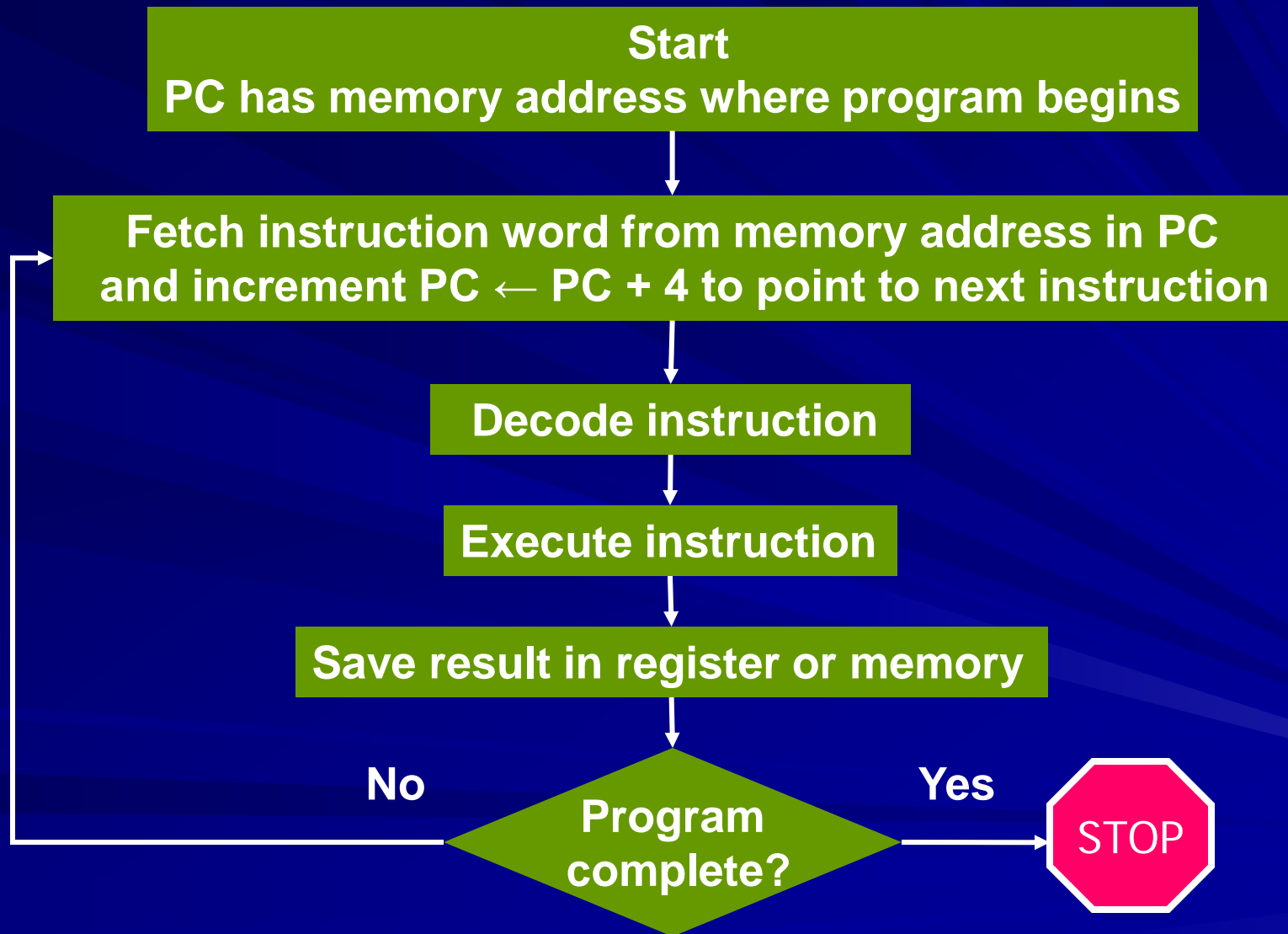

# Datapath and Control


- Datapath: Memory, registers, adders, ALU, and communication buses. Each step (fetch, decode, execute, save result) requires communication (data transfer) paths between memory, registers and ALU.
- Control: Datapath for each step is set up by control signals that set up dataflow directions on communication buses and select ALU and memory functions. Control signals are generated by a control unit consisting of one or more finite-state machines.

# Datapath for Instruction Fetch

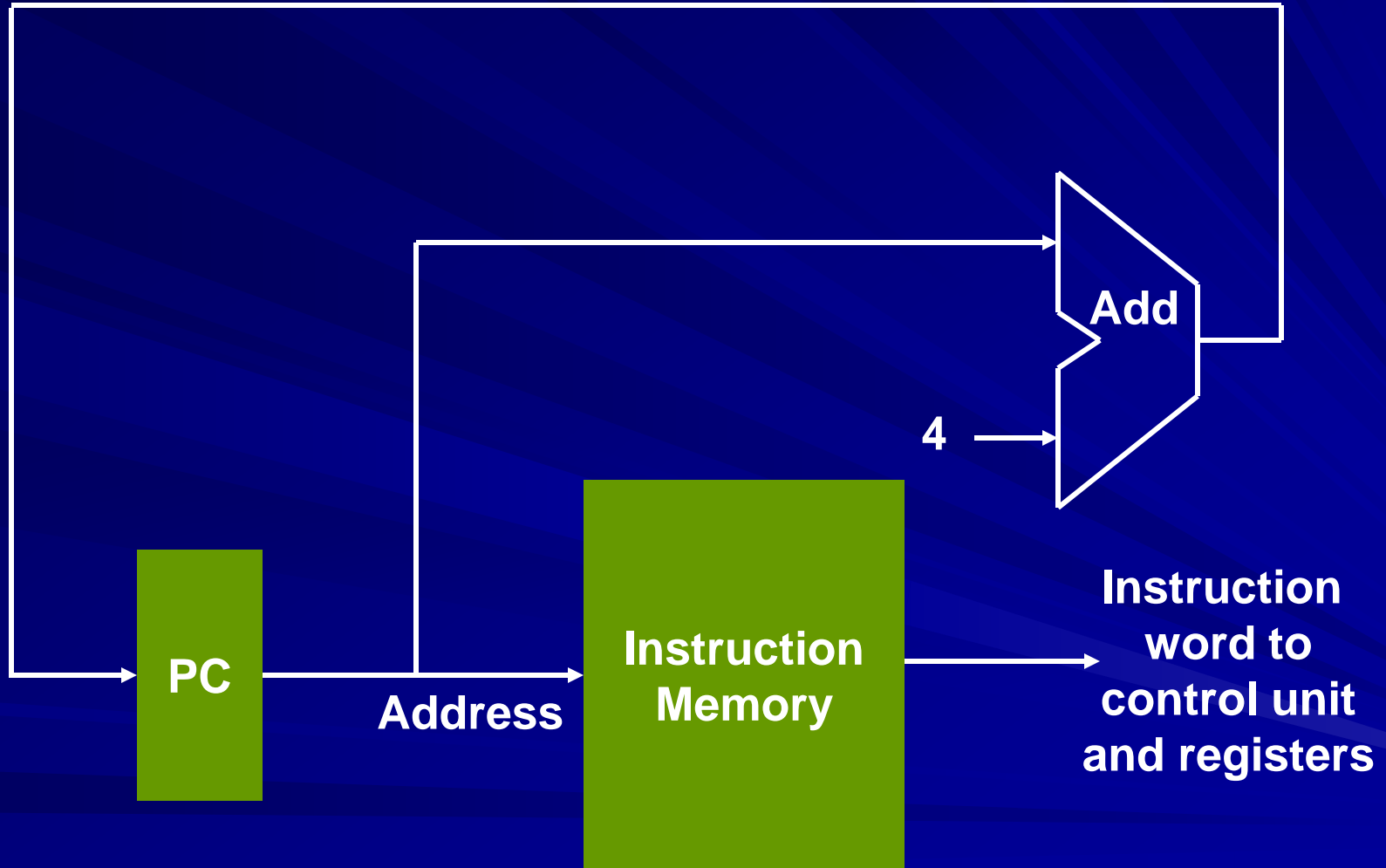




# Register File: A Datapath Component

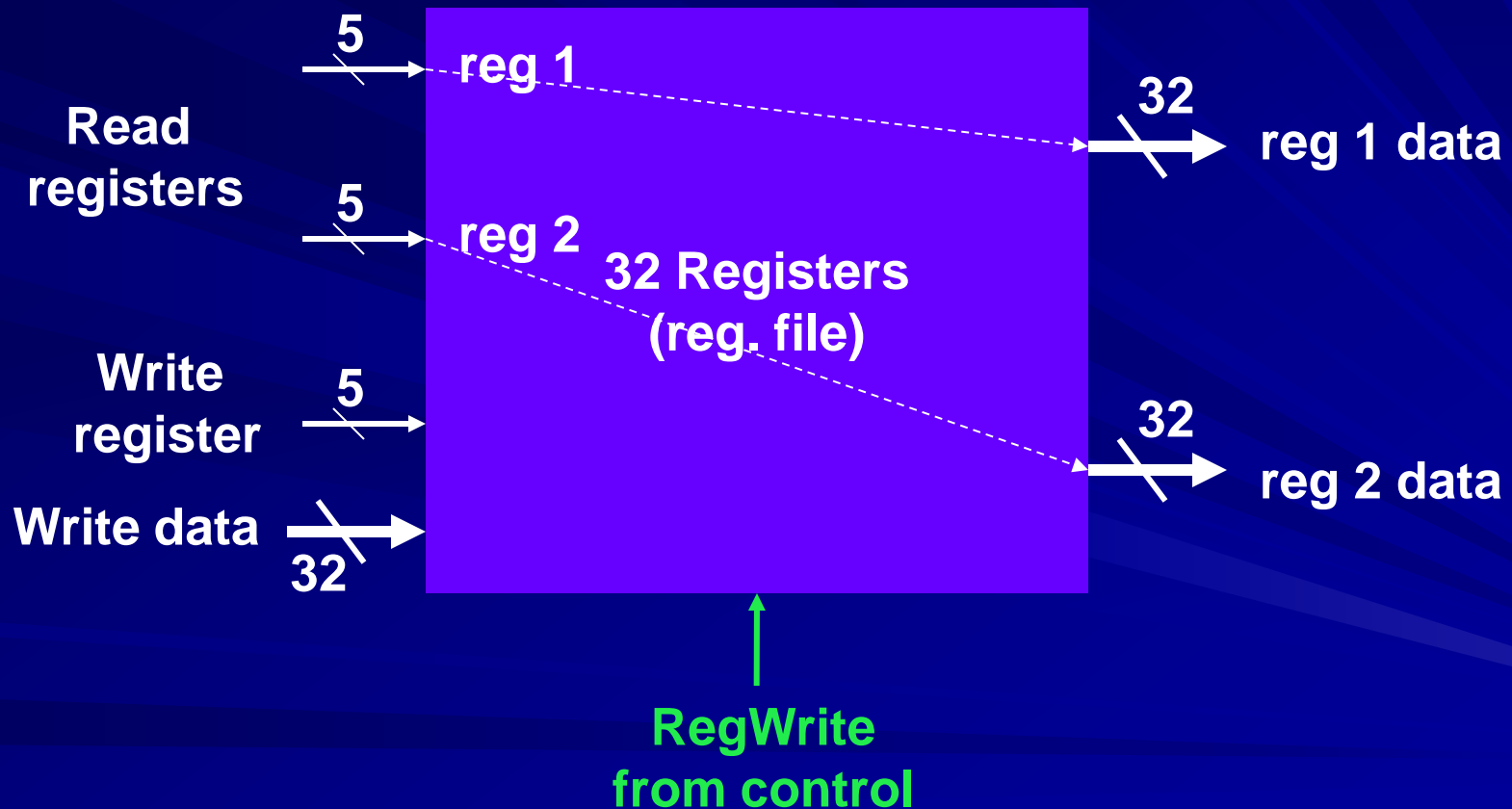



# Multi-Operation ALU

Operation select	ALU function
000	AND
001	OR
010	Add
110	Subtract
111	Set on less than

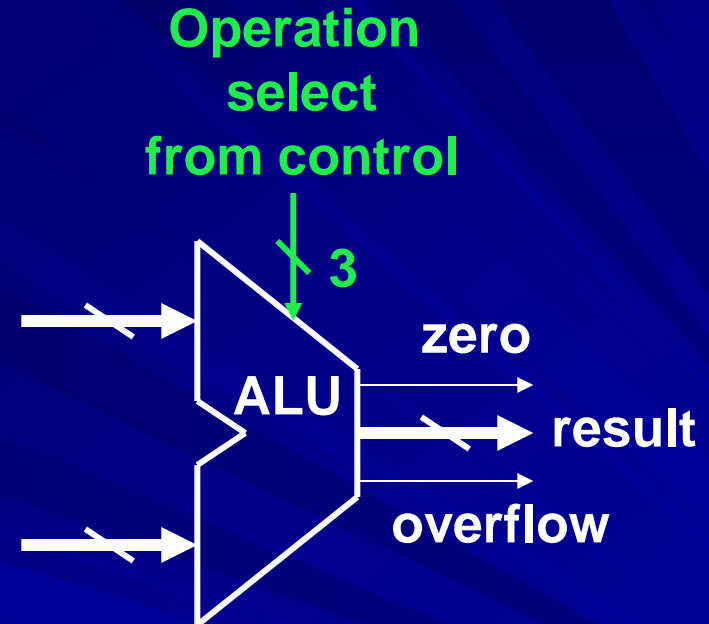

zero = 1, when all bits of result are 0

# R-Type Instructions

- Also known as arithmetic-logical instructions

- add, sub, slt

- Example: add      \$t0, \$s1, \$s2

- Machine instruction word

000000 10001 10010 01000 00000 100000  
opcode    \$s1    \$s2    \$t0                    function

- Read two registers

- Write one register


- Opcode and function code go to control unit that generates RegWrite and ALU operation code.

# Datapath for R-Type Instruction

000000 10001 10010 01000 00000 100000  
opcode \$s1 \$s2 \$t0 function (add)

Operation  
select

from control (add)

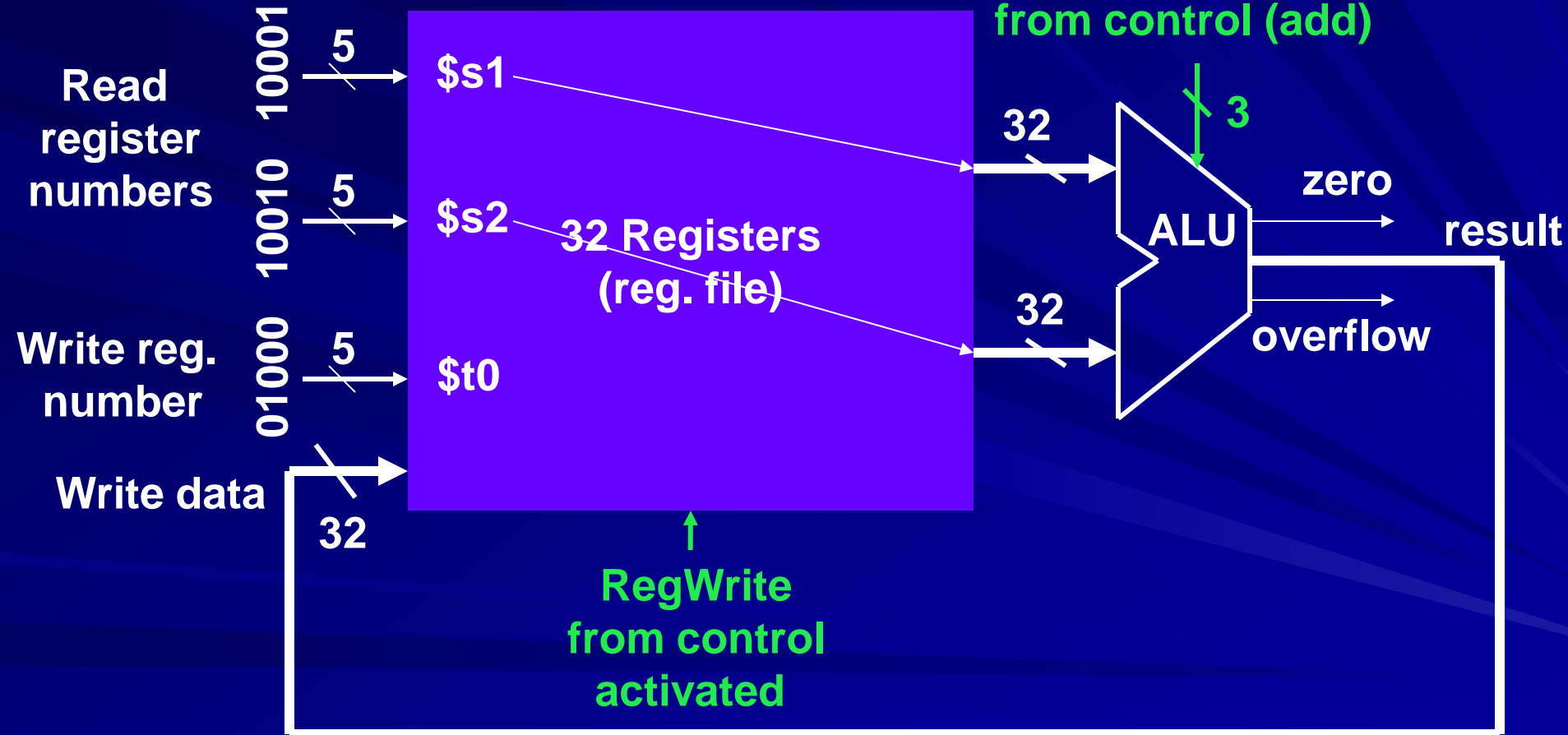

# Load and Store Instructions

- I-type instructions

- lw        \$t0, 1200 (\$t1)        # incr. in bytes

100011 01001 01000 0000 0100 1011 0000

opcode \$t1    \$t0            1200


- sw        \$t0, 1200 (\$t1)        # incr. in bytes

101011 01001 01000 0000 0100 1011 0000

opcode \$t1    \$t0            1200

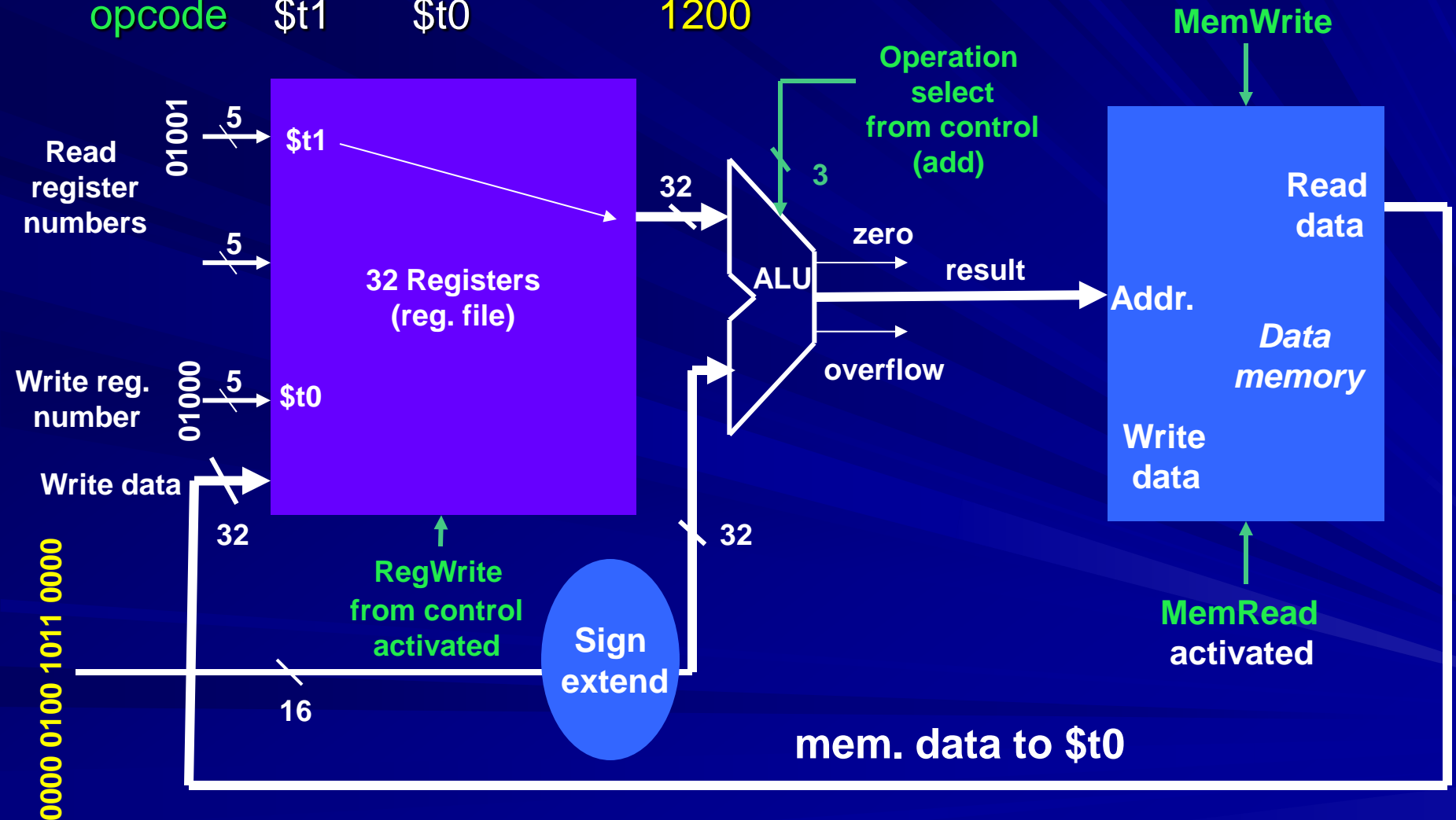
# Datapath for lw Instruction

100011 01001 01000 0000 0100 1011 0000  
 opcode \$t1 \$t0 1200


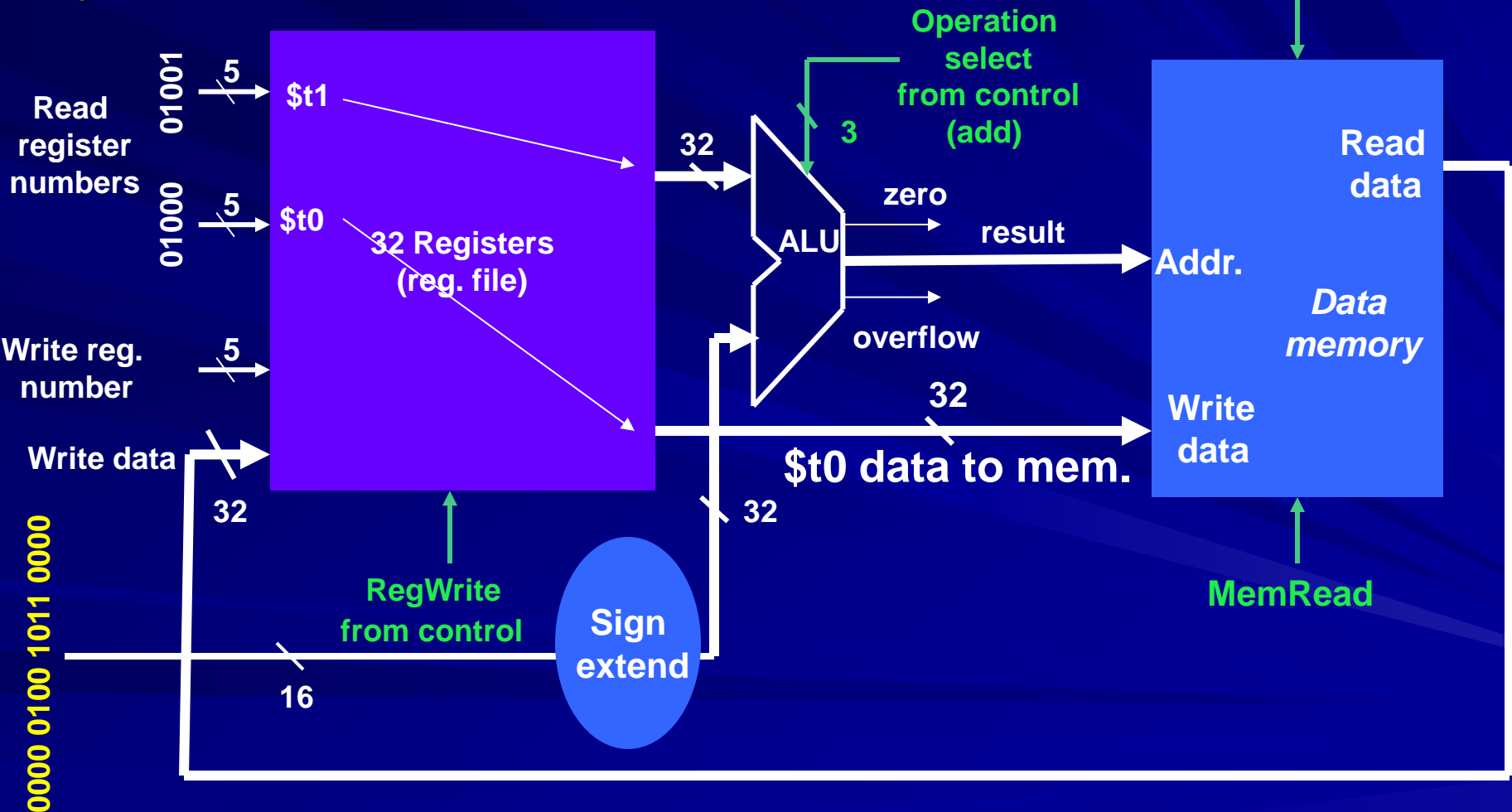
# Datapath for sw Instruction

101011 01001 01000 0000 0100 1011 0000  
 opcode \$t1 \$t0 1200



0000 0100 1011 0000

# Branch Instruction (I-Type)

- `beq $s1, $s2, 25` # if  $\$s1 = \$s2$ , advance PC through 25 instructions

000100 10001 10010 0000 0000 0001 1001  
opcode \$s1 \$s2 25

← 16-bits →


**Note:** Can branch within  $\pm 2^{15}$  words from the current instruction address in PC.


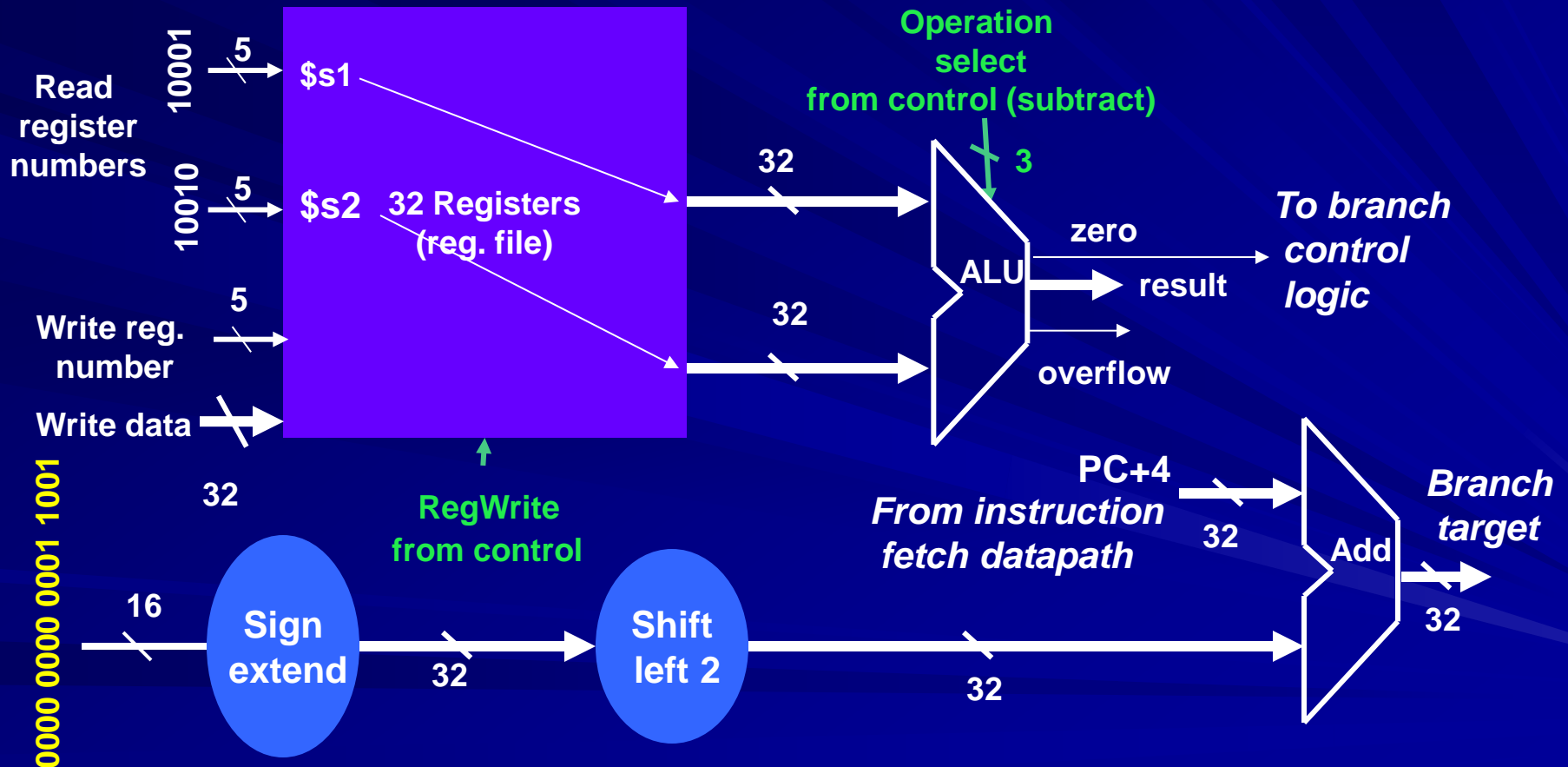
# Datapath for beq Instruction

16-bits

000100 10001 10010 0000 0000 0001 1001  
 opcode \$s1 \$s2 25




# J-Type Instruction


■ **j 2500** # jump to instruction 2,500




# Datapath for Jump Instruction

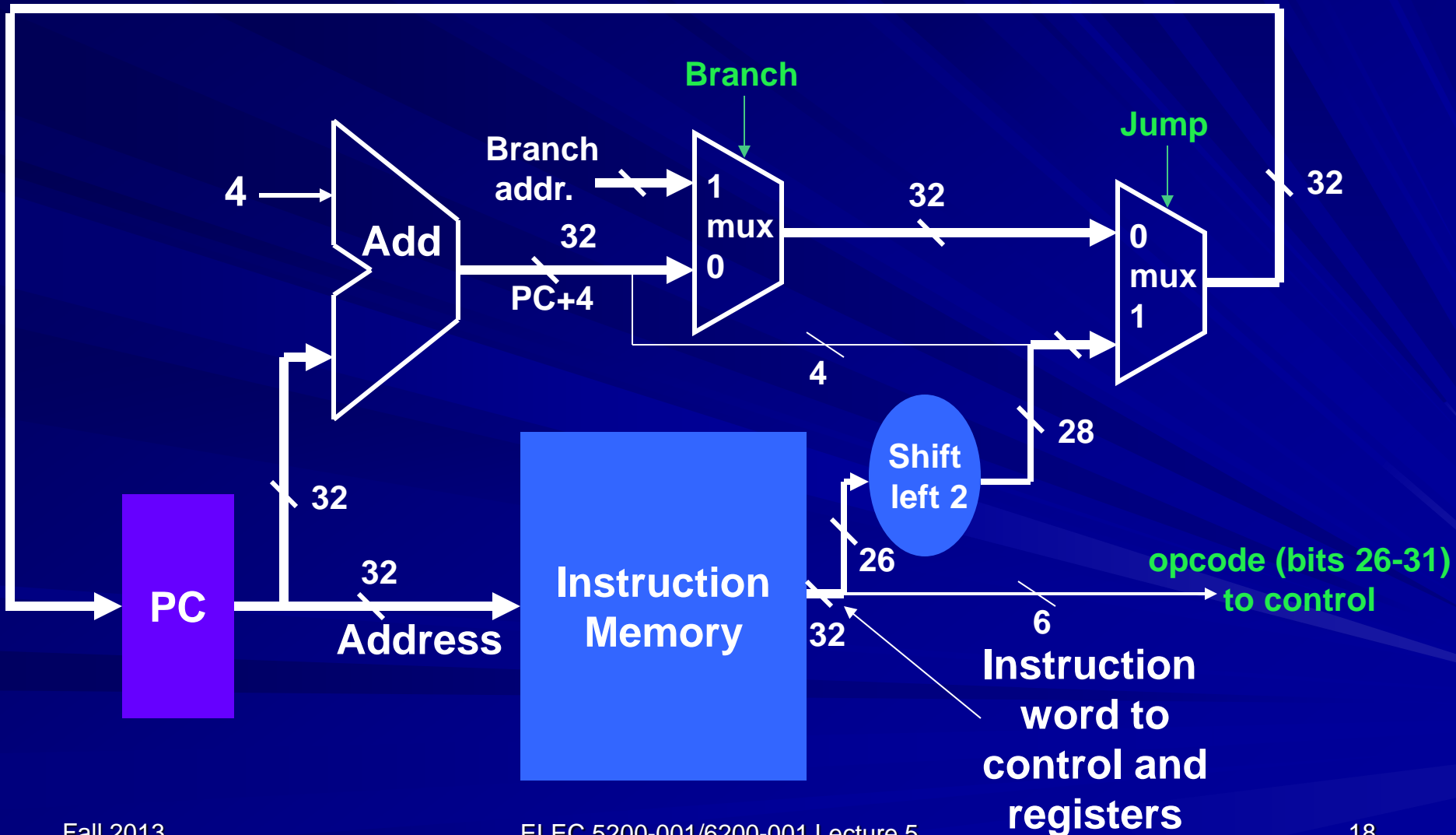

# Combined Datapaths

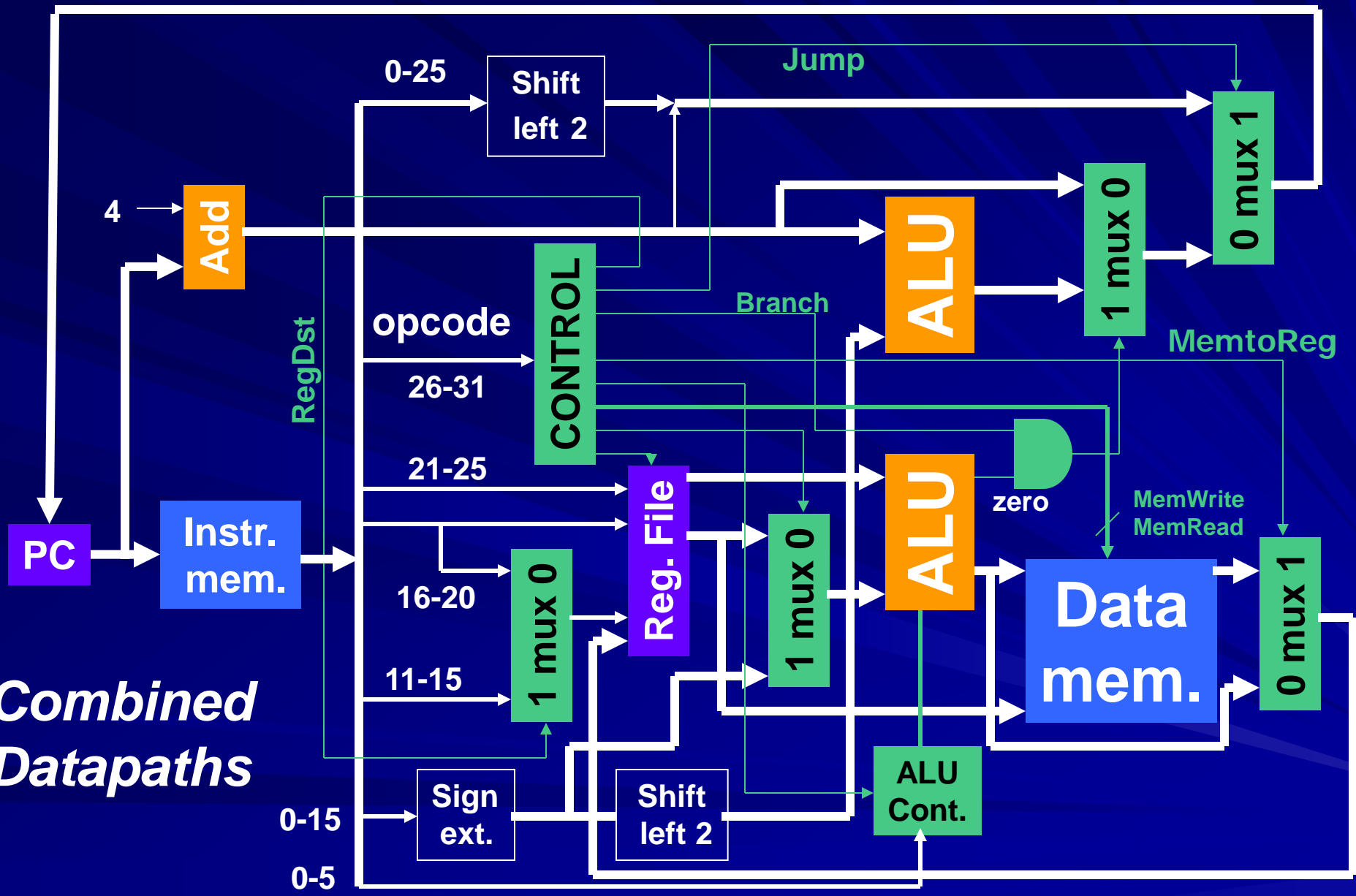

# Control

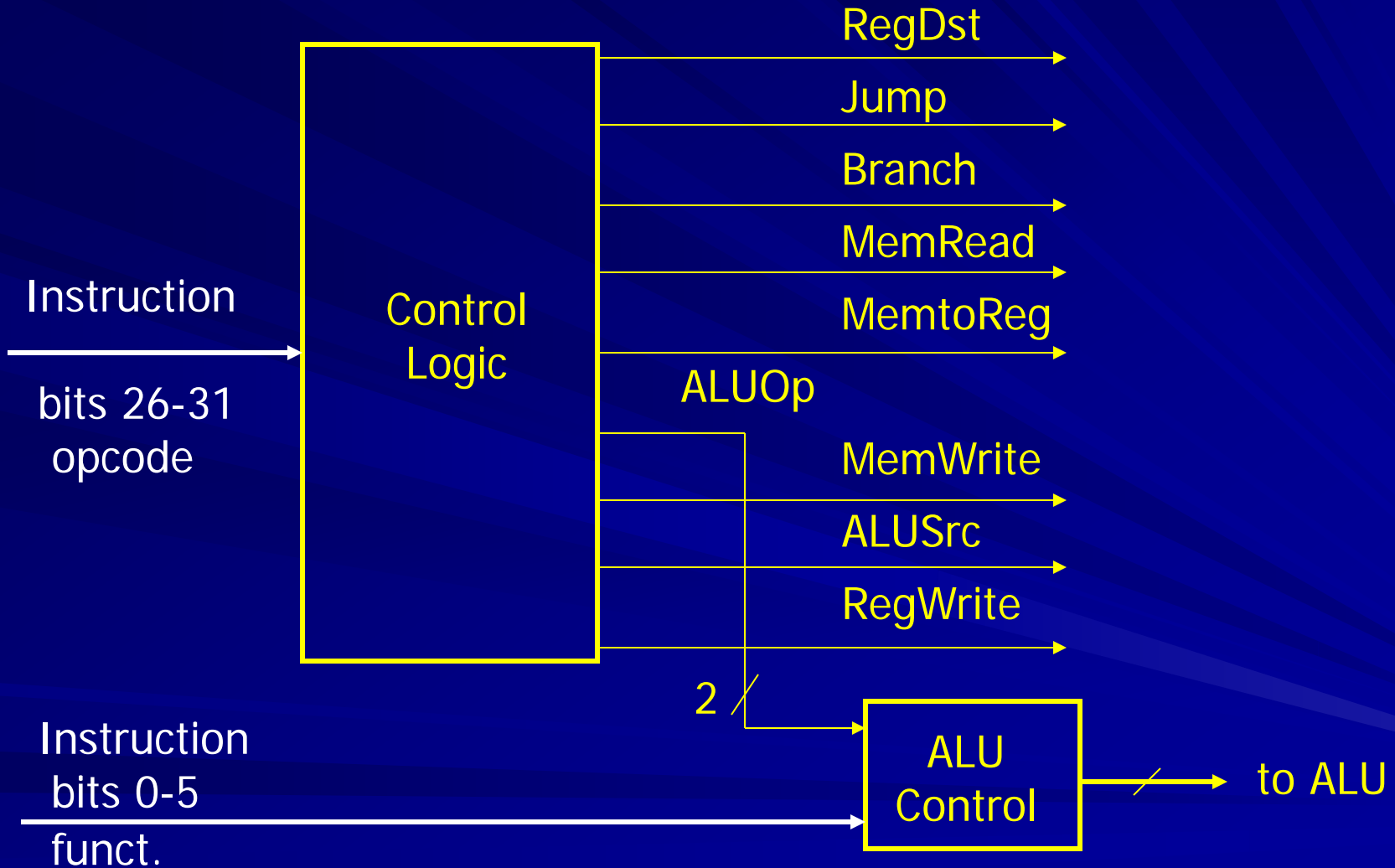

# Control Logic: Truth Table

Instr type	Inputs: instr. opcode bits						Outputs: control signals									
	31	30	29	28	27	26	RegDst	Jump	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALOp1	ALOp2
R	0	0	0	0	0	0	1	0	0	0	1	0	0	0	1	0
lw	1	0	0	0	1	1	0	0	1	1	1	1	0	0	0	0
sw	1	0	1	0	1	1	X	0	1	X	0	0	1	0	0	0
beq	0	0	0	1	0	0	X	0	0	X	0	0	0	1	0	1
j	0	0	0	0	1	0	X	1	X	X	0	X	0	X	X	X

# How Long Does It Take?

- Assume control logic is fast and does not affect the critical timing. Major time delay components are ALU, memory read/write, and register read/write.

- Arithmetic-type (R-type)

■ Fetch (memory read)	2ns
■ Register read	1ns
■ ALU operation	2ns
■ Register write	1ns
■ <b>Total</b>	<b>6ns</b>



# Time for lw and sw (I-Types)

- ALU (R-type) 6ns
- Load word (I-type)
  - Fetch (memory read) 2ns
  - Register read 1ns
  - ALU operation 2ns
  - Get data (mem. Read) 2ns
  - Register write 1ns
  - Total 8ns
- Store word (no register write) 7ns

# Time for beq (I-Type)

■ ALU (R-type)	6ns
■ Load word (I-type)	8ns
■ Store word (I-type)	7ns
■ Branch on equal (I-type)	
– Fetch (memory read)	2ns
– Register read	1ns
– ALU operation	2ns
– <b>Total</b>	<b>5ns</b>


# Time for Jump (J-Type)

■ ALU (R-type)	6ns
■ Load word (I-type)	8ns
■ Store word (I-type)	7ns
■ Branch on equal (I-type)	5ns
■ Jump (J-type)	
– Fetch (memory read)	2ns
– <b>Total</b>	<b>2ns</b>


# How Fast Can Clock Run?

- If every instruction is executed in one clock cycle, then:
  - Clock period must be at least 8ns to perform the longest instruction, i.e.,  $l/w$ .
  - This is a single cycle machine.
  - It is slower because many instructions take less than 8ns but are still allowed that much time.
- Method of speeding up: Use multicycle datapath.


# A Single Cycle Example

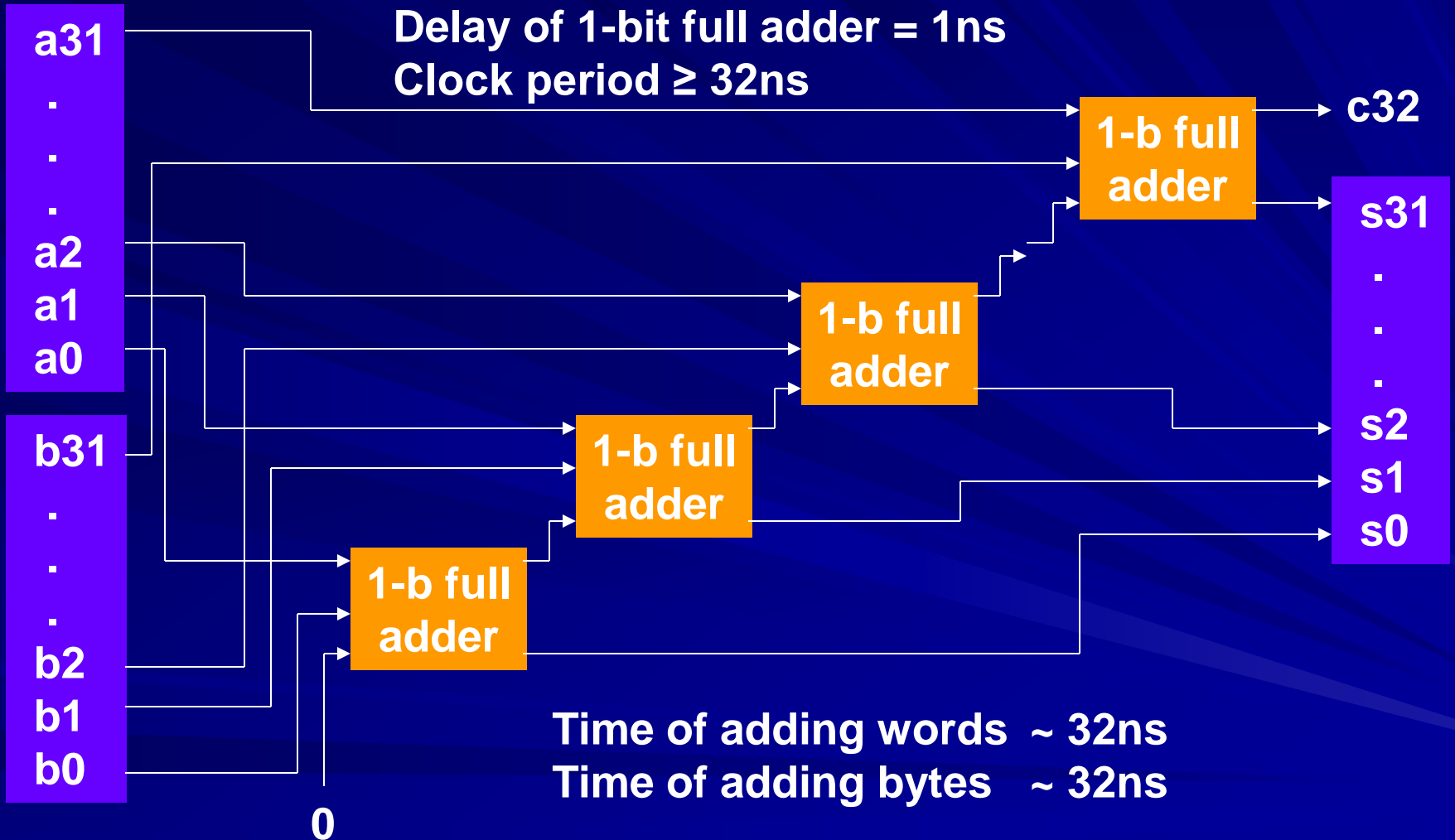

# A Multicycle Implementation

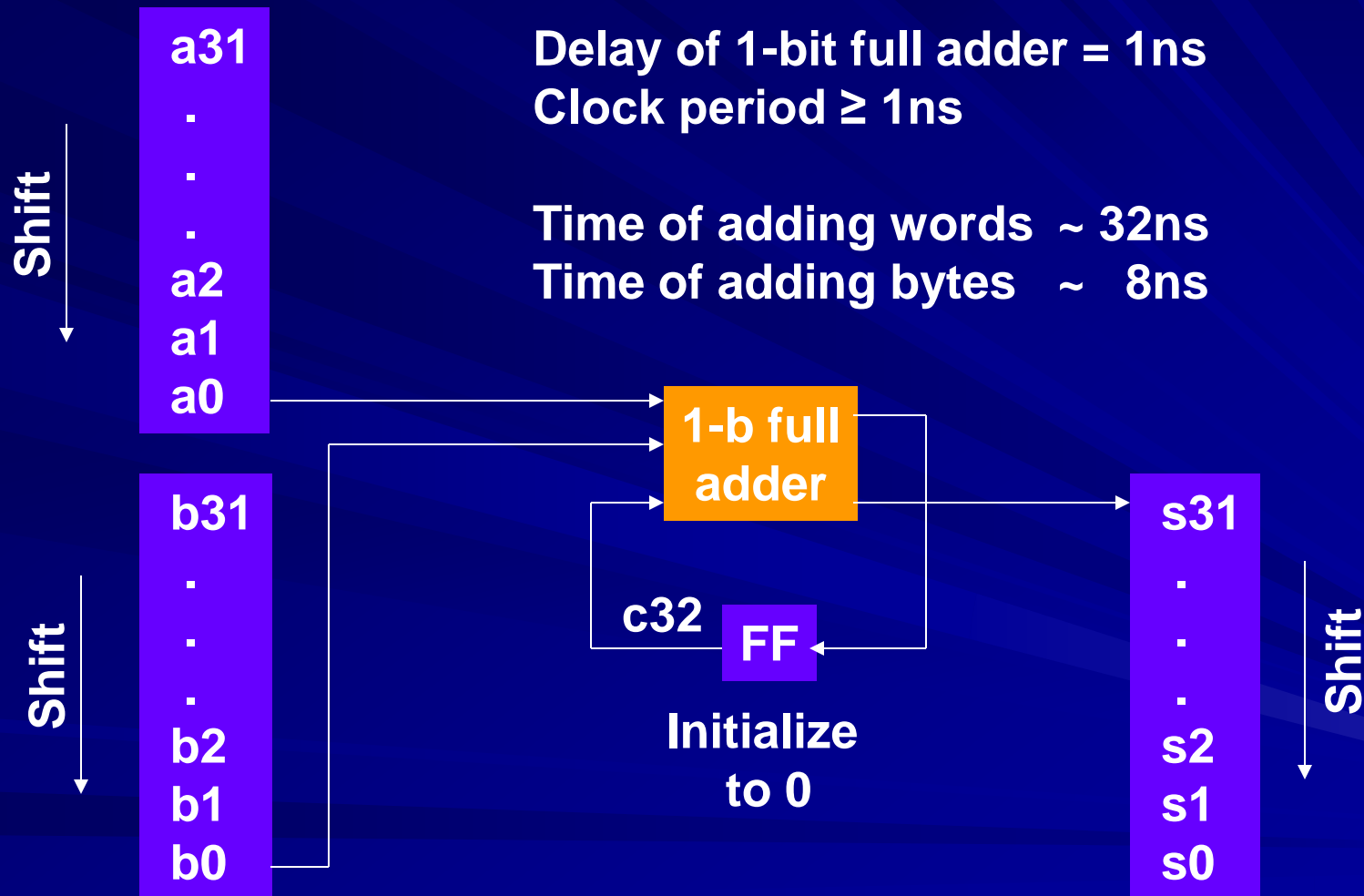


# Single-cycle Datapaths

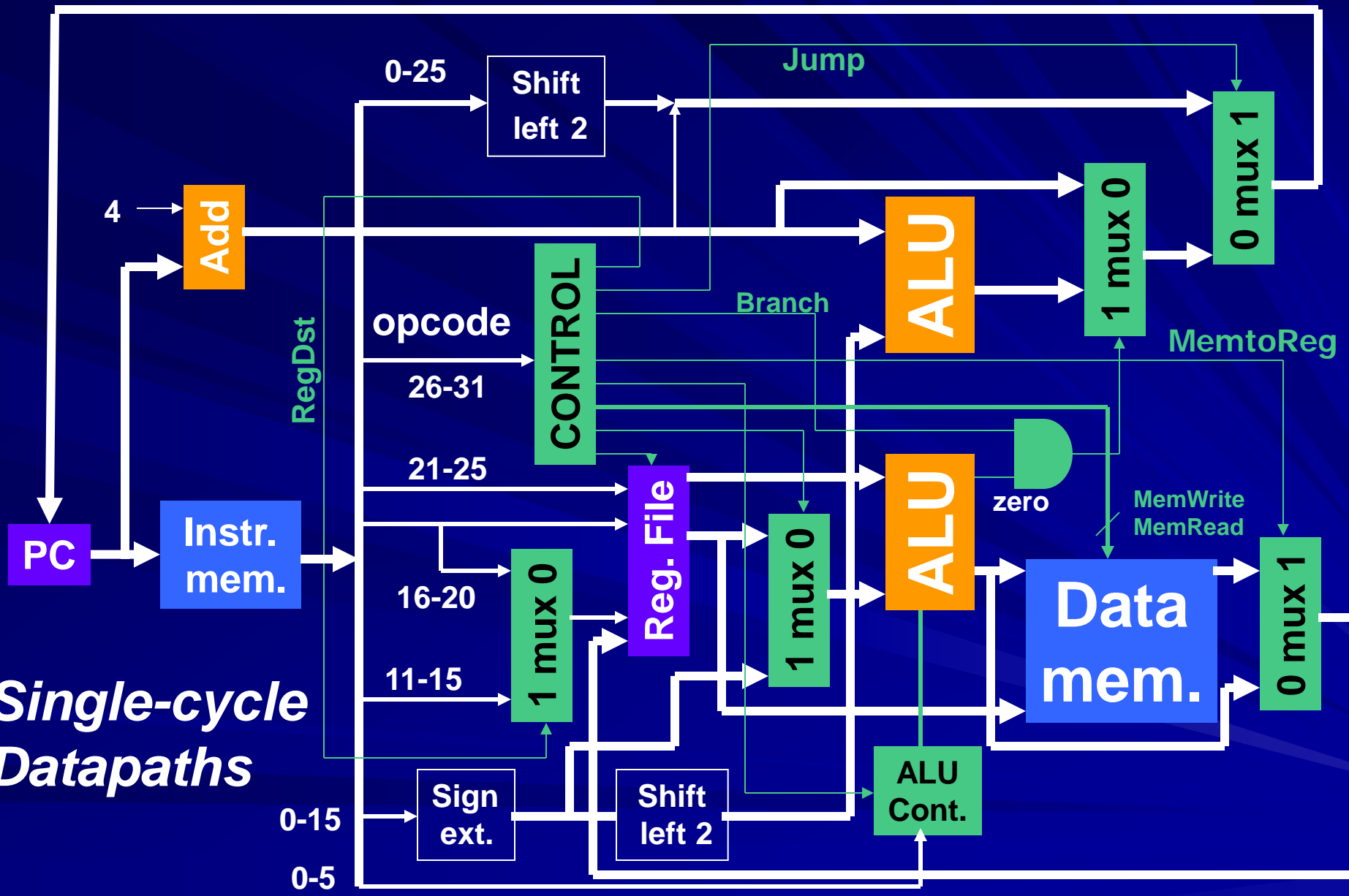




# Multicycle Datapath

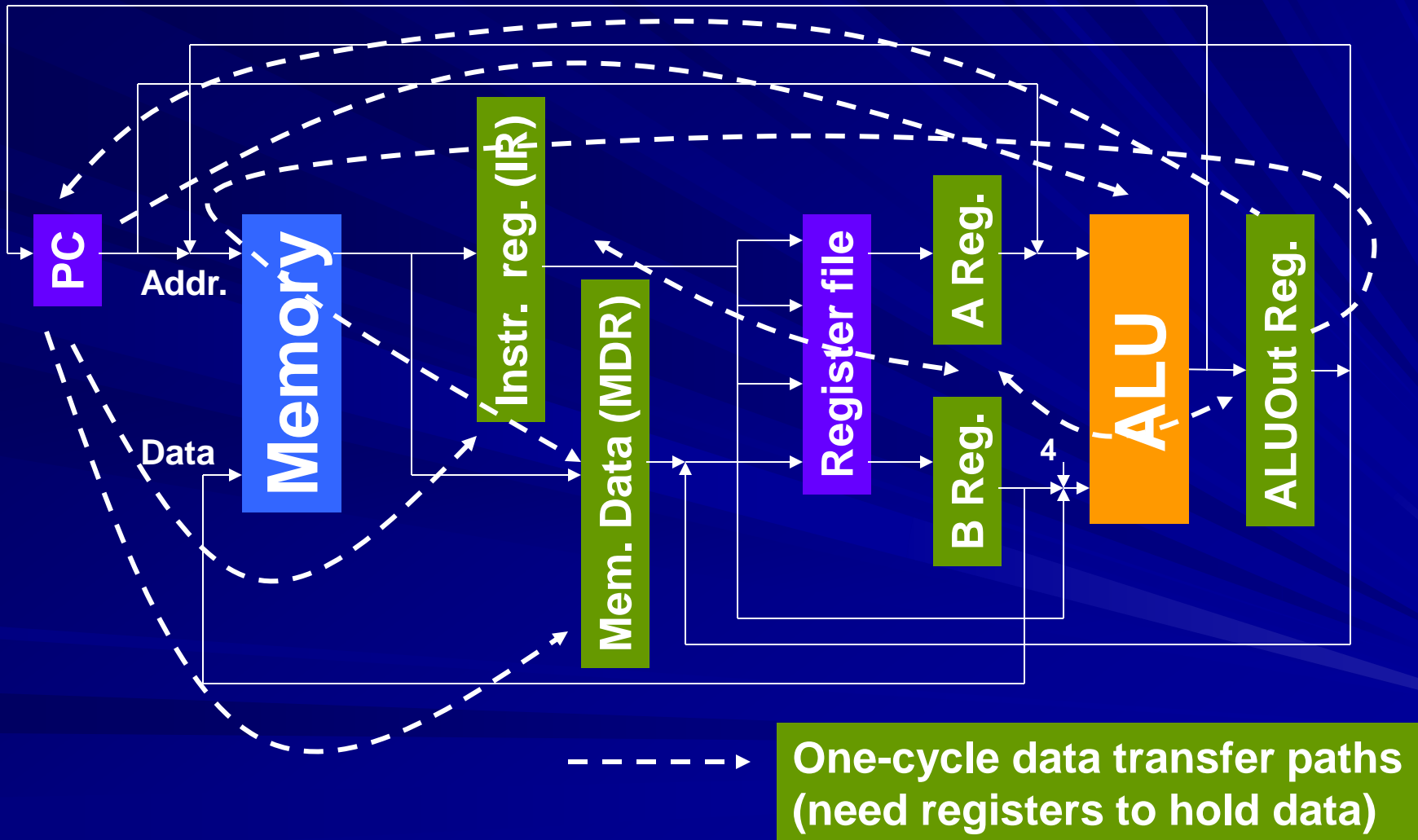

# Multicycle Datapath Requirements

- Only one ALU, since it can be reused.
- Single memory for instructions and data.
- Five registers added:
  - Instruction register (IR)
  - Memory data register (MDR)
  - Three ALU registers, A and B for inputs and ALUOut for output

# Multicycle Datapath

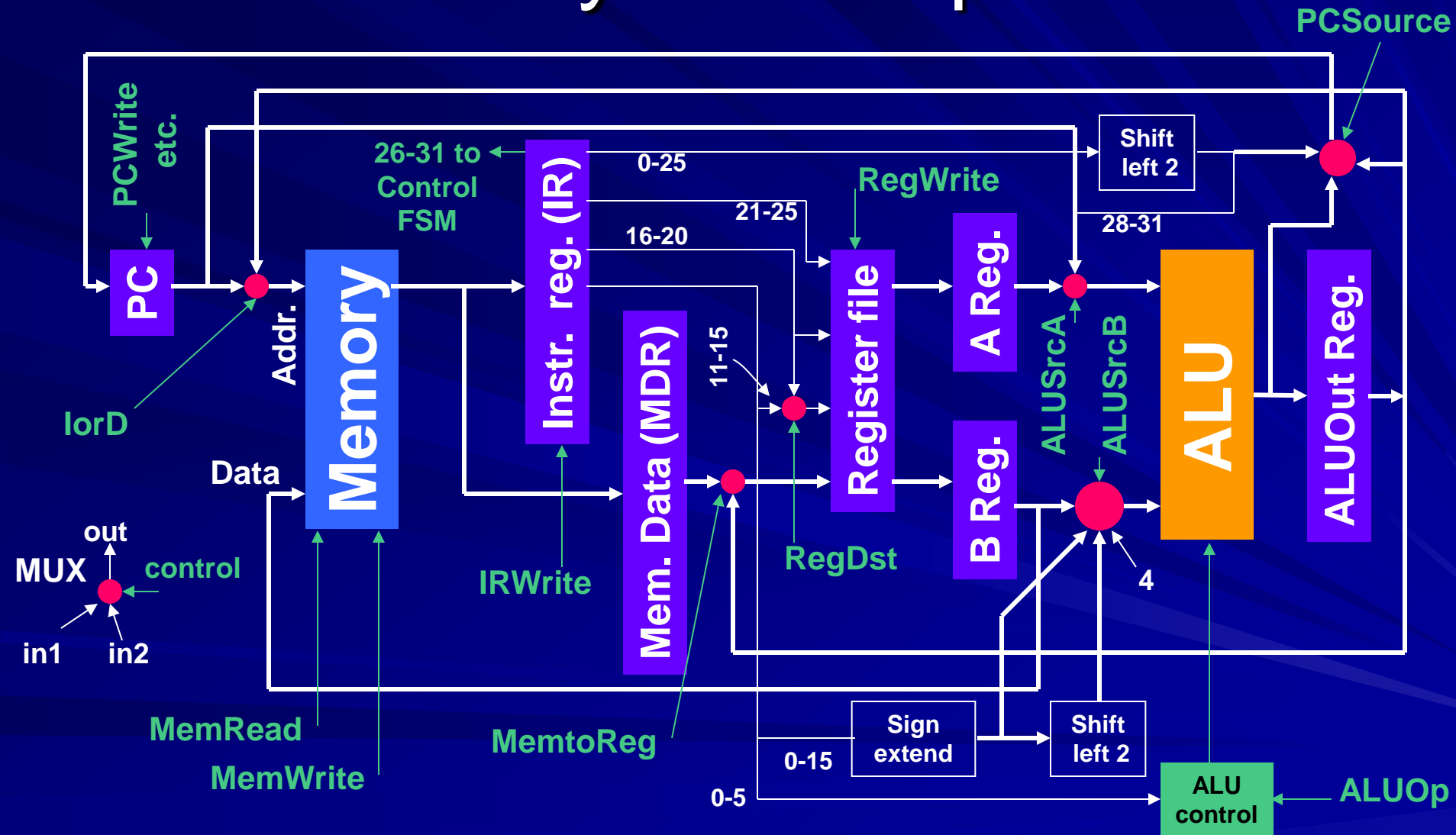

# 3 to 5 Cycles for an Instruction

Step	R-type (4 cycles)	Mem. Ref. (4 or 5 cycles)	Branch type (3 cycles)	J-type (3 cycles)
<b>Instruction fetch</b>	$IR \leftarrow \text{Memory}[PC]; PC \leftarrow PC+4$			
<b>Instr. decode/ Reg. fetch</b>	$A \leftarrow \text{Reg}(IR[21-25]); B \leftarrow \text{Reg}(IR[16-20])$ $ALUOut \leftarrow PC + (\text{sign extend } IR[0-15]) \ll 2$			
<b>Execution, addr. Comp., branch &amp; jump completion</b>	$ALUOut \leftarrow$ $A \text{ op } B$	$ALUOut \leftarrow$ $A + \text{sign extend}$ $(IR[0-15])$	<b>If (A= =B) then <math>PC \leftarrow ALUOut</math></b>	$PC \leftarrow PC[28-$ $31]$ $\parallel$ $(IR[0-25] \ll 2)$
<b>Mem. Access or R-type completion</b>	$\text{Reg}(IR[11-$ $15]) \leftarrow$ $ALUOut$	$MDR \leftarrow M[ALUout]$ or $M[ALUOut] \leftarrow B$		
<b>Memory read completion</b>		$\text{Reg}(IR[16-20]) \leftarrow$ $MDR$		

# Cycle 1 of 5: Instruction Fetch (IF)

## ■ Read instruction into IR, $M[PC] \rightarrow IR$

### ■ Control signals used:

■ <code>lorD</code>	=	0	select PC
■ <code>MemRead</code>	=	1	read memory
■ <code>IRWrite</code>	=	1	write IR

## ■ Increment PC, $PC + 4 \rightarrow PC$

### ■ Control signals used:

■ <code>ALUSrcA</code>	=	0	select PC into ALU
■ <code>ALUSrcB</code>	=	01	select constant 4
■ <code>ALUOp</code>	=	00	ALU adds
■ <code>PCSource</code>	=	00	select ALU output
■ <code>PCWrite</code>	=	1	write PC

# Cycle 2 of 5: Instruction Decode (ID)

	31-26	25-21	20-16	15-11	10-6	5-0
R	opcode	reg 1	reg 2	reg 3	shamt	fncode
I	opcode	reg 1	reg 2	word address increment		
J	opcode	word address jump				

- Control unit decodes instruction

- Datapath prepares for execution

- R and I types, reg 1 → A reg, reg 2 → B reg

- No control signals needed

- Branch type, compute branch address in ALUOut

- ALUSrcA = 0 select PC into ALU

- ALUSrcB = 11 Instr. Bits 0-15 shift 2 into ALU

- ALUOp = 00 ALU adds



# Cycle 3 of 5: Execute (EX)

- R type: execute function on reg A and reg B, result in ALUOut

- Control signals used:

■ ALUSrcA	=	1	A reg into ALU
■ ALUsrcB	=	00	B reg into ALU
■ ALUOp	=	10	instr. Bits 0-5 control ALU

- I type, lw or sw: compute memory address in ALUOut  $\leftarrow$  A reg + sign extend IR[0-15]

- Control signals used:

■ ALUSrcA	=	1	A reg into ALU
■ ALUSrcB	=	10	Instr. Bits 0-15 into ALU
■ ALUOp	=	00	ALU adds



# Cycle 3 of 5: Execute (EX)

- I type, beq: subtract reg A and reg B, write ALUOut to PC

- Control signals used:

- ALUSrcA = 1 A reg into ALU
- ALUsrcB = 00 B reg into ALU
- ALUOp = 01 ALU subtracts
- If zero = 1, PCSource = 01 ALUOut to PC
- If zero = 1, PCwriteCond = 1 write PC
- **Instruction complete, go to IF**

- J type: write jump address to PC  $\leftarrow$  IR[0-25] shift 2 and four leading bits of PC

- Control signals used:

- PCSource = 10
- PCWrite = 1 write PC
- **Instruction complete, go to IF**

# Cycle 4 of 5: Reg Write/Memory

## ■ R type, write destination register from ALUOut

### ■ Control signals used:

- **RegDst** = 1 Instr. Bits 11-15 specify reg.
- **MemtoReg** = 0 ALUOut into reg.
- **RegWrite** = 1 write register
- **Instruction complete, go to IF**

## ■ I type, lw: read M[ALUOut] into MDR

### ■ Control signals used:

- **lorD** = 1 select ALUOut as mem adr.
- **MemRead** = 1 read memory to MDR

## ■ I type, sw: write M[ALUOut] from B reg

### ■ Control signals used:

- **lorD** = 1 select ALUOut as mem adr.
- **MemWrite** = 1 write memory
- **Instruction complete, go to IF**

# Cycle 5 of 5: Reg Write

## ■ I type, lw: write MDR to reg[IR(16-20)]


### ■ Control signals used:

- RegDst = 0 instr. Bits 16-20 are write reg
- MemtoReg = 1 MDR to reg file write input
- RegWrite = 1 read memory to MDR
- **Instruction complete, go to IF**

For an alternative method of designing datapath, see  
N. Tredennick, *Microprocessor Logic Design, the Flowchart Method*,  
Digital Press, 1987.

# 1-bit Control Signals


Signal name	Value = 0	Value =1
RegDst	Write reg. # = bit 16-20	Write reg. # = bit 11-15
RegWrite	No action	Write reg. $\leftarrow$ Write data
ALUSrcA	First ALU Operand $\leftarrow$ PC	First ALU Operand $\leftarrow$ Reg. A
MemRead	No action	Mem.Data Output $\leftarrow$ M[Addr.]
MemWrite	No action	M[Addr.] $\leftarrow$ Mem. Data Input
MemtoReg	Reg.File Write In $\leftarrow$ ALUOut	Reg.File Write In $\leftarrow$ MDR
IorD	Mem. Addr. $\leftarrow$ PC	Mem. Addr. $\leftarrow$ ALUOut
IRWrite	No action	IR $\leftarrow$ Mem.Data Output
PCWrite	No action	PC is written
PCWriteCond	No action	PC is written if zero(ALU)=1

 

# 2-bit Control Signals

Signal name	Value	Action
ALUOp	00	ALU performs add
	01	ALU performs subtract
	10	Funct. field (0-5 bits of IR ) determines ALU operation
ALUSrcB	00	Second input of ALU $\leftarrow$ B reg.
	01	Second input of ALU $\leftarrow$ 4 (constant)
	10	Second input of ALU $\leftarrow$ 0-15 bits of IR sign ext. to 32b
	11	Second input of ALU $\leftarrow$ 0-15 bits of IR sign ext. and left shift 2 bits
PCSource	00	ALU output (PC +4) sent to PC
	01	ALUOut (branch target addr.) sent to PC
	10	Jump address IR[0-25] shifted left 2 bits, concatenated with PC+4[28-31], sent to PC


# Control: Finite State Machine

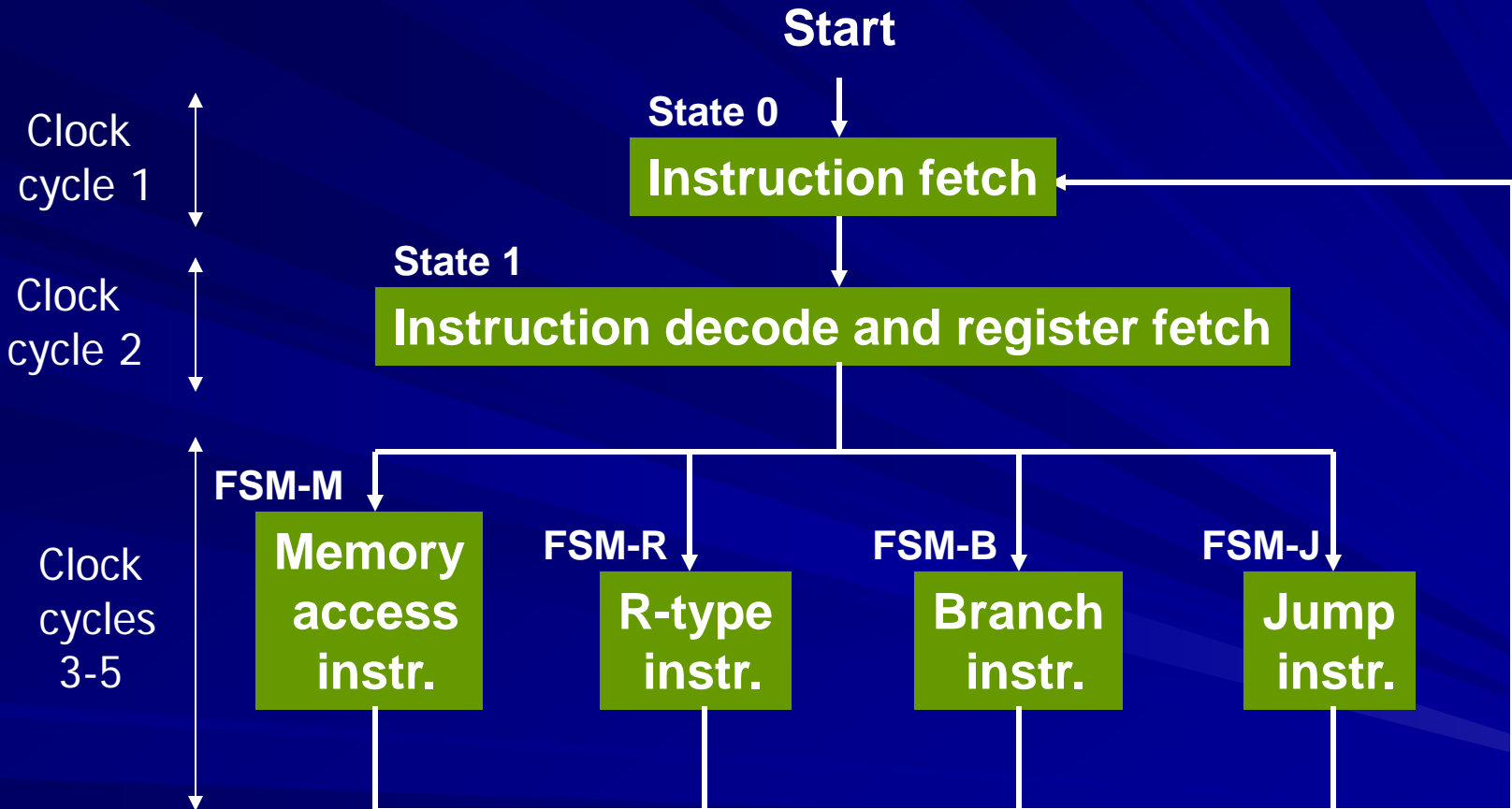




# State 0: Instruction Fetch (CC1)

PCSource=00

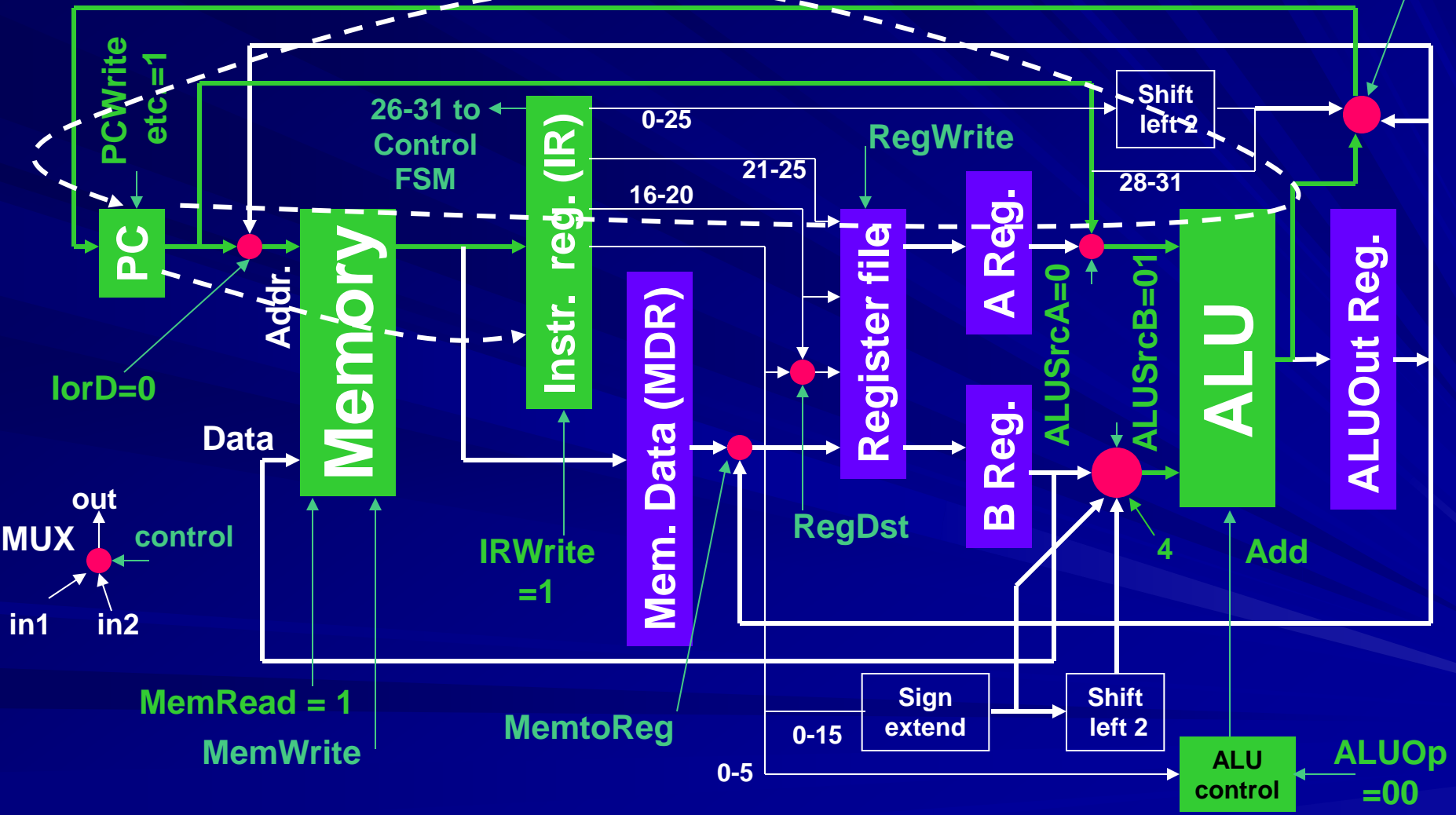





# State 0 Control FSM Outputs

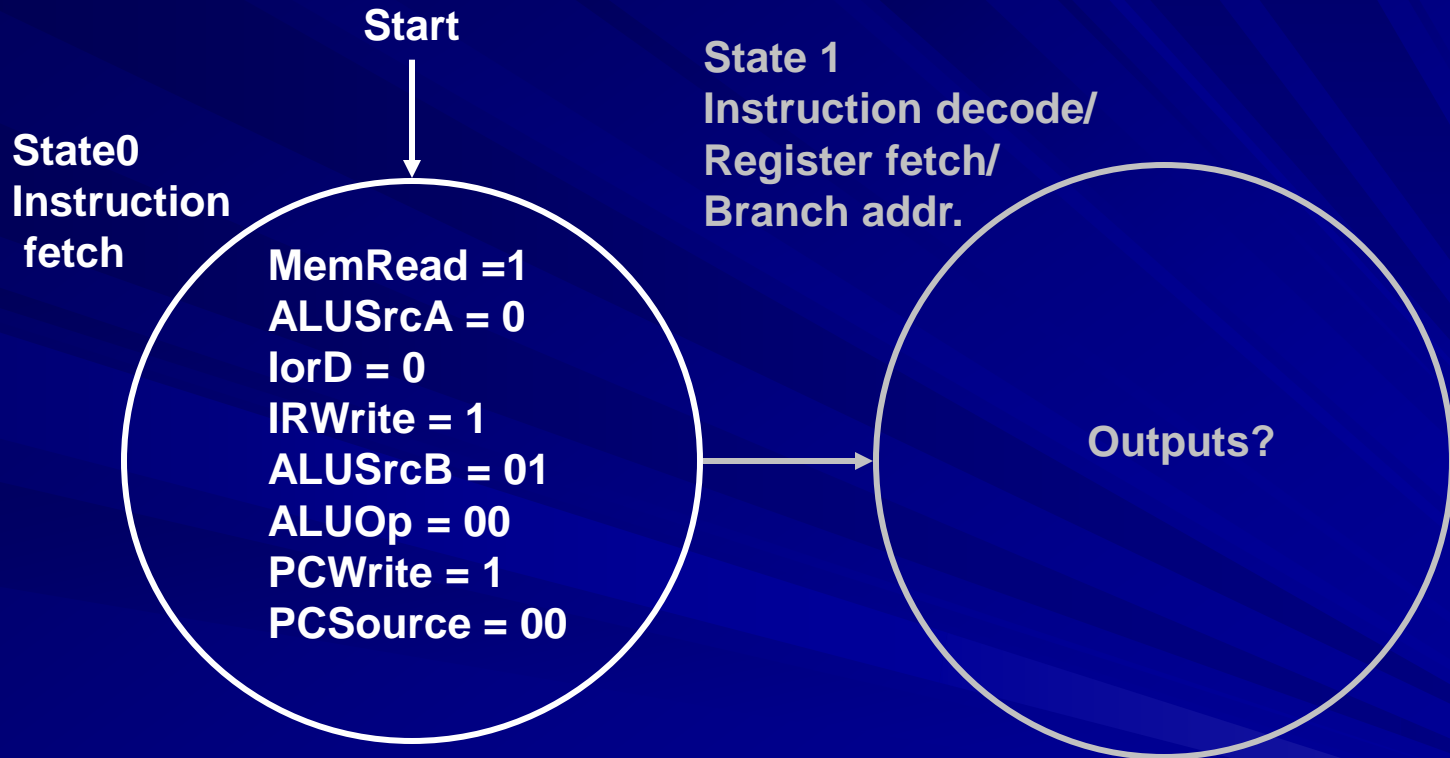

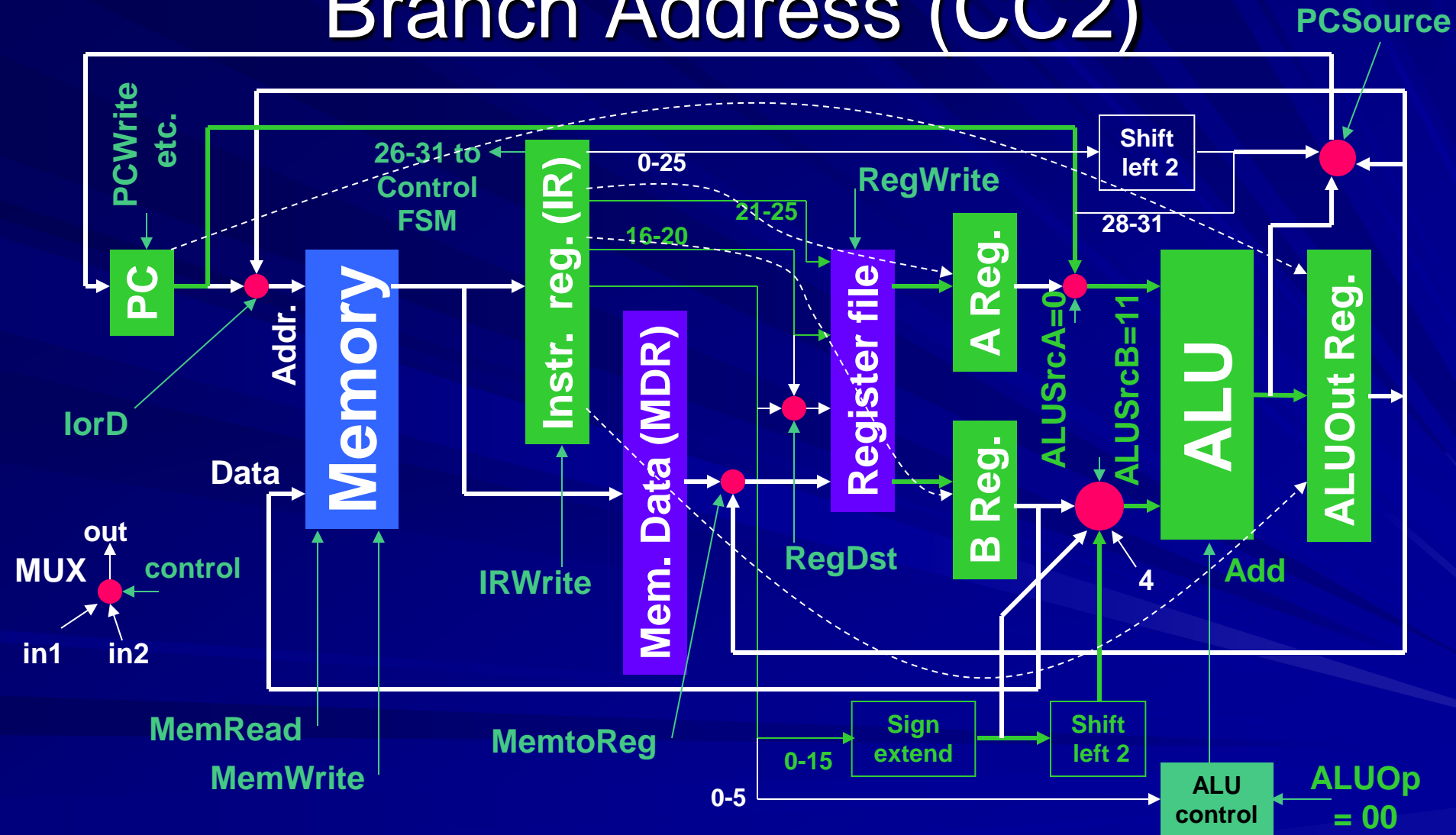
# State 1: Instr. Decode/Reg. Fetch/ Branch Address (CC2)




# State 1 Control FSM Outputs

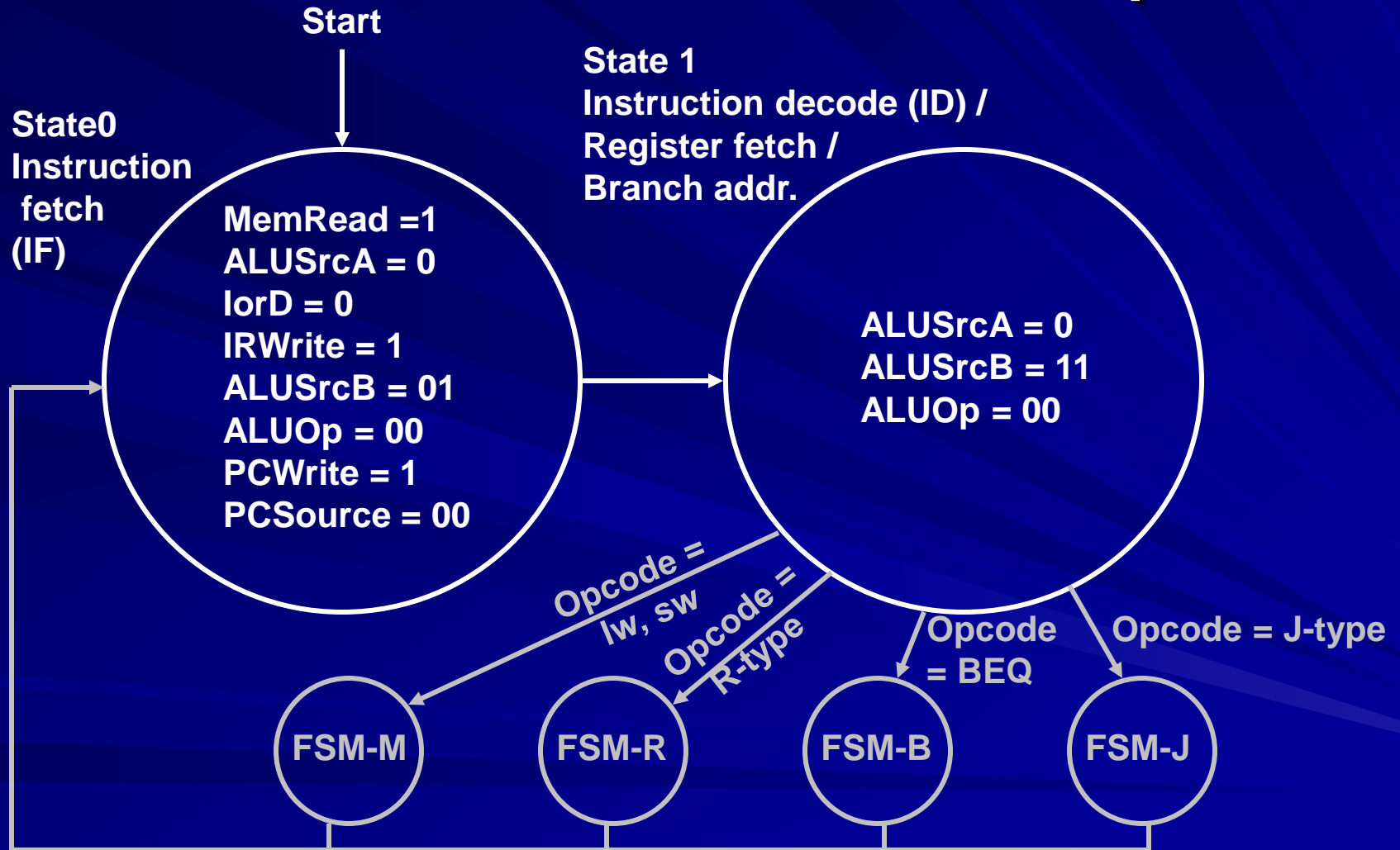


# State 1 (Opcode = lw) → FSM-M (CC3-5)

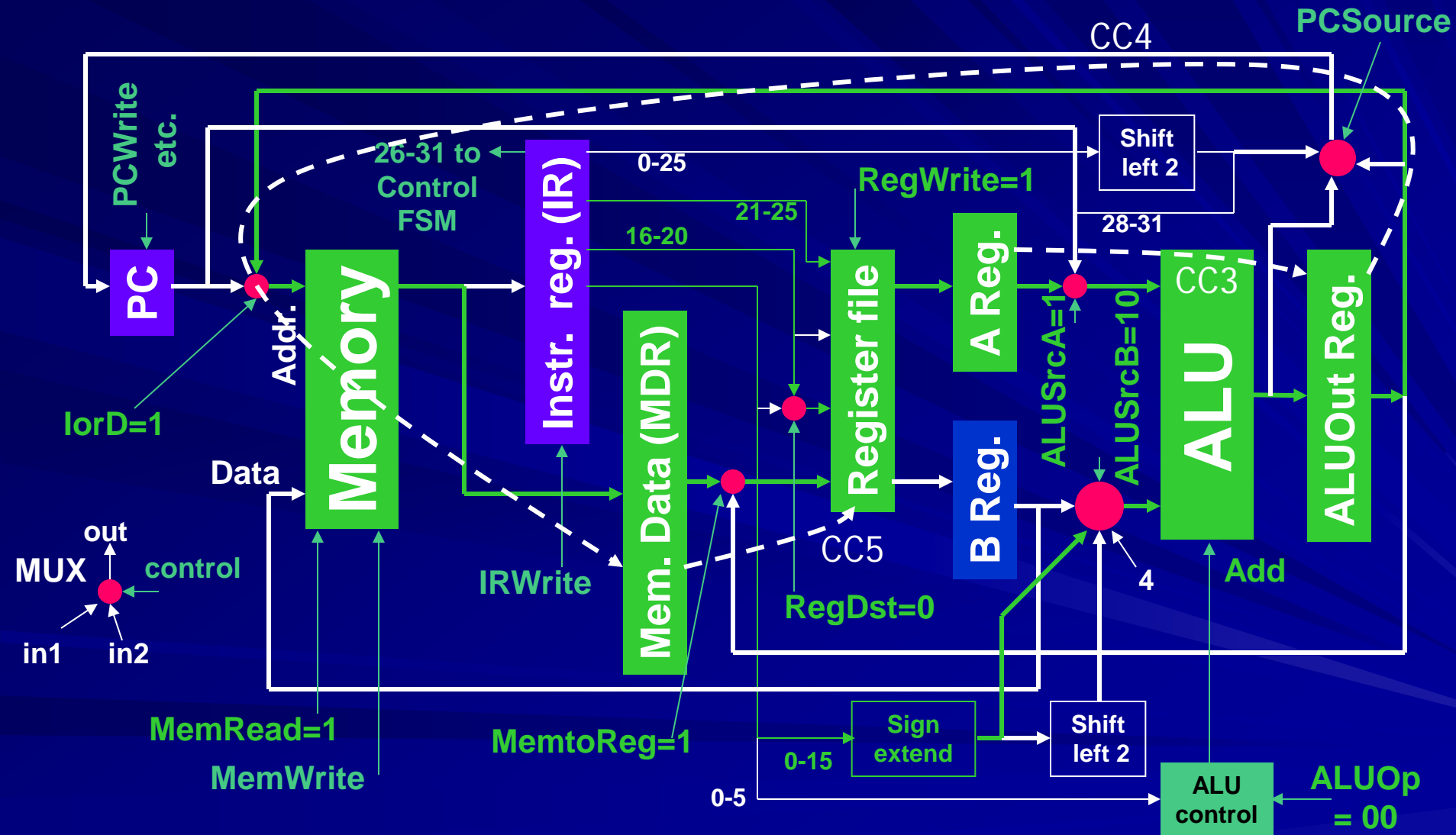


# State 1 (Opcode= sw) → FSM-M (CC3-4)

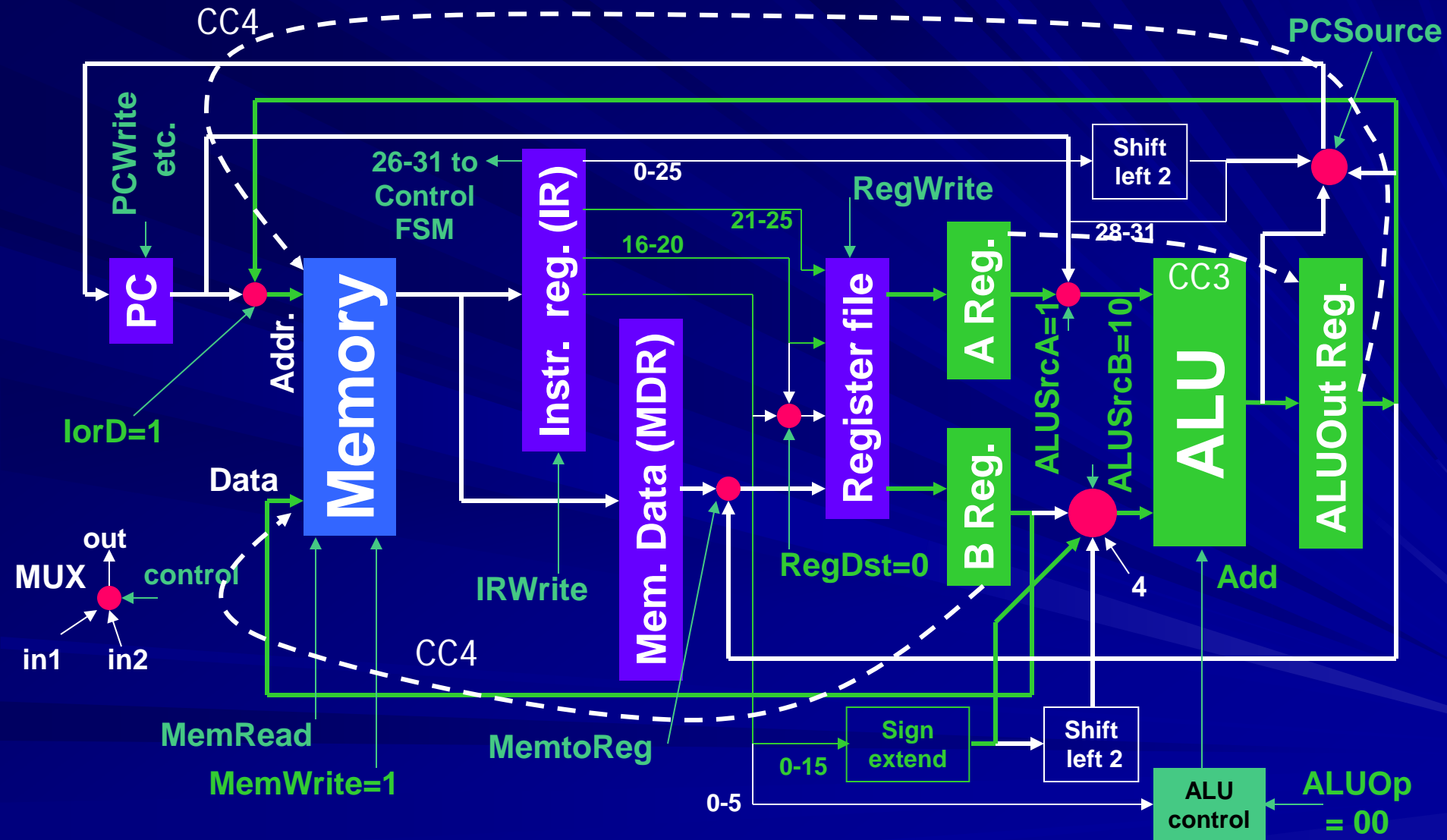

# FSM-M (Memory Access)

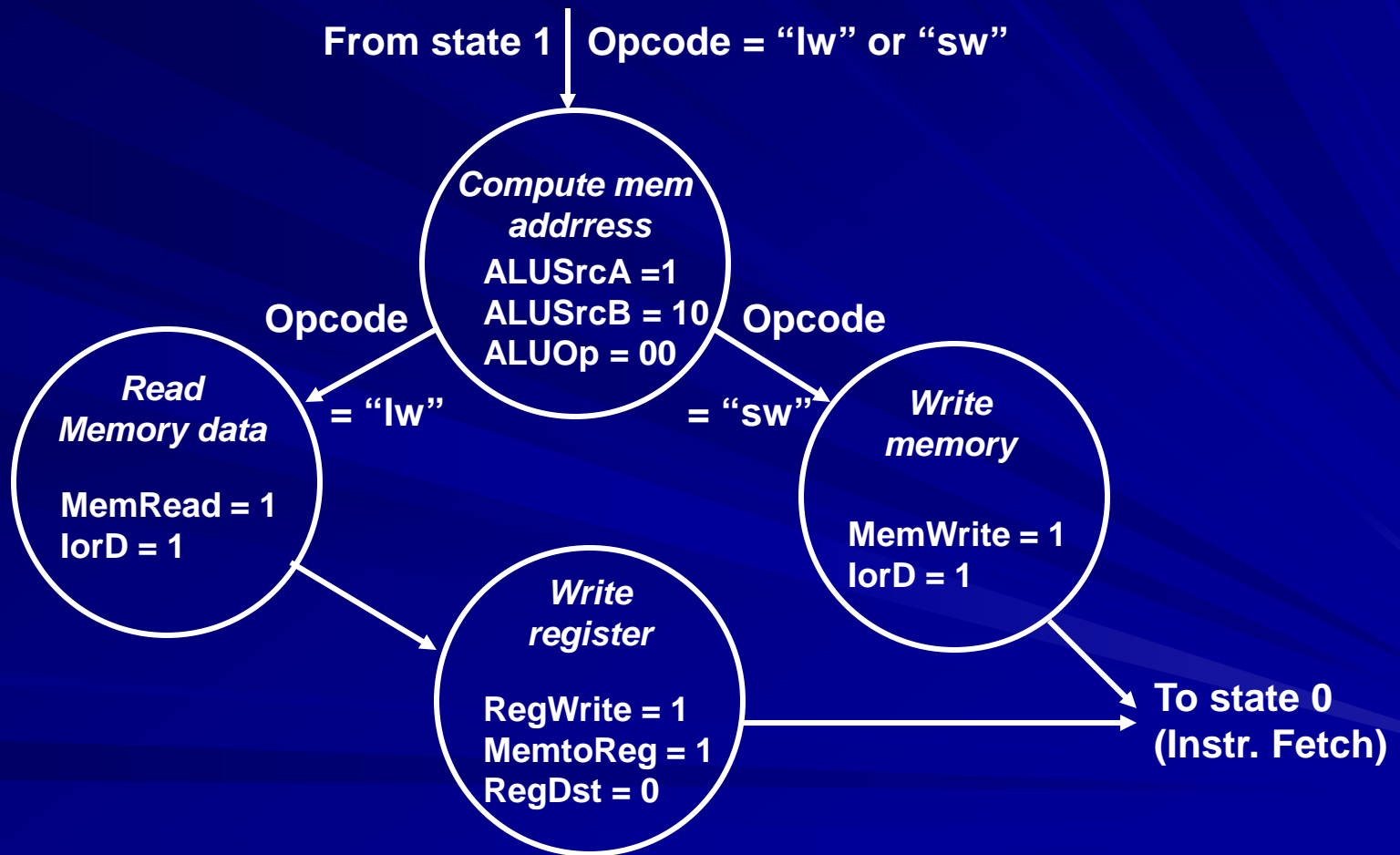

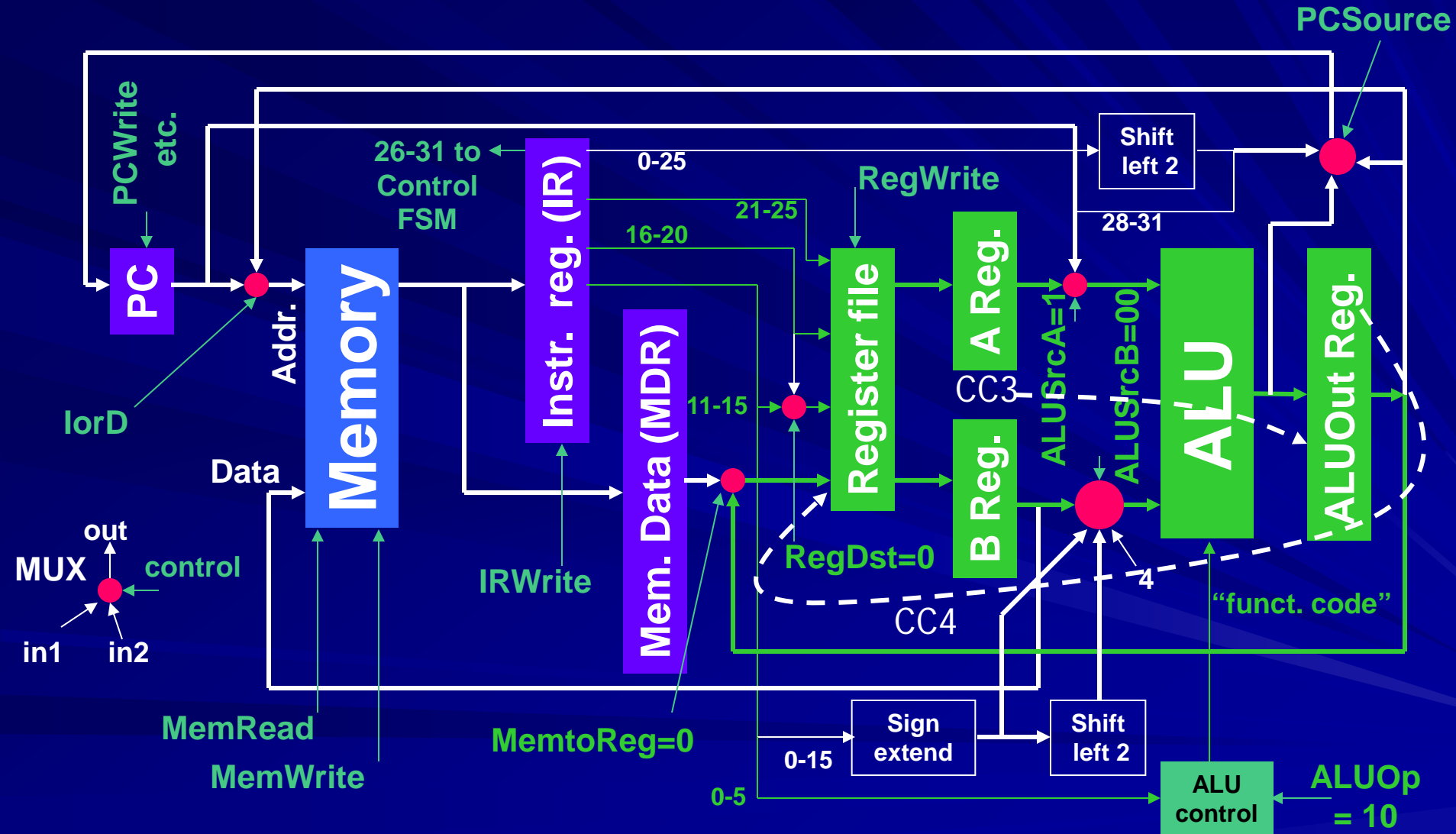
# State 1 (Opcode=R-type) → FSM-R (CC3-4)






# FSM-R (R-type Instruction)

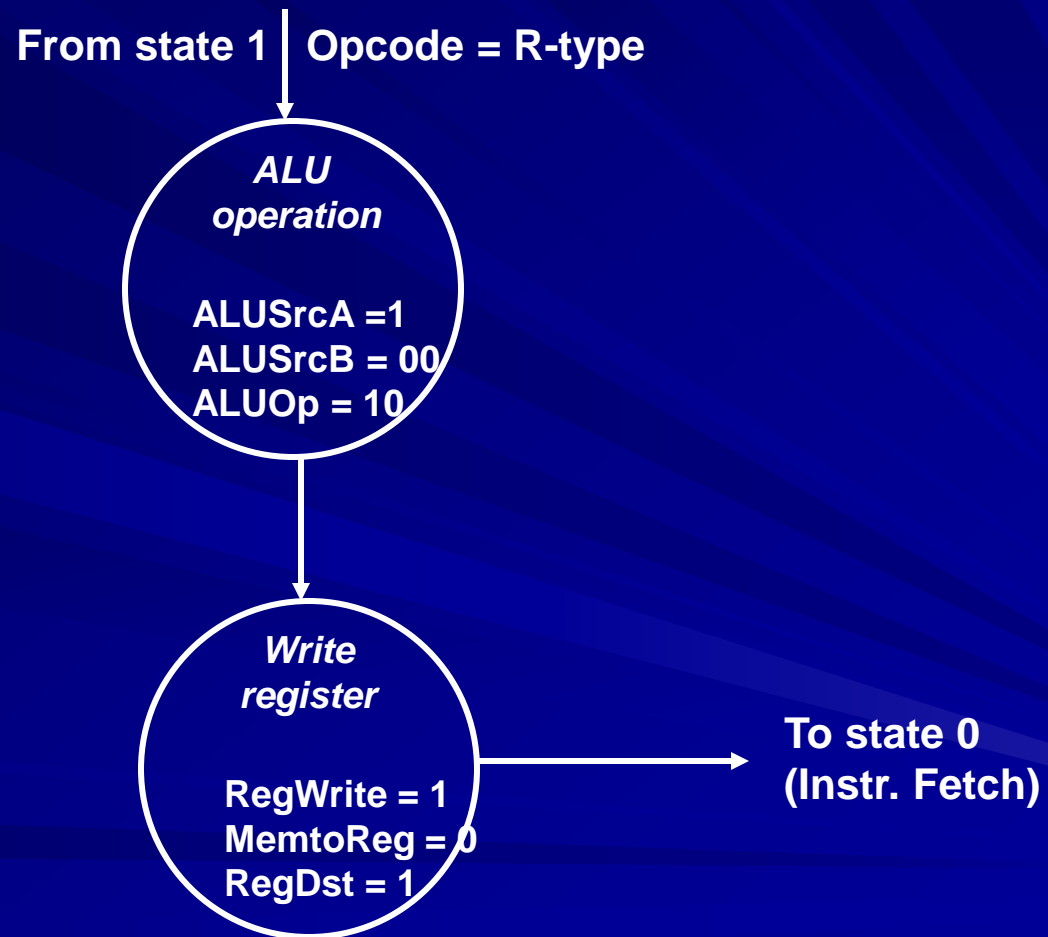


# State 1 (Opcode = beq) → FSM-B (CC3)

If(zero)

PCSource  
01

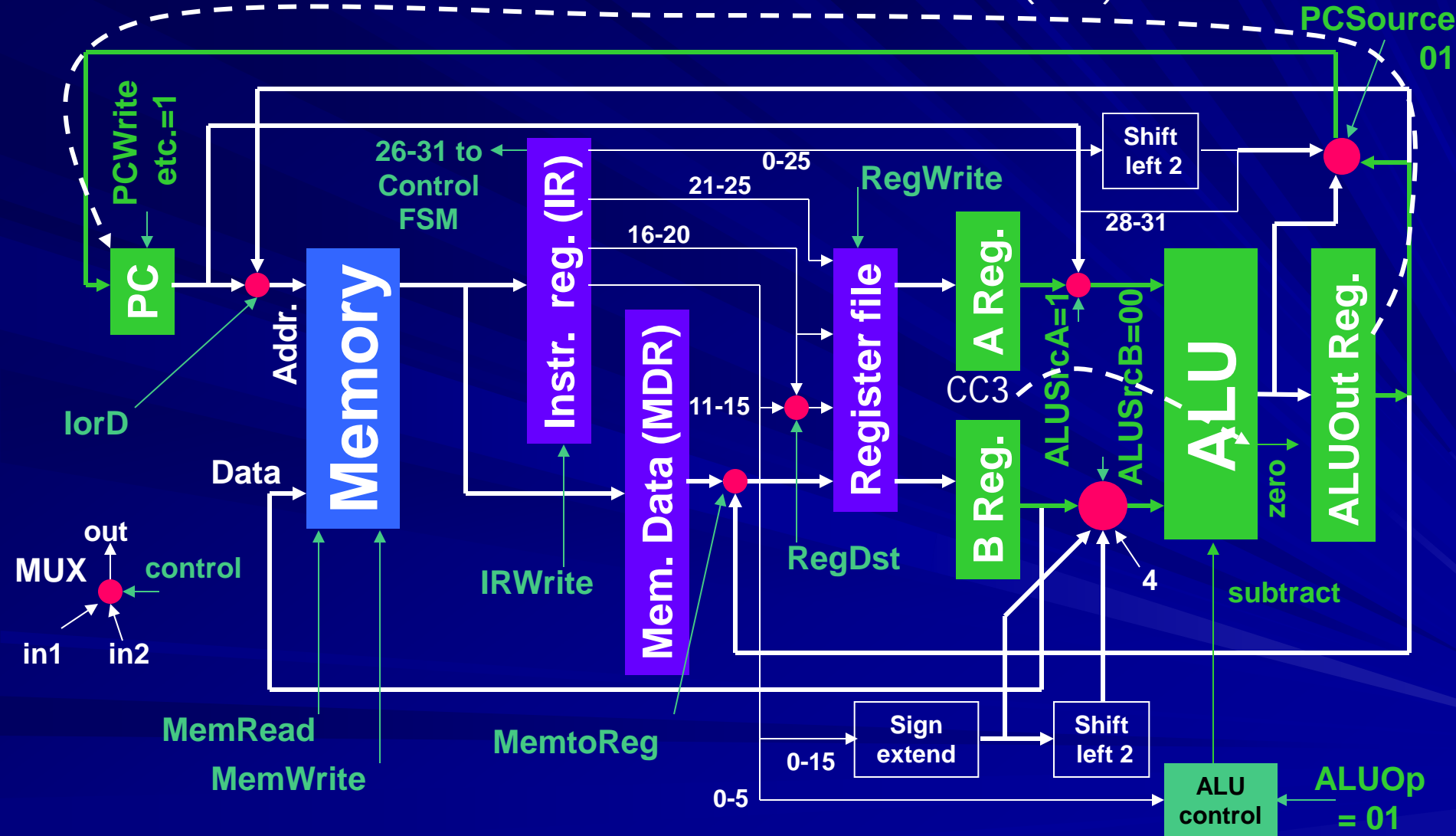

# Write PC on “zero”

 

PCWrite = 1, unconditionally write PC  
Cycle 1, fetch  
Cycle 3, jump

# FSM-B (Branch)

From state 1 | Opcode = "beq"

*Write PC on  
branch condition*


ALUSrcA = 1  
ALUSrcB = 00  
ALUOp = 01  
PCWriteCond=1  
PCSource=01

*Branch condition:*


*If  $A - B = 0$   
zero = 1*

To state 0  
(Instr. Fetch)

# State 1 (Opcode = j) → FSM-J (CC3)

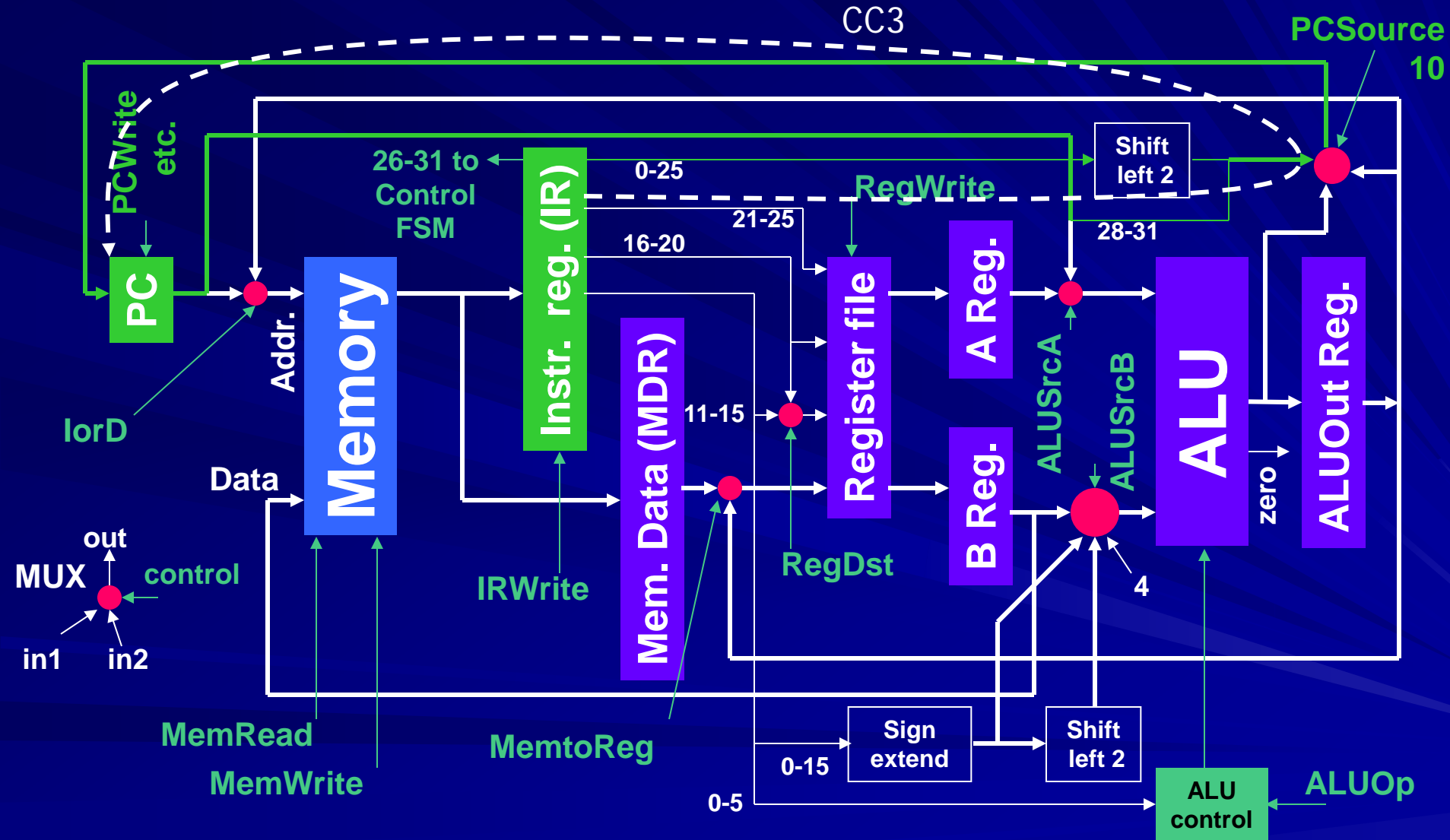


# Write PC

 


PCWrite = 1, unconditionally write PC  
Cycle 1, fetch  
Cycle 3, jump

# FSM-J (Jump)

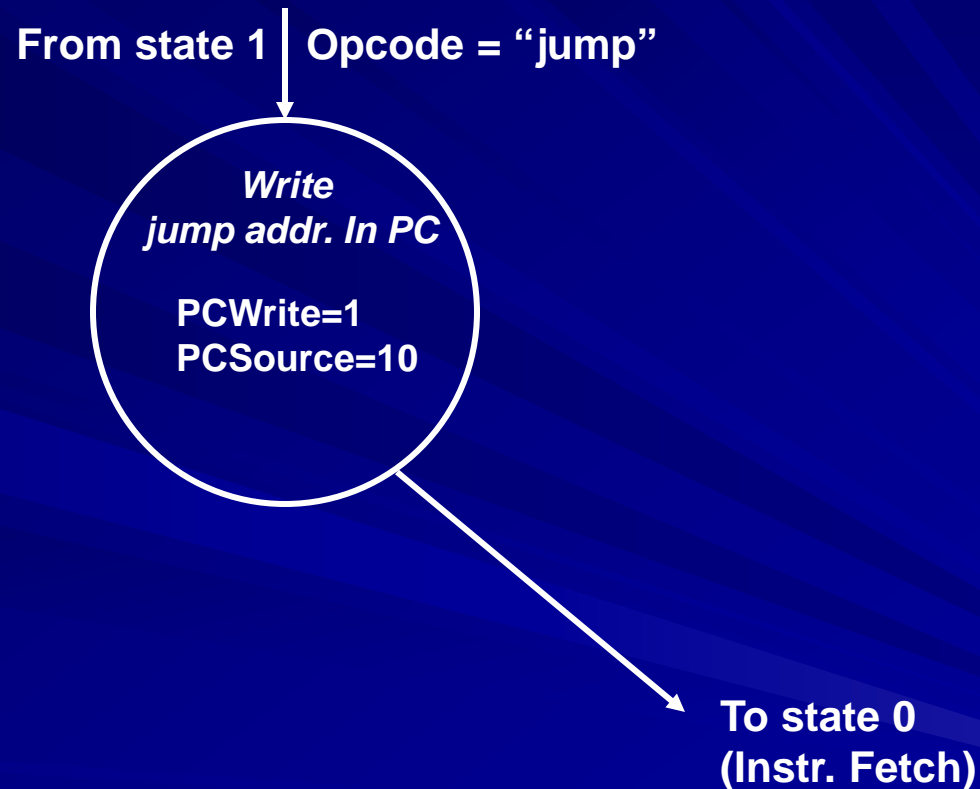




# Control FSM

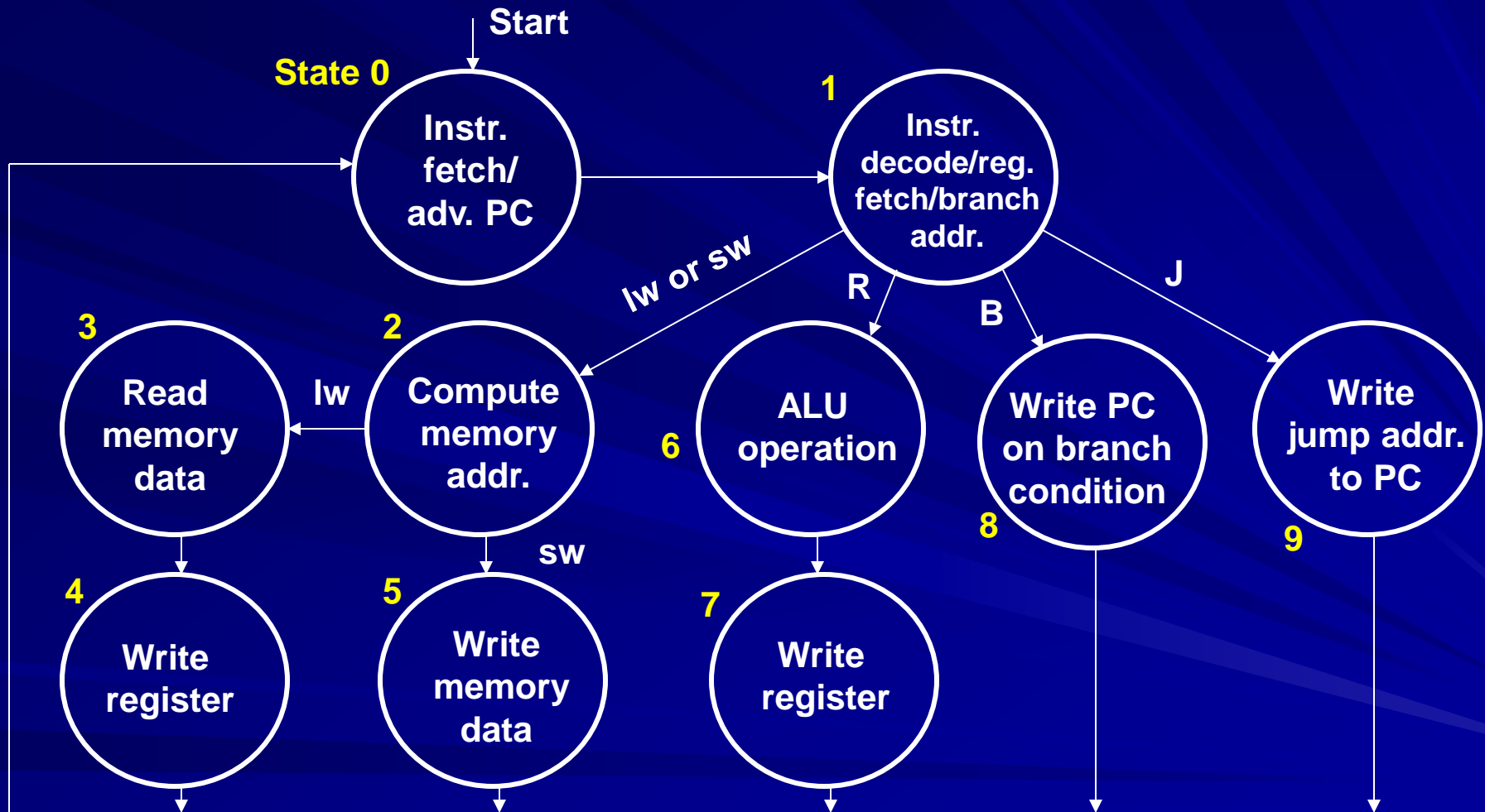

# Control FSM (Controller)

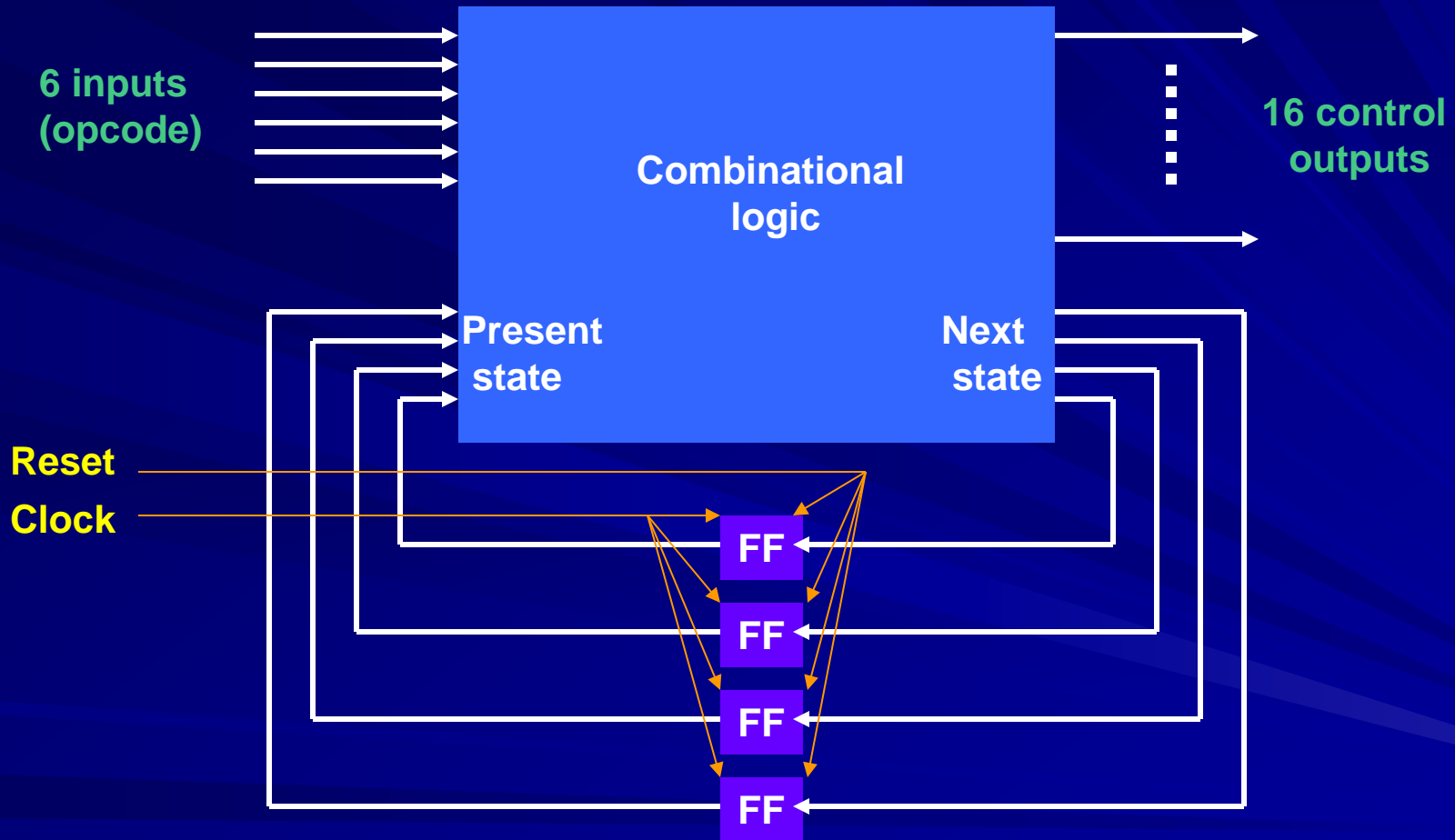


# Designing the Control FSM

- Encode states; need 4 bits for 10 states, e.g.,
  - State 0 is 0000, state 1 is 0001, and so on.
- Write a truth table for combinational logic:

Opcode	Present state	Control signals	Next state
000000	0000	0001000110000100	0001
.....	.....	.....	.....

- Synthesize a logic circuit from the truth table.
- Connect four flip-flops between the next state outputs and present state inputs.


# Block Diagram of a Processor

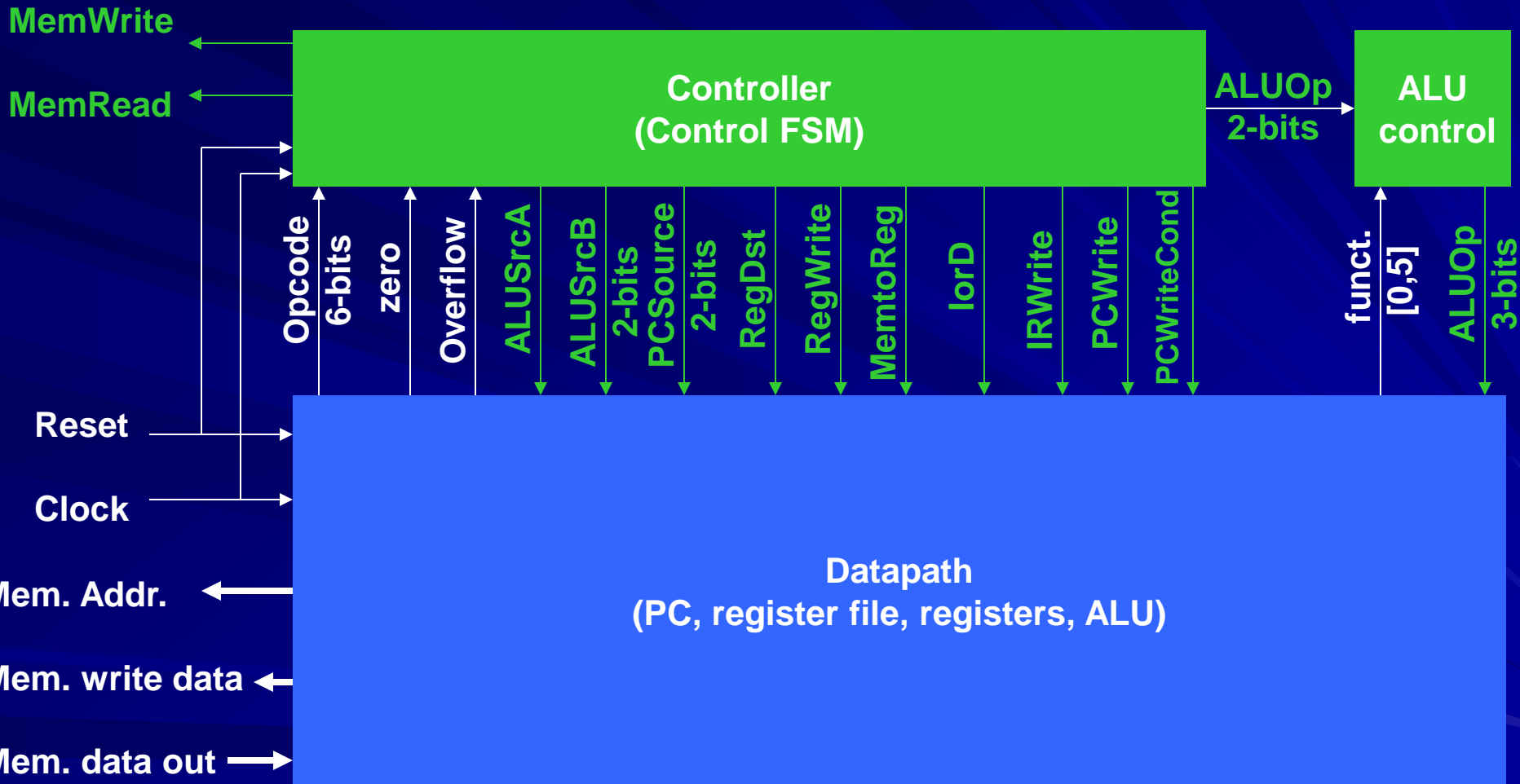

# Exceptions or Interrupts

- Conditions under which the processor may produce incorrect result or may “hang”.
  - Illegal or undefined opcode.
  - Arithmetic overflow, divide by zero, etc.
  - Out of bounds memory address.
- EPC: 32-bit register holds the affected instruction address.
- Cause: 32-bit register holds an encoded exception type. For example,
  - 0 for undefined instruction
  - 1 for arithmetic overflow

# Implementing Exceptions

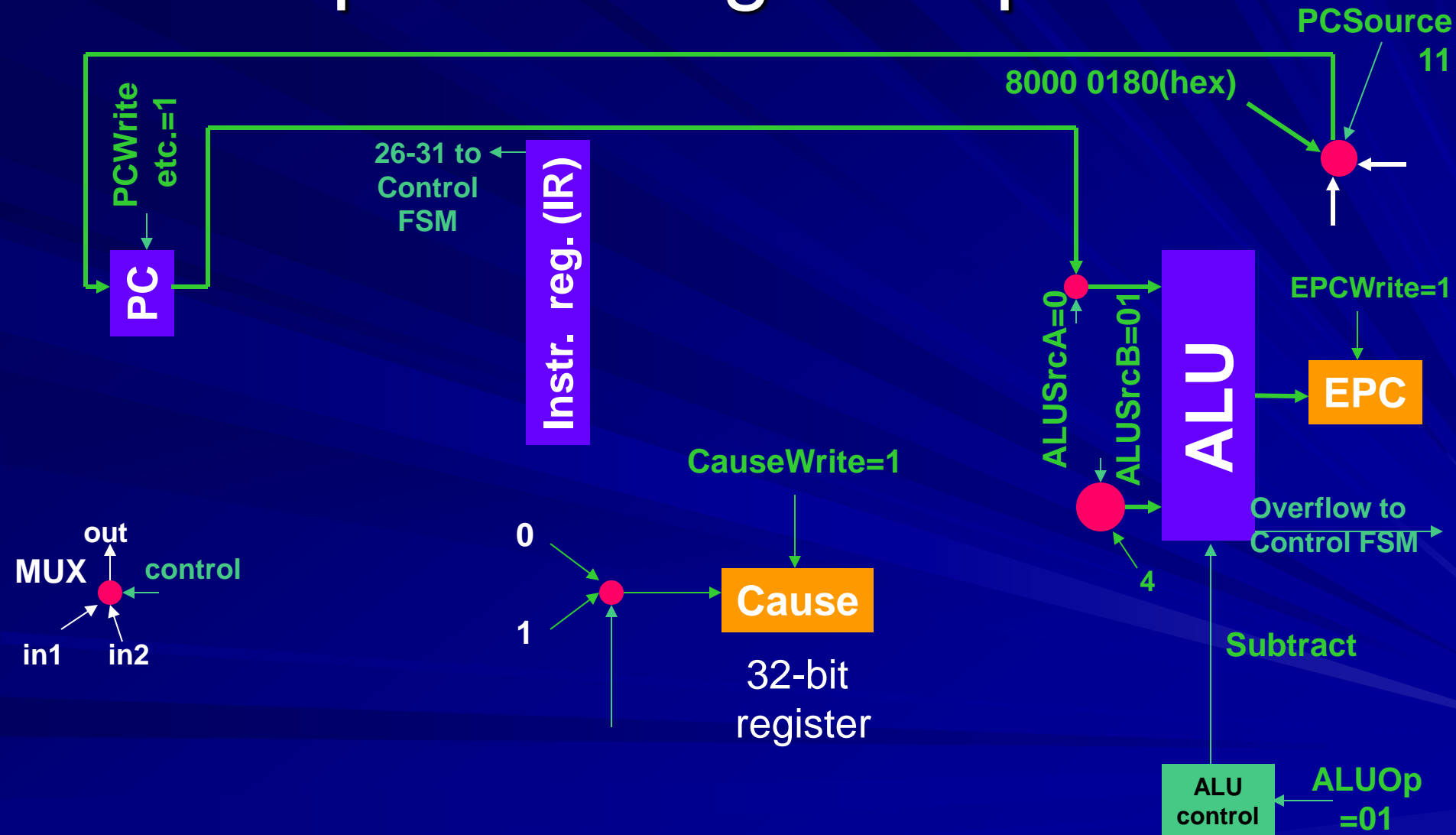


# How Long Does It Take? Again

- Assume control logic is fast and does not affect the critical timing. Major time components are ALU, memory read/write, and register read/write.
- Time for hardware operations, suppose
  - Memory read or write 2ns
  - Register read 1ns
  - ALU operation 2ns
  - Register write 1ns



# Single-Cycle Datapath

- R-type 6ns
  - Load word (I-type) 8ns
  - Store word (I-type) 7ns
  - Branch on equal (I-type) 5ns
  - Jump (J-type) 2ns
  - **Clock cycle time = 8ns**
  - Each instruction takes *one* cycle
- 

# Performance Parameters

- Average cycles per instruction (CPI)
- Cycle time (clock period,  $T$ )
- Execution time of a program
- For single-cycle datapath:
  - $CPI = 1$
  - $T =$  hardware time for lw instruction
  - Execution time of a program  
$$= T \times CPI \times (\text{Total instructions executed})$$

# Multicycle Datapath

- Clock cycle time is determined by the longest operation, ALU or memory:

- Clock cycle time = 2ns

- Cycles per instruction:

■ lw	5	(10ns)
■ sw	4	(8ns)
■ R-type	4	(8ns)
■ beq	3	(6ns)
■ j	3	(6ns)

# CPI of a Multicycle Computer

$$\text{CPI} = \frac{\sum_k (\text{Instructions of type } k) \times \text{CPI}_k}{\sum_k (\text{instructions of type } k)}$$

where

$$\text{CPI}_k = \text{Cycles for instruction of type } k$$

*Note: CPI is dependent on the instruction mix of the program being run. Standard benchmark programs are used for specifying the performance of CPUs.*

# Example

## ■ Consider a program containing:

■ loads	25%
■ stores	10%
■ branches	11%
■ jumps	2%
■ Arithmetic	52%

■ CPI =  $0.25 \times 5 + 0.10 \times 4 + 0.11 \times 3 + 0.02 \times 3 + 0.52 \times 4$   
= 4.12 for multicycle datapath

■ CPI = 1.00 for single-cycle datapath

# Multicycle vs. Single-Cycle

$$\begin{aligned} \text{Performance ratio} &= \text{Single cycle time} / \text{Multicycle time} \\ &= \frac{(\text{CPI} \times \text{cycle time}) \text{ for single-cycle}}{(\text{CPI} \times \text{cycle time}) \text{ for multicycle}} \\ &= \frac{1.00 \times 8\text{ns}}{4.12 \times 2\text{ns}} = 0.97 \end{aligned}$$

*Single cycle is faster in this case, but is it always so?*

# Consider Another Example

## ■ For this program:

■ loads	5%
■ stores	5%
■ branches	30%
■ jumps	10%
■ Arithmetic	50%

$$\begin{aligned}\text{■ CPI} &= 0.05 \times 5 + 0.05 \times 4 + 0.30 \times 3 + \\ &\quad 0.10 \times 3 + 0.50 \times 4 \\ &= 3.65 \text{ for multicycle datapath}\end{aligned}$$

$$\text{■ CPI} = 1.00 \text{ for single-cycle datapath}$$



# Multicycle vs. Single-Cycle

$$\begin{aligned} \text{Performance ratio} &= \text{Single cycle time} / \text{Multicycle time} \\ &= \frac{(\text{CPI} \times \text{cycle time}) \text{ for single-cycle}}{(\text{CPI} \times \text{cycle time}) \text{ for multicycle}} \\ &= \frac{1.00 \times 8\text{ns}}{3.65 \times 2\text{ns}} = 1.096 \end{aligned}$$

*Multicycle is faster in this case, so the performance ratio depends on the instruction mix. Can we do better?*

# Next: Pipelining