

Chapter outline



Sunday, June 10, 2012 10:38 AM

MOSFET Chapter Outline

- Describe field effects and operation of MOSFETs.
- Understand cutoff, linear and saturation operation regions for given circuit.
- Develop mathematical models for I-V characteristics of MOSFETs.
- Develop concept of load line for MOSFET circuits
- Analyze operation of resistor load inverter
- Describe sources of capacitance in MOSFETs.
- Master dc/dc sweep simulation of MOSFET circuits using spice, including spice model parameter editing and W/L specification

N-channel (electron channel) MOS Field Effect Transistor

Sunday, June 10, 2012 10:39 AM

 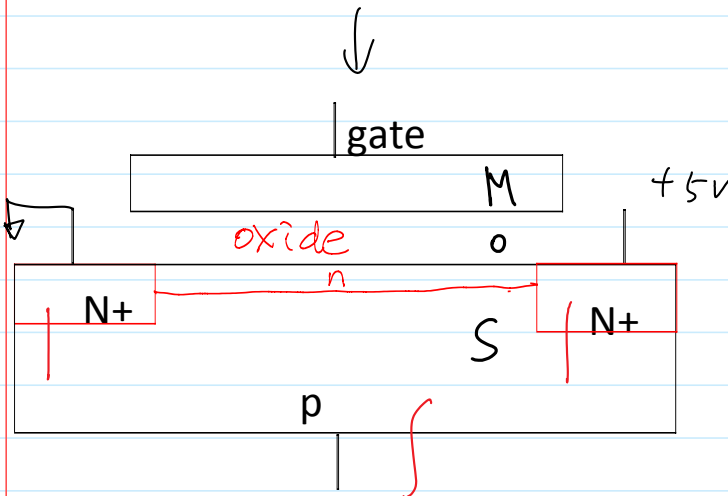


circuit symbol

arrow points from P-body -> N-channel

n-channel MOSFET
shared by all

- p-substrate
- gate and gate oxide
- two N+ regions (meaning ND is high)
- Gate bias can be used to invert the surface from p-type to n-type, creating an electron channel connecting the two N+
- we can thus control current flowing between the two N+ using gate bias


Other Symbols of N-MOSFET:

 


175

in our text

body not shown

 


 2 terminal MOS Capacitor Physical Structure



- (**M**etal) Gate electrode: low-resistivity metal in early days, and later polycrystalline silicon (N^+ or P^+ for low resistivity) - now metal again in year 2011
- (**O**xide) Silicon dioxide: stable high-quality electrical insulator. T_{ox} is as thin as 1-2nm in state of the art technologies
- (**S**emiconductor) Semiconductor substrate or Body: n - or p -type Si

 What happens in an ordinary capacitor if we apply a voltage difference (vertical field)?



$$Q = C \cdot V$$


$$C = \text{Area} \cdot \frac{\epsilon_{ox}}{t_{ox}}$$

$$C'_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

We will induce negative charge - electrons on the negative metal plate in an ordinary capacitor.

- ★ If the negative plate is p-type semiconductor instead of metal, at lower voltage, the negative charge is initially made of ionized acceptors (Na), when the capacitor voltage exceeds a threshold, electrons are induced at the surface, we say the surface is inverted (as it was p-type at voltages below threshold, now is n-type at voltages above threshold). In fact, the positive electrode is semiconductor too, say, N+ Si.

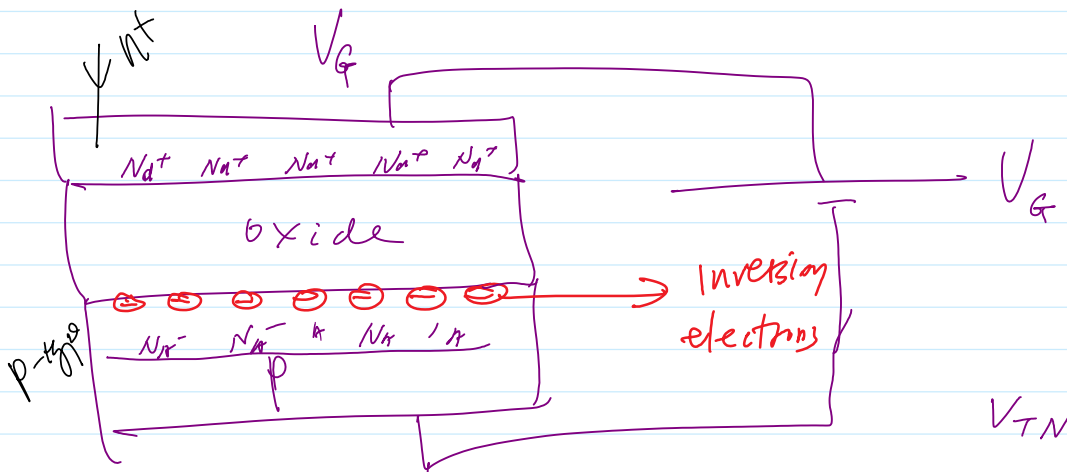What happens in an N+/oxide/p-Si capacitor if we apply a voltage difference?



$$C_{ox}'' = \frac{\epsilon_{ox}}{t_{ox}}$$


$$Q_I' = -C_{ox}'' (V_G - V_{TH})$$

$$\approx 0$$

$$V_G \geq V_{TH}$$

$$V_G \leq V_{TH}$$

 Vertical Field Effect in nMOS (p-substrate)



If V_G is sufficiently small compared to a threshold, surface is accumulated with holes.

Surface is depleted of electrons and holes

At high enough V_G , vertical field is strong enough to induce electrons at the surface of p-body.

Surface is now inverted from p-type to n-type electrically.

Vertical Field Induced Inversion Charge Density (charge per unit area)

area)

Inversion electron charge density to first order:

$$Q_I' = -C_{ox}''(V_G - V_{TN})$$

V_{TN} : is called **threshold voltage**, the threshold gate voltage level for creating significant amount of inversion charge

the *negative sign* simply indicates the **charge is made of inversion electrons**

$C_{ox}'' = \epsilon_{ox}/t_{ox}$ is oxide capacitance per unit area

ϵ_{ox} = oxide permittivity (F/cm)

t_{ox} = oxide thickness (cm)


Equation only applicable when $V_{GS} > V_{TH}$!!!
That is, the number of inversion electrons must be positive!

Numerical Example:

Consider a ~~state-of-the-art 22nm technology~~ MOS capacitor with $V_T = 0.2V$, $t_{ox} = 1nm$.

1) Find the number of inversion electrons induced per square nm area (nm^2) at $V_g = 1.2V$.

 2) For a $66nm \times 22nm$ area MOS cap in the 22nm CMOS technology above, how many inversion electrons are induced at $V_g = 1.2V$?



$$Q_I' = -C_{ox}''(V_g - V_{TH}^{0.2V})$$

$$C_{ox}'' = \frac{\epsilon_{ox}}{t_{ox} \ll 1nm}$$

$$Q_{inv}' = -C_{ox}''(V_g - V_T) = -\frac{\epsilon_{ox}}{t_{ox}}(V_g - V_T)$$

$$Q_{inv} = -C_{ox} (V_g - V_T) = -\frac{\epsilon_{ox}}{t_{ox}} (V_g - V_T)$$

$$N_{inv} = \frac{Q_{inv}}{-q}$$

$$N = N_{inv} \times 66 \text{ nm} \times 22 \text{ nm}$$

Solution:

oxide permittivity = $3.9 * \epsilon_{0}$

ϵ_{0} : vacuum permittivity,

$\epsilon_{0} = 8.854187817620 \times 10^{-14} \text{ F/cm}$

```
epox_r = 3.9 # dimensionless
ep0 = 8.85e-14 # F/cm
nm_to_cm = 1e-7
cm_to_nm = 1./nm_to_cm
epox = epox_r * ep0
```

```
tox_nm = 1
tox_cm = tox_nm * nm_to_cm
```

```
coxpp = epox / tox_cm # F / cm^2
```

```
vt = 0.2
vg = 1.2
vgt = vg - vt
```

```
area_nm2 = 66 * 22
```

```
qinvp = coxpp * vgt # F*V/cm^2, so C/cm^2
q = 1.6e-19
```

```
num_electrons_per_cm2 = qinvp / q
```

```
num_electrons_per_nm2 = num_electrons_per_cm2 * (nm_to_cm)**2
```

```
print 'For tox = %3.1f nm, VT = %3.1f V, %g electrons are induced per nm^2 area
at %3.1f V gate voltage' % (tox_nm, vt, num_electrons_per_nm2, vg)
```

For $t_{ox} = 1.0 \text{ nm}$, $V_T = 0.2 \text{ V}$, 0.215719 electrons are induced per nm^2 area at 1.2 V gate voltage


For an area of 1452.0 nm^2 , 313.224 electrons are induced

q	float	1.6e-19
qinvp	float	3.4515000000000003e-06
tox_cm	float	1e-07
tox_nm	int	1
vg	float	1.2
vgt	float	1.0
vt	float	0.2

area_nm2	float	1452.0
cm_to_nm	float	10000000.0
coxpp	float	3.4515000000000003e-06
ep0	float	8.85e-14
epox	float	3.4515e-13
epox_r	float	3.9
main	function	<function main at 0x0377F230>
nm_to_cm	float	1e-07
num_electrons	float	313.223625
num_electrons_per_cm2	float	21571875000000.004
num_electrons_per_nm2	float	0.21571875000000001


N-MOS Field Effect Transistor (n-MOSFET)

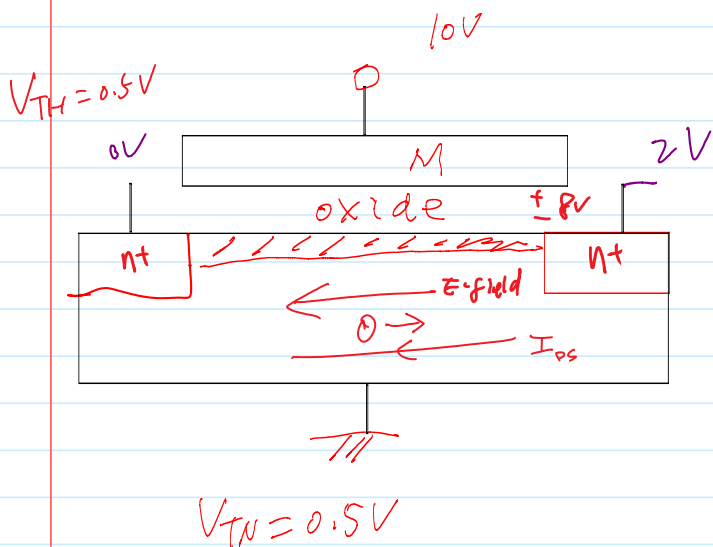
- Substrate is **p-type**, there are two n+ regions
- assume $V_{TN} = 0.5V$, if we apply 10V at the gate, such that $V_{GS} (10V) > V_{TN}$, the surface is **inverted** to n-type
- The two N+ regions are now connected by the **inverted n-surface, or channel**
- now let us add 2V to the second N+ region, the first N+ region is grounded, to which direction should electrons drift?



- What is direction of electron drift motion?
- What is direction of current flow?
- Which n+ is source of electron flow? (left, right)
- Which n+ is drain of electron flow? (left, right)

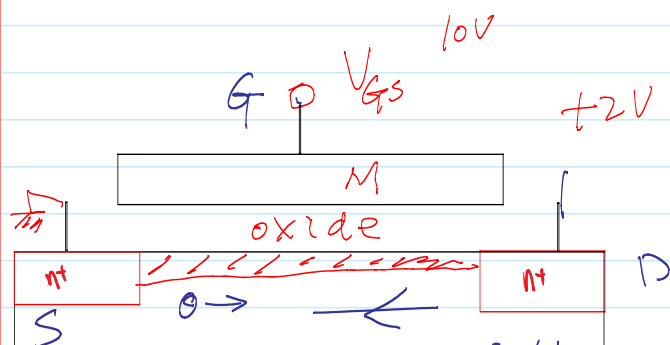- Electrons drift from lower voltage N+ to higher voltage N+
- So the lower voltage N+ region is the Source of electron flow and the higher voltage N+ region is the Drain of electron flow (exit)
- current flows from Drain to Source



 

In NMOSFET:

**Higher Voltage N+ side is
(Electrical) Drain**

**Lower voltage N+ side is
(Electrical) Source**


**Electrical source/drain is
determined electrically and can
dynamically change from time
to time!**

**Current flows from Drain to
Source!**

**Drain and Source
Exercise for n-MOSFET**

$$V_T = 1V$$


$$V_{xT} = V_x - V_T$$

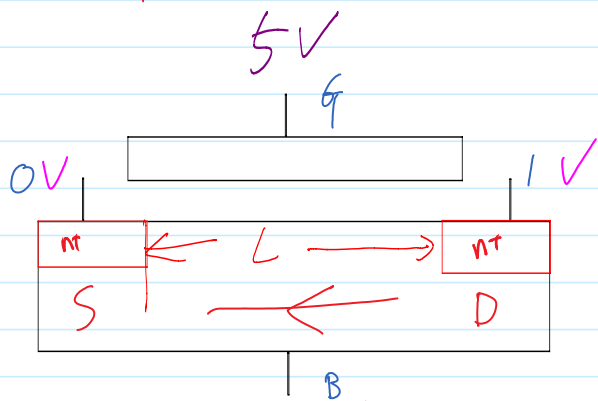

-2V Body

$$V_{GS} = ? \quad 5V$$


$$V_{DS} = ? \quad 1V$$

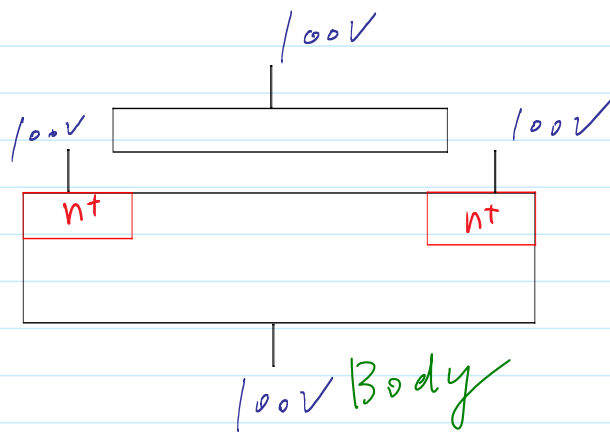


$$V_{GS} = ? \quad 0$$

$$V_{DS} = ? \quad 0$$

A 3-D Picture / Gate Width

 

$$\frac{W}{L}$$

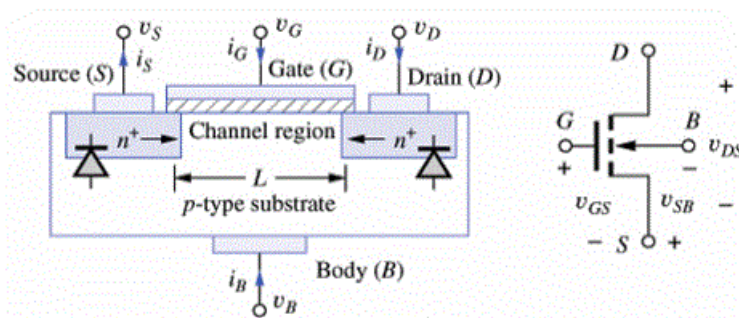

- 4 device terminals: Gate(G), Drain(D), Source(S) and Body(B).
- Source and drain regions form pn junctions with substrate.
- v_{SB} , v_{DS} and v_{GS} always positive during normal operation.
- v_{SB} always $<$ v_{DS} and v_{GS} to reverse bias pn junctions


Cutoff Operation Region ($V_{GS} < V_{TN}$)

Turn-on Region ($V_{GS} \geq V_{TN}$)

- Linear Region ($V_{DS} < V_{GT}$)
- Saturation Region ($V_{DS} \geq V_{GT}$)

$V_{GS} - V_{TN}$
 V_{TH}

Inversion Charge Density Along channel

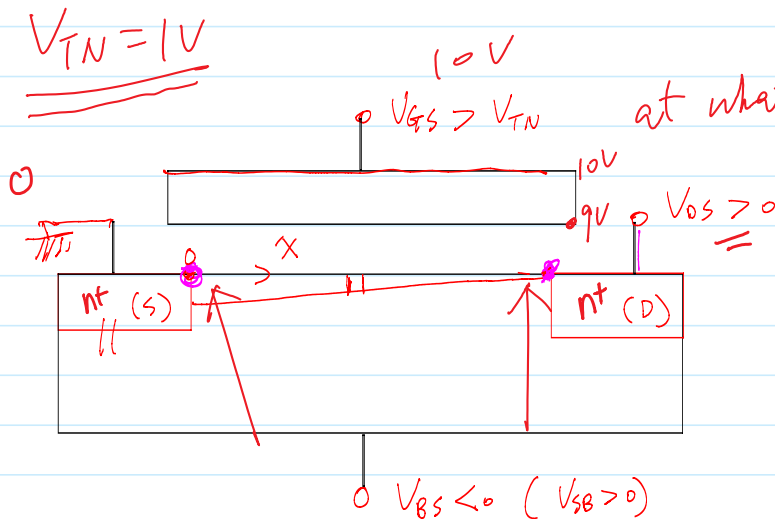

at what V_{DS} $Q'_I(x=L) = 0$?

thickness of red channel indicates inversion charge density

thicker means higher

$$Q'_I(x) = -C_{ox}'' (V_{GS} - V(x) - V_{TN})$$

$V_{GS} - V(x)$: Net voltage available to induce an inversion layer, it decreases from S to D

$V(x) = 0$ at $x = 0$ (S end)

$$V(x) = 0 \quad \text{at } x=0 \quad (\text{S end})$$

$$V(x) = V_{DS} \quad \text{at } x=L \quad (\text{D end})$$

$$Q_I'(x=L) = -C_{ox}'' (V_{GS} - V_{DS} - V_{TN})$$

layer, it decreases from S to D

$V(x)$: potential at x with respect to source

Difference between Net Voltage and threshold voltage determines inversion charge density
net voltage must be above threshold to produce inversion charge


Inversion charge density at source is:

$$Q_{IS}' = -C_{ox}''(V_{GS} - V_{TN})$$

Inversion charge density at drain is:

$$Q_{ID}' = -C_{ox}''(V_{GS} - V_{DS} - V_{TN})$$

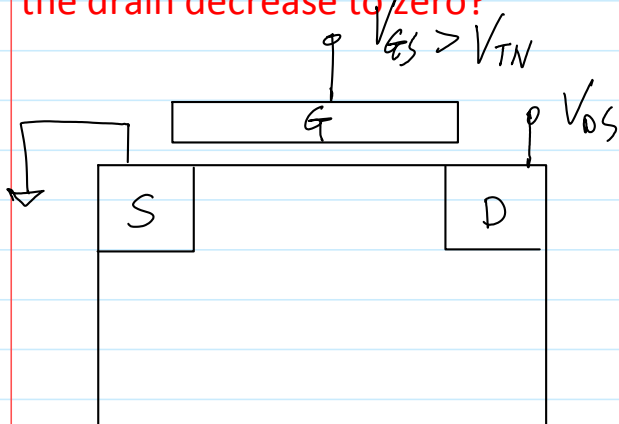Question: at what V_{DS} will the inversion charge at the drain decrease to zero?



The **linear** or triode **region** of operation is defined as one in which the **entire channel** region between source and drain is **inverted**.

$$V_{GS} > V_{TH}, \quad 0 < V_{DS} < V_{GT}$$

$$V_{GT} \triangleq V_{GS} - V_{TH}$$

Again, for a given V_{GS} , at what V_{DS} does the inversion charge density at drain become zero?

$$V_{DS} < V_{GS} - V_{TN}$$

Drain end inversion charge decreases to "zero" or


VGD is just equal to threshold voltage (V_{TN})

$$V_{GD} = V_{GS} - V_{DS}$$

$$V_{GD} = V_{TN}$$

So MOSFET is in linear operation region when $0 < V_{DS} < V_{GS} - V_{TN}$

or $0 < V_{DS} < V_{GT}$

 


Gate Overdrive VGT:

VGT = VGS - VTN is called the gate bias overdrive, the amount of overdrive with respect to threshold voltage V_{TN}

MOSFET Operation Regions

$V_{DS} \uparrow$

$$V_{DS} = V_{GS} - V_{TH}$$


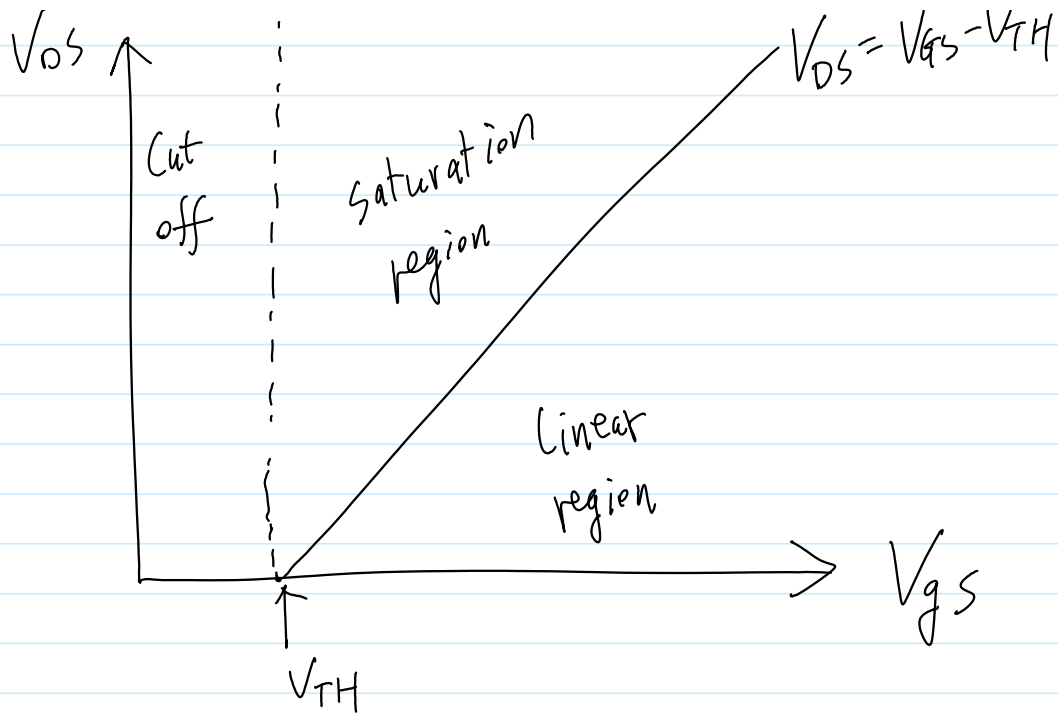


When $0 < V_{DS} < V_{GS} - V_{TH}$, NMOS works in linear region.

When $V_{DS} > V_{GS} - V_{TH}$, NMOS works in saturation region, so $V_{GS} - V_{TH}$ is also called Drain Saturation Voltage V_{DSAT} .


MOSFET I-V Equation Derivation Proper

MOSFET I_{DS} Equation derivation

  

Consider a small segment from

x to $x + \Delta x$

 

$$-C_{ox}'' (V_{gs} - V(x) - V_T)$$

$$\downarrow$$

$$Q_n' \cdot W \cdot \Delta x$$

Recall definition of current

$$I = \frac{\text{charge inside the bar}}{\text{time for all charges to move out}}$$

$$= \frac{W \cdot Q_n' \cdot \Delta x}{\frac{\Delta x}{v_n}}$$

$$= W Q_n' v_n$$

$$= W Q_n' V_n$$

Q_n' is electron charge per area

$$Q_n'(x) = -C_{ox}'' (V_{GS} - V(x) - V_{TN})$$


$$V_n = -\mu_n \cdot E = -\mu_n \cdot \left(-\frac{dV}{dx}\right)$$

$$I = -W C_{ox}'' \mu_n (V_{GT} - V(x)) \frac{dV}{dx}$$

$$-I dx = W C_{ox}'' \mu_n (V_{GT} - V(x)) dV(x)$$

$$V_{GT} \triangleq V_{GS} - V_{TN}$$

gate over drive

 

define I_{DS} (I from d to s)

$$\text{So } I_{DS} = -I$$

$$K' (kP) = \mu_n C_{ox}''$$


$$\int_0^L I_{DS} dx = W C_{ox}'' \mu_n \left[\int_{x=0}^L V_{GT} \cdot dV - \int_{x=0}^L V dV \right]$$

$$I_{DS} \cdot L = W C_{ox}'' \mu_n \left[V_{GT} (V_{DS} - 0) - \frac{1}{2} (V_{DS}^2 - 0^2) \right]$$

KP

$$K_n \triangleq K_n' \cdot \frac{W}{L}$$
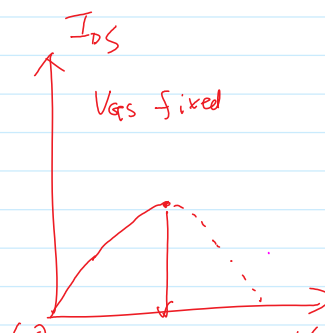
$$I_{DS} = \frac{W}{L} C_{ox}'' \mu_n \left[V_{GT} V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$



Keep in mind this holds

only when


$$Q_n(x) = -C_{ox}'' (V_{GT} - V(x)) < 0$$

or the number of inversion electrons > 0 .

That is $V_{GT} - V(x) > 0$

or

$$V(x) < V_{GT}$$

 



Recall $V(x)$ is highest at $x=L$

So as long as $V_{DS} < V_{GT}$,

this equation holds. That is

$$0 < V_{DS} < V_{GT}$$


Linear operation region.

  

$$Q_n(x=L) = -C_{ox}'' (V_{GT} - V_{DS})$$

$$V_{GT} - V_{DS} > 0 < 0$$

$$V_{DS} < V_{GT}$$

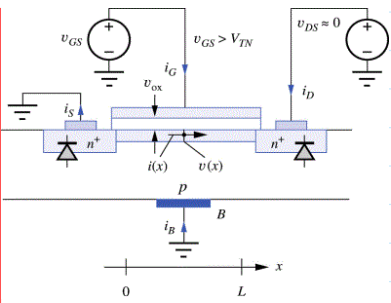

$$I_{DS} = 0 \quad \text{if } V_{GS} < V_{TN}$$

$$\text{if } 0 < V_{DS} < V_{DSAT} \quad (V_{GT} \triangleq V_{GS} - V_T)$$

$$I_{DS} = K_n \left(V_{GT} - \frac{V_{DS}}{2} \right) V_{DS} \quad \leftarrow$$


$$K_n = K_n' \cdot \frac{W}{L} \quad \underline{\underline{K_n}} = \mu_n C_{ox} \frac{W}{L}$$

$$\text{If } V_{DS} > V_{DSAT} \quad (V_{GT})$$

$$I_{DS} = I_{DSAT} = K_n \cdot \frac{V_{GT}^2}{2} \quad \leftarrow$$

Id-Vd output curves

Friday, September 28, 2012 9:03 AM

 

① First identify which n^+ is S and D

② $V_{DS} > 0$ $V_{SB} > 0$


$$K_n = K_n' \frac{W}{L} \quad K_n' = \mu_n C_{ox}$$

If $V_{GS} < V_{TN}$, $I_D \approx 0$, device is "off"

else

if $0 < V_{DS} < V_{GT}$, $I_D = K_n \cdot \left(V_{GT} \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$ Linear

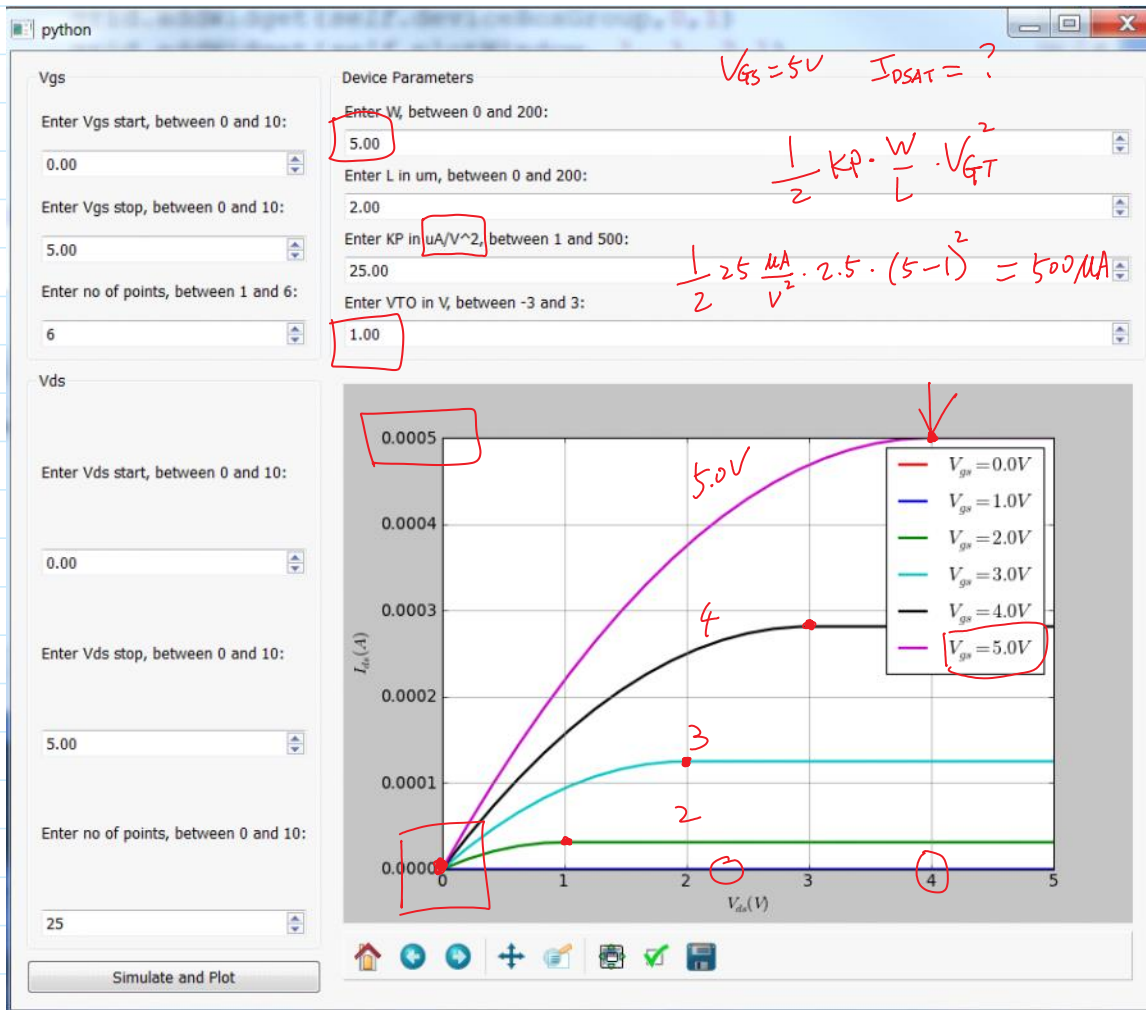if $V_{DS} \geq V_{GT}$, $I_D = K_n \cdot \frac{V_{GT}^2}{2}$ Saturation



Note where the drain current saturates with V_{ds} - it occurs at $V_{ds} = V_{gt}$ ($V_{gs} - V_t$)

In our text, V_t for NMOS is written as V_{tn} .

I'd like you to remember some critically important biasing conditions at which $I_{ds} = 0$:

- $V_{ds} = 0$ independent of V_{gs}
- $V_{gs} < V_t$ independent of V_{ds}

Determining NMOS current

Sunday, June 10, 2012 11:04 AM

Determining N-MOSFET Current

First figure out S, D, G, B

Figure out VGS, VDS, VTN

Calculate gate overdrive VGT=VGS-VTN

If VGT < 0, device is in cutoff (or off), IDS = 0

If VGT > 0, device is on. Vdsat = VGT


If Vds < Vdsat, Ids follows Ids = Kn * (VGT - Vds/2) * Vds,

If Vds > Vdsat, Ids saturates at constant value Idsat, independent of vDS.

I_{dsat} is simply Ids at Vds=Vdsat,

$$I_{dsat} = k_n * V_{gt}^2 / 2$$

Summary:

 

① First identify which n⁺ is S and D

② V_{DS} > 0 V_{SB} > 0

$$K_n = K_n' \frac{W}{L} \quad K_n' = \mu_n C_{ox}$$

If $V_{GS} < V_{TN}$, $I_D \approx 0$, device is "off"

else

if $0 < V_{DS} < V_{GT}$, $I_D = K_n \cdot \left(V_{GT} \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$ Linear



if $V_{DS} \geq V_{GT}$, $I_D = K_n \cdot \frac{V_{GT}^2}{2}$ Saturation

end



V_{DS} ↑

$$V_{DS} = V_{GS} - V_{TH}$$

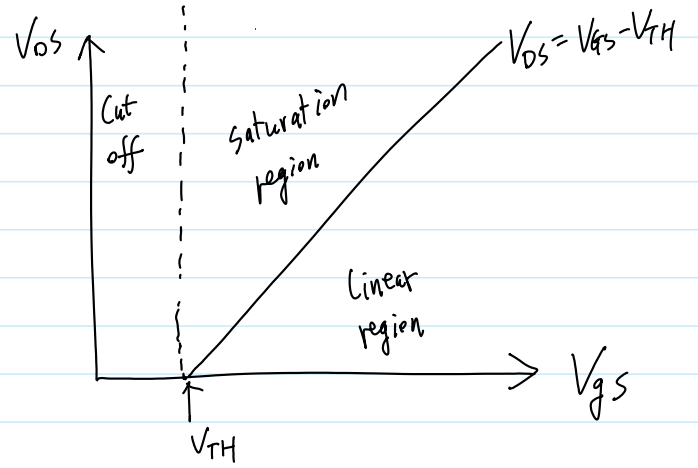 


Experimental I-V

Sunday, June 10, 2012 12:05 PM


Real MOSFET I-V Characteristics

 
We will make this measurement in our lab with two OPAMP's and a shunt resistor for converting current to voltage




CD4007 NMOS

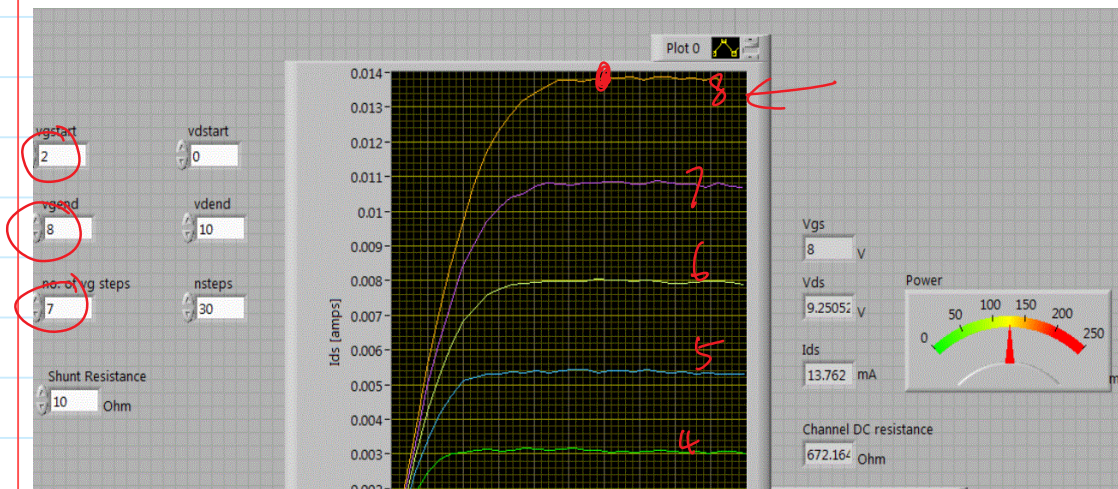Can you estimate V_{TH} ? What about V_{dsat} at $V_{gs}=8V$?



 

Circuit used:

 

Spice simulation and numerical example of I-V

Monday, March 12, 2012 4:42 PM

```
** nmos_id_vd **
```

```
*
```

```
* NI Multisim to SPICE Netlist Export
```

```
* Generated by: GuofuNiu
```

```
* Mon, Sep 26, 2011 10:08:53
```

```
*
```

```
*## Multisim Component V2 ##*
```

```
vV2 d 0 dc 12 ac 0 0
```

```
+ distof1 0 0
```

```
+ distof2 0 0
```

```
*## Multisim Component V1 ##*
```

```
vV1 g 0 dc 12 ac 0 0
```

```
+ distof1 0 0
```

```
+ distof2 0 0
```

```
*## Multisim Component Q1 ##*
```

```
MQ1 d g 0 0 IDEAL_4TEN__TRANSISTORS_VIRTUAL__1__
```

```
1 L=2e-006 W=5e-006 AD=0 AS=0 PD=0 PS=0 NRD=1 NRS=
```

```
1 M=1
```

```
.MODEL IDEAL_4TEN__TRANSISTORS_VIRTUAL__1__1
```

```
NMOS
```

```
+ (
```

```
+ LEVEL= 1
```

$k' \rightarrow k_p$

+ LEVEL= 1
+ VTO= 1
+ KP= 25e-6
~~+ GAMMA= 0.0~~
+ PHI= 0.6
+ LAMBDA= 0.0
+ RS= 0.0
+ RD= 0.0
+ CBD= 0.0
+ CBS= 0.0
+ IS= 1.0e-14
+ PB= 0.8
+ CGSO= 0.0
+ CGDO= 0.0
+ CGBO= 0.0
+ RSH= 0.0
+ CJ= 0.0
+ MJ= 0.5
+ CJSW= 0.0
+ MJSW= 0.5
+ JS= 0.0
+ TOX= 1.0e-7
+ NSS= 0.0
+ TPG= 1.0
+ LD= 0.0
+ UO= 600.0
+ KF= 0.0
+ AF= 1.0
+ FC= 0.5

$K \rightarrow KP$

$25 \mu A/V^2$

$25 \times 10^{-6} A/V^2$

+ TNOM= 27

+)

Multisim Simulation of MOSFET Circuits

```
.MODEL IDEAL_4TEN__TRANSISTORS_VIRTUAL__1__1
```

```
NMOS
```

```
+ (
```

```
+ LEVEL= 1
```

```
+ VTO= 1
```

```
+ KP= 25e-6
```

Note:

the letter "P" in KP does NOT stand for "p-channel"!!!

The "P" stands for "Pri",

KP is the k' parameter in our equation,

Its physical meaning is $\mu * C_{ox}$

$\mu C_{ox}''$

Its unit is A/V^2 .


Use virtual 4 terminal NMOS you can edit model name

(rename) so that you can have different transistor models in one simulation.


VTO is threshold voltage at zero VSB.
Its unit is Volt.

VT depends on substrate bias VSB also, which we will address later.

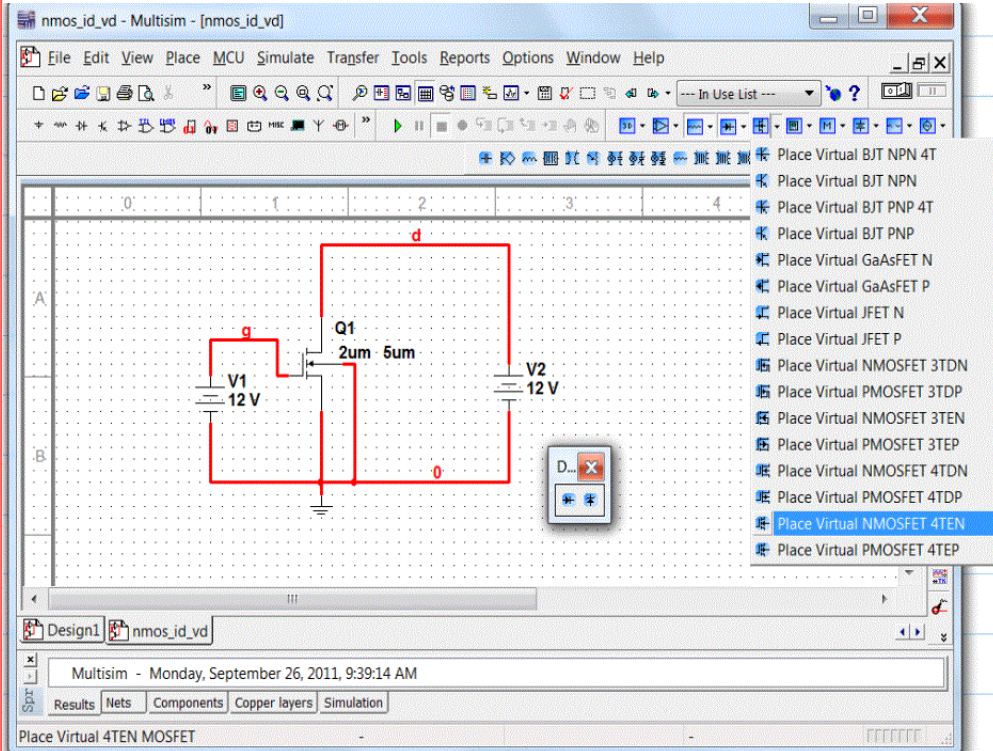Simulate NMOS in Multisim place transistor, wire circuit



 
double click transistor, specify W, L values,
name g, d nodes as we did for bipolar transistor



Spreadsheet data shown for entire design


Net name	Sheet	Color	Trace width min (mil)	Trace width (mil)
0	nmos_id_vd	Default		
d	nmos_id_vd	Default		
g	nmos_id_vd	Default		


"Edit Model" to edit model parameters

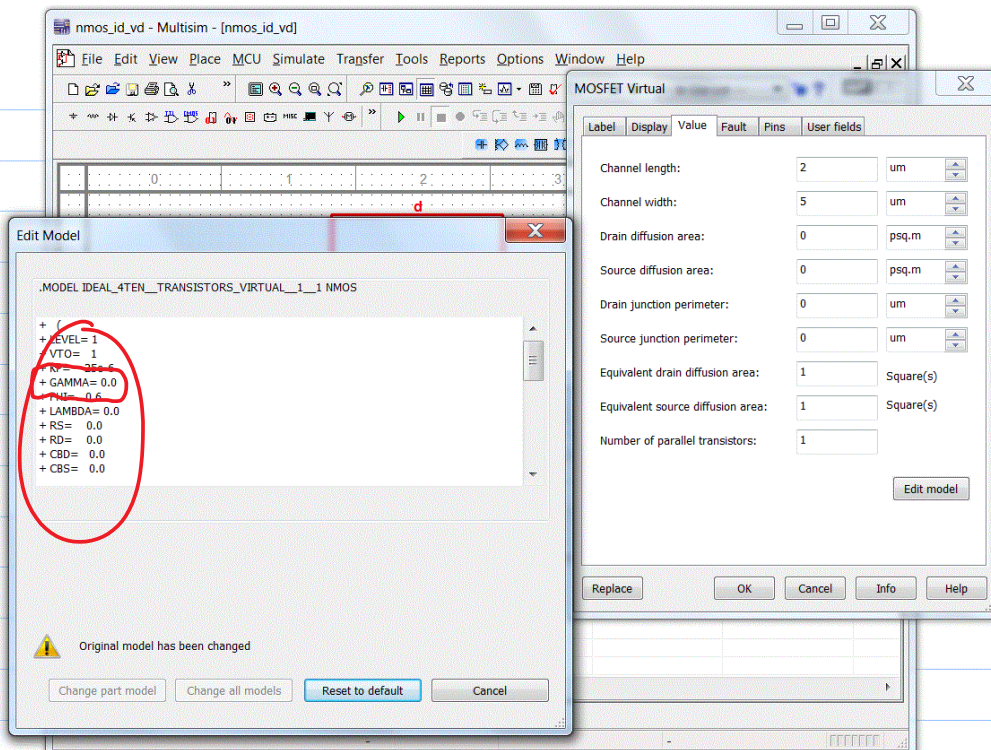

NMOS I_{ds} - V_{ds} (output) Characteristics

 Example: simulate I_{ds} - V_{ds} output curves (varying V_{gs}) for the above transistor in multisim. Can you identify linear and saturation regions on each curve?



 

I_{ds} - V_{ds} curves for different V_{gs}

If $V_{GT} < 0$, device is in cutoff (or off), $I_{DS} = 0$


If $V_{GT} > 0$, device is on. $V_{dsat} = V_{GT}$

If $V_{ds} < V_{dsat}$, $I_{ds} = K_n * (V_{GT} - V_{ds}/2) * V_{ds}$,

I_{ds} saturates at constant value I_{dsat} , when $V_{ds} > V_{dsat}$

Analog amplification is mostly done in Saturation region

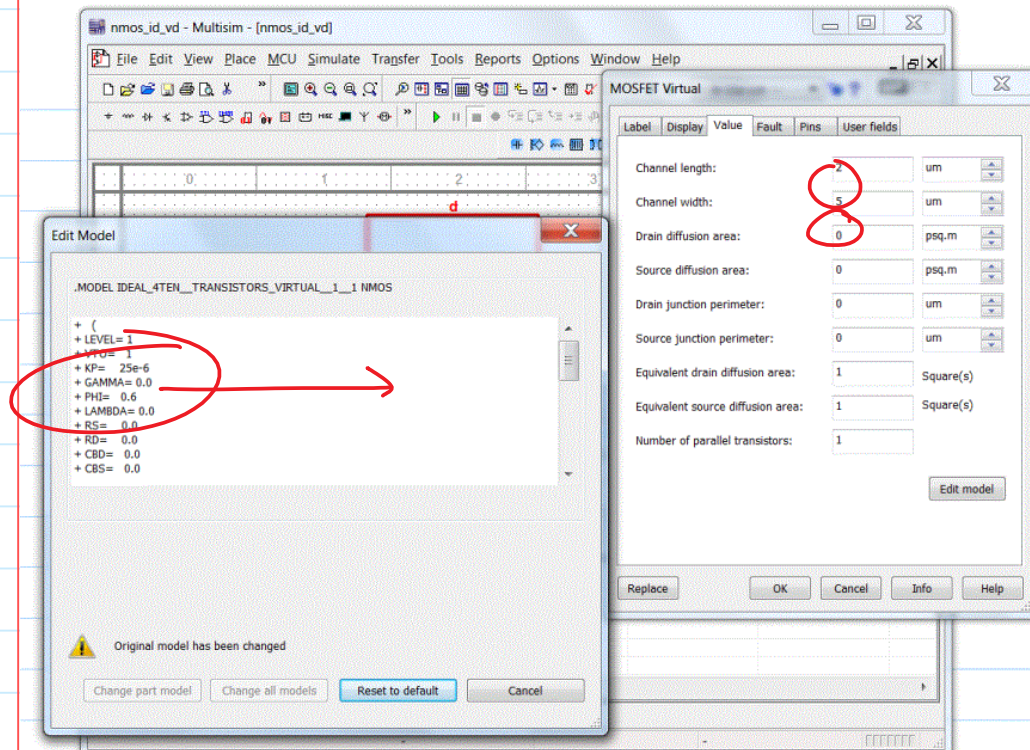Example: compare the simulation above with hand calculation for V_{dsat} and I_{dsat} at $V_{gs}=5V$.



$$V_{GT} = V_{GS} - V_T = 5 - 1 \text{ V} = 4 \text{ V}$$

$$V_{dsat} = V_{GT}$$

$$L = 2 \mu\text{m}$$

$$W = 5 \mu\text{m}$$

$$V_T = 1 \text{ V}$$

$$K' = 25 \times 10^{-6} \frac{\text{A}}{\text{V}^2} = 25 \mu\text{A}/\text{V}^2$$

$$I_{Dsat} = K_n \cdot \frac{V_{GT}^2}{2} = K_n \frac{W}{L} \frac{V_{GT}^2}{2}$$

$$V_{DS} \geq V_{DSAT}$$

// // // //

T - T

$$V_{DSAT} = V_{GT} = V_{GS} - V_{TN}$$


$$I_{DS} = I_{DSAT}$$

$$\begin{aligned} V_{DSAT} &= V_{GS} - V_T \\ &= 5V - 1V \\ &= 4V. \end{aligned}$$


$$\begin{aligned} I &= \frac{K}{2} \cdot V_{GT}^2 \\ &= \frac{K_P \cdot W}{2 \cdot L} \cdot V_{GT}^2 \\ &= \frac{1}{2} \times 25 \times 10^{-6} \frac{A}{V^2} \cdot \frac{5}{2} \cdot \\ &\quad \times (4V)^2 \\ &= 500 \mu A \end{aligned}$$

N-MOS I_{ds} - V_{gs} (transfer) Characteristics

 Example: simulate I_{ds} - V_{gs} curves for various V_{ds} for the above MOSFET. Can you identify the saturation and linear regions on each curve?



DC Transfer Characteristic

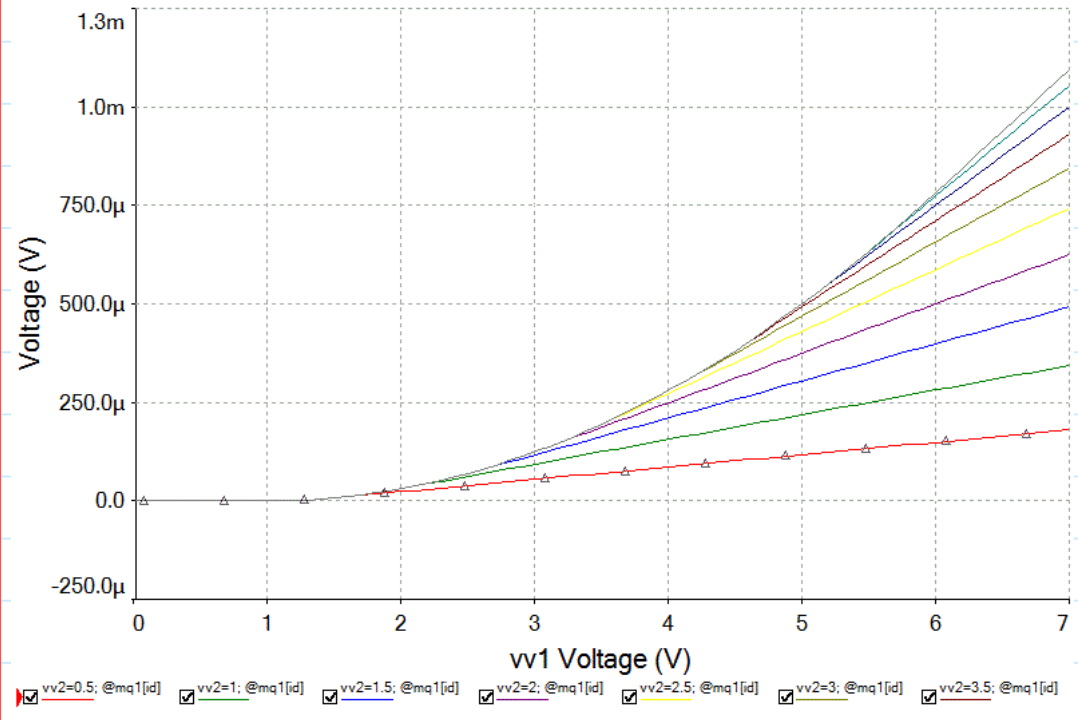


$$V_{DS} = 2V \quad V_{TH} = 1V$$

$$0 < V_{DS} < V_{GS} - V_{TH}$$

Linear


$$V_{GS} > V_{DS} + V_{TH}$$

$$V_{GS} > 3V \text{ Linear}$$

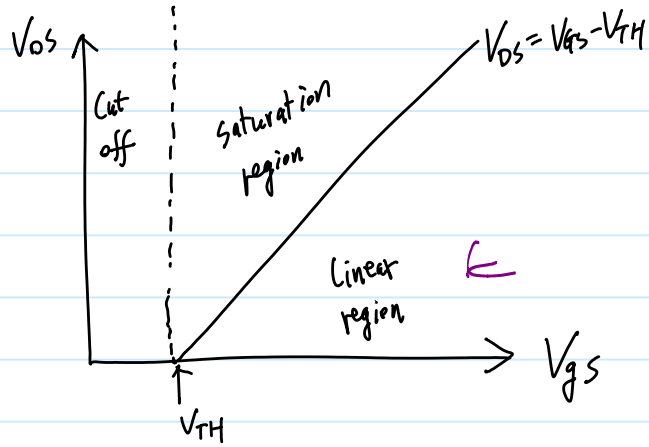

What happens when $V_{DS} > V_{DS,sat}$?

 Past pinchoff, further increases in lateral electric field are absorbed by the creation of a narrow high field region with low carrier density
 (Jn=qnμnE, so if n is small E is large)




Channel-Length Modulation

As v_{DS} increases above v_{DSAT} , length of depleted channel beyond pinch-off point, DL, increases to support additional voltage and actual L decreases.

This "pinched-off" region is high impedance, and a small

 distance can support a large amount of voltage
 i_D increases slightly with v_{DS} instead of being constant
 due to reduction of effective electrical channel length
 (distance over which inversion is high)



$$i_D = \frac{K_n' W}{2 L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$




$K_P = K_n'$
 λ
 W : L : V_{T0} : V_{TN} for $V_{GS} = 0$,
 LAMBDA

Depletion-Mode MOSFET ($V_{TN} < 0$)

NMOS transistors with

Ion implantation process used to form a built-in n-type channel in device to connect source and drain by a resistive channel

 Non-zero drain current for $v_{GS} = 0$, negative v_{GS} required to turn device off.




$$T = \frac{\sqrt{2q\epsilon_s N_a}}{C_{ox}}$$

Non-zero v_{SB} changes threshold voltage, causing substrate sensitivity modeled by


$$V_{TN} = V_{TO} + \gamma \left(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$

V_{TO} = zero substrate bias for V_{TN} (V)

 gamma= body-effect parameter ()
 2phi_F= Fermi potential parameter (V)



Level 1 MOSFET Model in SPICE

 

Typical default values used by SPICE:

$$K_n \text{ or } K_p = 20 \mu\text{A}/\text{V}^2$$

$$\gamma = 0$$

$$\lambda = 0$$

$$V_{TO} = 1 \text{ V}$$

$$\mu_n \text{ or } \mu_p = 600 \text{ cm}^2/\text{V}\cdot\text{s}$$

$$2\Phi_F = 0.6 \text{ V}$$

$$C_{GDO} = C_{GSO} = C_{GBO} = C_{JSW} = 0$$

$$T_{ox} = 100 \text{ nm}$$

Transconductance of a MOS Device

Transconductance relates the change in drain current to a change in gate-source voltage

$$g_m = \left. \frac{di_D}{dv_{GS}} \right|_{Q-pt}$$

Taking the derivative of the expression for the drain current in saturation region,

$$g_m = K_n \frac{W}{L} (V_{GS} - V_{TN}) = \frac{2I_D}{V_{GS} - V_{TN}}$$

Homework on MOSFET, due Wed, Feb 27 class

Monday, March 12, 2012 5:48 PM

1. 4.25 (a)

2. For a MOSFET with the following process parameters $V_{TO}=0.5V$, $K_P=25\mu A/V^2$, $W=4\mu m$, $L=2\mu m$.

(a) Using Multisim, simulate I_{DS} versus V_{DS} curves for $V_{GS}=0$ to $5V$ in $0.5V$ step.

Identify the (V_{dsat}, I_{dsat}) point on each curve with a marker (you can do this by hand on printed plots). V_{DS} range is from 0 to $5V$.

Hint: Use the 4 terminal virtual NMOSFET

(b) Calculate by hand the V_{dsat} and I_{dsat} for $V_{GS}=2.5V$, compare result with simulation from (a).