
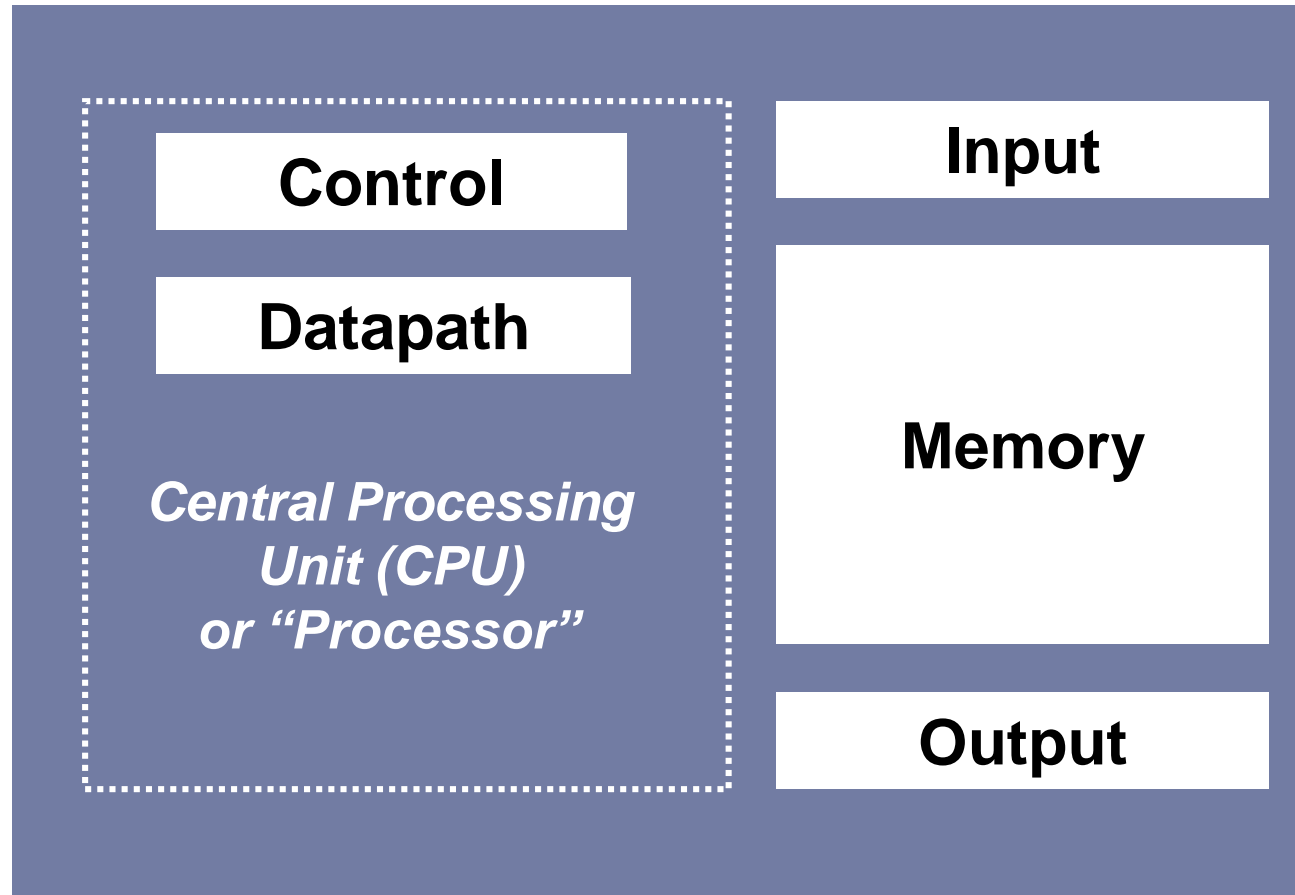


Lecture 6 - Modeling of Memory and Register Files

A typical Computing System

 

Types of Computer Memories



From the cover of:

A. S. Tanenbaum, *Structured Computer Organization, Fifth Edition*, Upper Saddle River, New Jersey: Pearson Prentice Hall, 2006.

Random Access Memory (RAM)

Address bits



**Address
decoder**



**Memory
cell
array**




**Read/write
circuits**



Data bits


Six-Transistor SRAM Cell

 

Dynamic RAM (DRAM) Cell



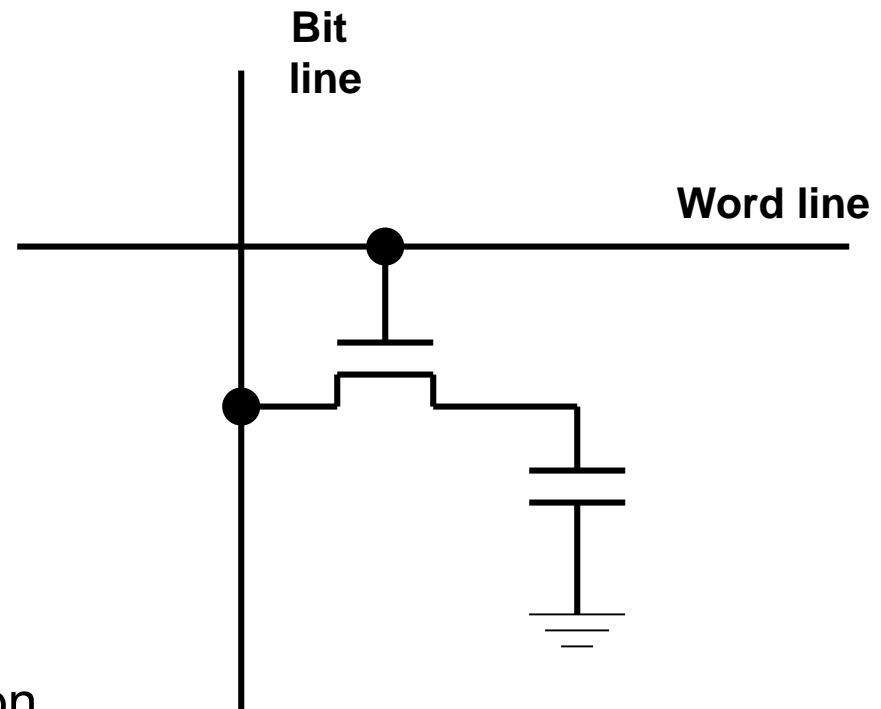“Single-transistor DRAM cell”
Robert Dennard’s 1967 invention



Electronic Memory Devices

Memory technology	Typical access time	\$ per GiB in 2012
SRAM semiconductor memory	0.5–2.5 ns	\$500–\$1000
DRAM semiconductor memory	50–70 ns	\$10–\$20
Flash semiconductor memory	5,000–50,000 ns	\$0.75–\$1.00
Magnetic disk	5,000,000–20,000,000 ns	\$0.05–\$0.10

For more on memories:


Semiconductor Memories: A Handbook of Design, Manufacture and Application, by Betty Prince, Wiley 1996.

Emerging Memories: Technologies and Trends, by Betty Prince, Springer 2002.

DRAM Evolution


Year introduced	Chip size	\$ per GiB	Total access time to a new row/column	Average column access time to existing row
1980	64 KiB	\$1,500,000	250 ns	150 ns
1983	256 KiB	\$500,000	185 ns	100 ns
1985	1 MeB	\$200,000	135 ns	40 ns
1989	4 MeB	\$50,000	110 ns	40 ns
1992	16 MeB	\$15,000	90 ns	30 ns
1996	64 MeB	\$10,000	60 ns	12 ns
1998	128 MeB	\$4,000	60 ns	10 ns
2000	256 MeB	\$1,000	55 ns	7 ns
2004	512 MeB	\$250	50 ns	5 ns
2007	1 GiB	\$50	45 ns	1.25 ns
2010	2 GiB	\$30	40 ns	1 ns
2012	4 GiB	\$1	35 ns	0.8 ns

Classical RAM Organization (~Square)

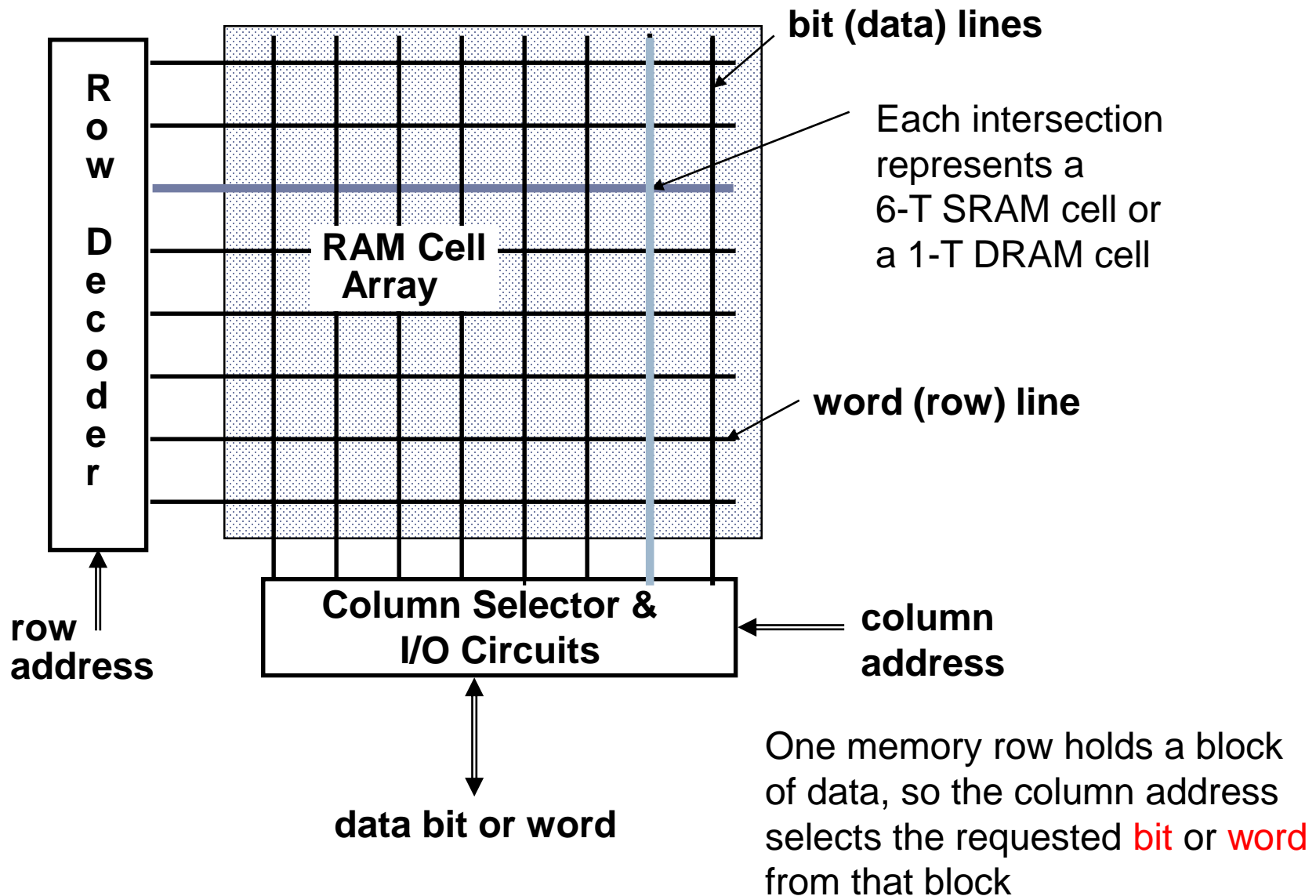



Classical DRAM Organization (~Square Planes)

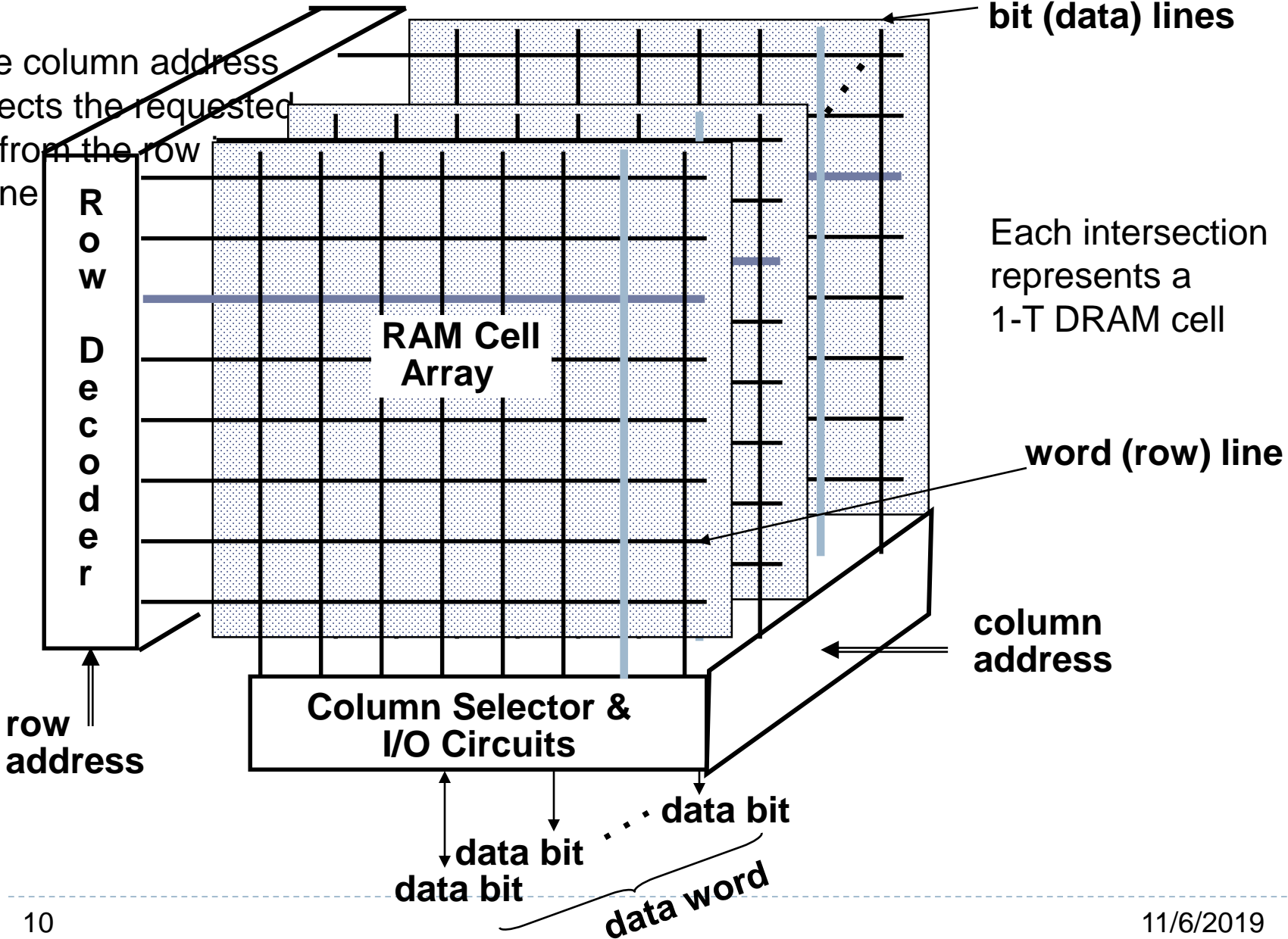The column address selects the requested bit from the row plane





Classical DRAM Operation

  - DRAM Organization:
 - N rows x N column x M-bit
 - Read or Write M-bit at a time
 - Each M-bit access requires a RAS / CAS cycle





Page Mode DRAM Operation

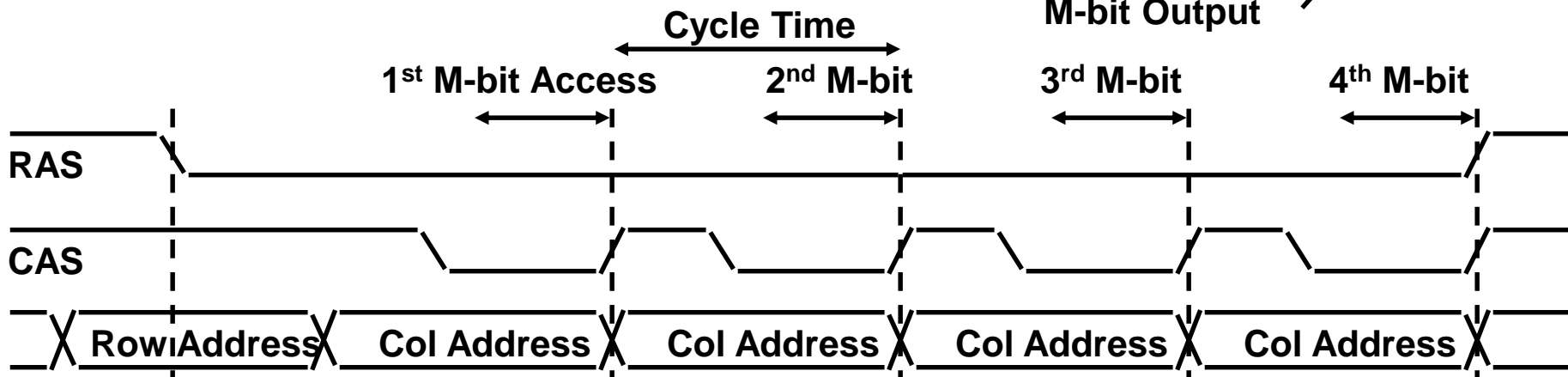 - Page Mode DRAM
 - $N \times M$ SRAM to save a row
- After a row is read into the SRAM “register”
 - Only CAS is needed to access other M-bit words on that row
 - RAS remains asserted while CAS is toggled



Synchronous DRAM (SDRAM) Operation

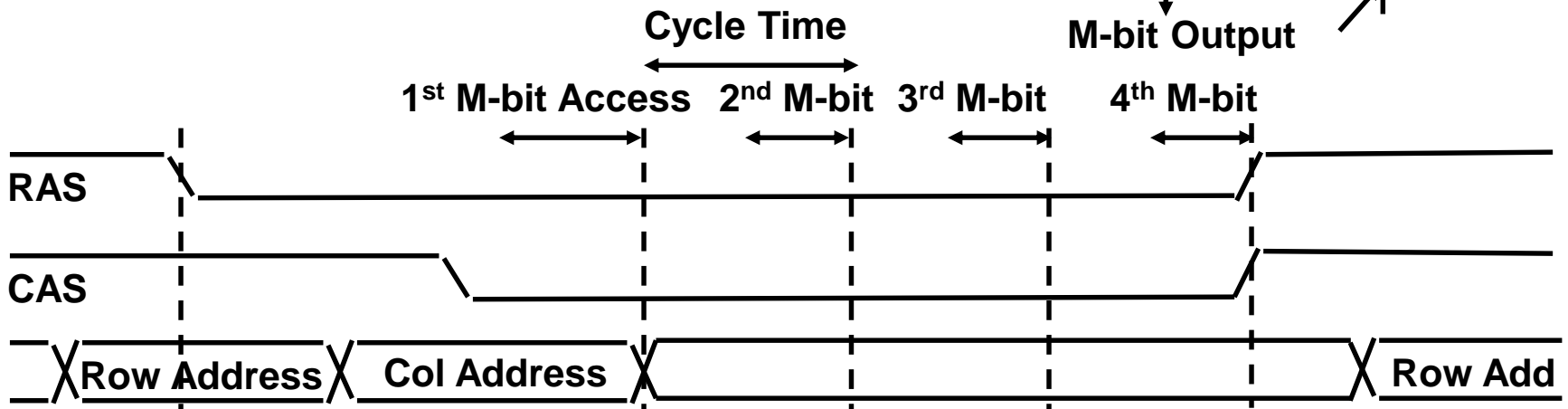
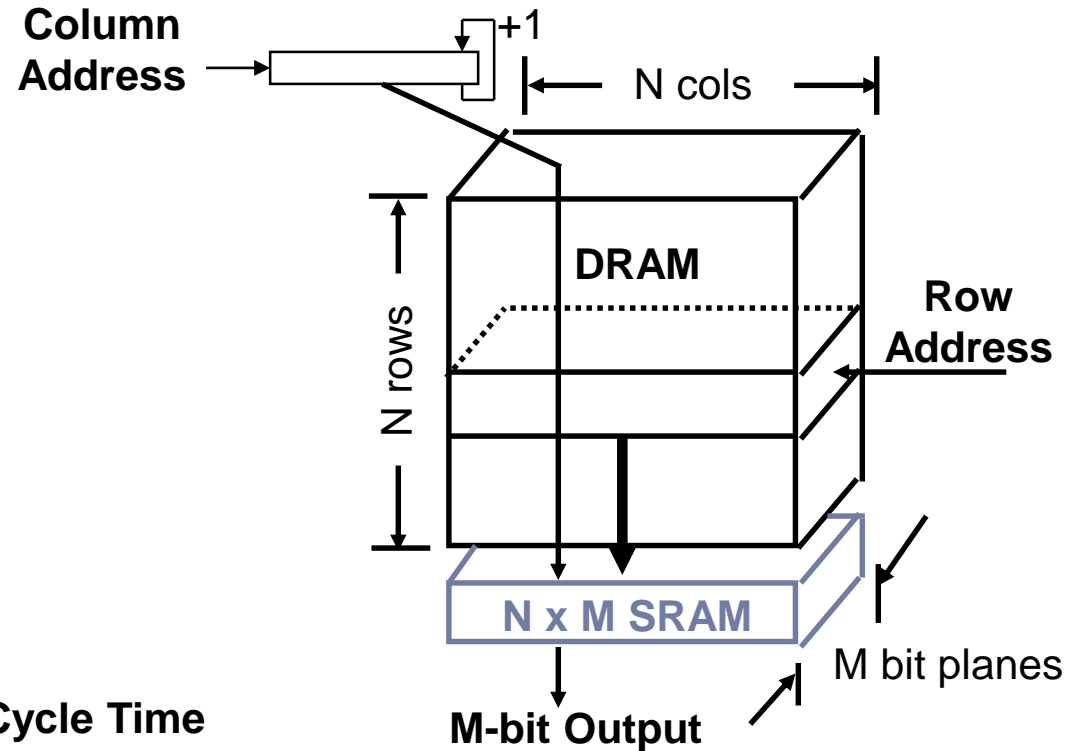
- After a row is read into the SRAM register
 - Inputs CAS as the starting “burst” address along with a burst length
 - Transfers a burst of data from a series of sequential addresses within that row
 - A **clock** controls transfer of successive words in the burst – 300MHz in 2004



Other SDRAM Architectures

■ Double Data Rate SDRAMs – DDR-SDRAMs


- Double data rate because they transfer data on both the rising and falling edge of the clock
 - Most widely used form of SDRAMs
- For DDR memory, $2n$ prefetch architecture means
 - Internal bus width is twice of external bus width
 - Hence, internal column access freq can be half of external data rate
- For users, $2n$ prefetch means that data access occurs in pairs
 - A single READ fetches two data words
 - A single WRITE, two data words must be provided

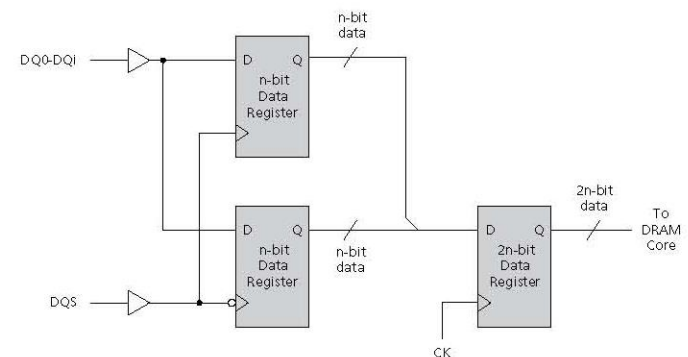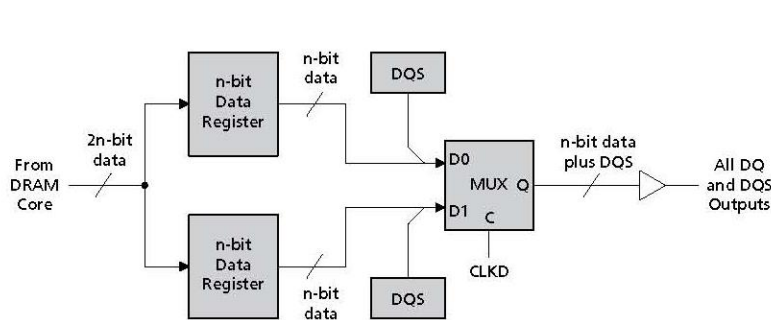

14 Figure 1. Simplified Block Diagram of 2n-Prefetch READ

Figure 2. Simplified Block Diagram of 2n-Prefetch WRITE


Other SDRAM Architectures- Cont.

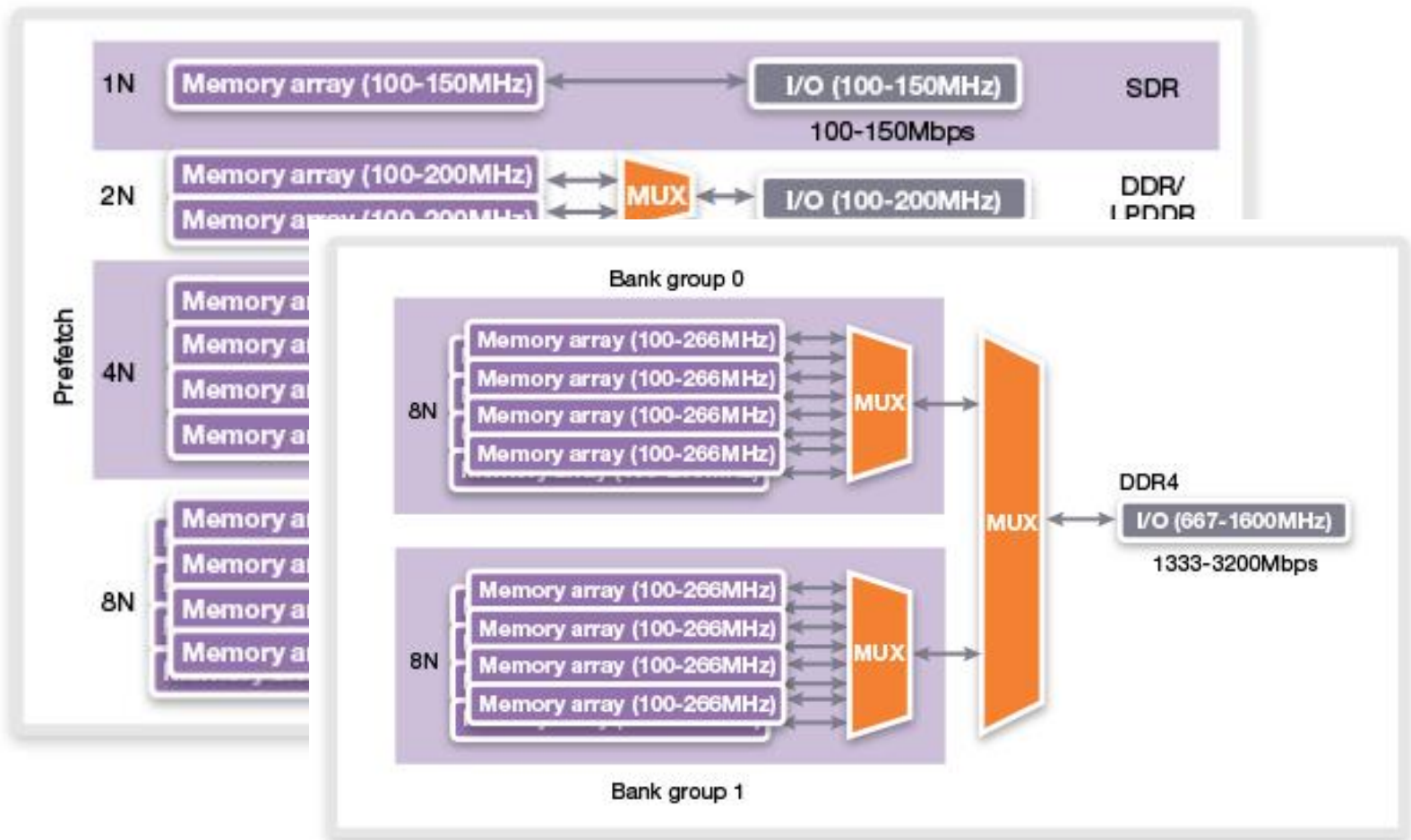

Memory Synthesis

- Approaches:
 - Random logic using flip-flops or latches
 - Register files in data paths
 - RAM standard components
 - RAM compilers
- Computer “register files” are often just multi-port RAMs
 - ARM CPU: 32-bit registers R0-R15 => 16 x 32 RAM
 - MIPS CPU: 32-bit registers R0-R31 => 32 x 32 RAM
- Communications systems often use dual-port RAMs as transmit/receive buffers
 - FIFO (first-in, first-out RAM)

Basic memory/register array

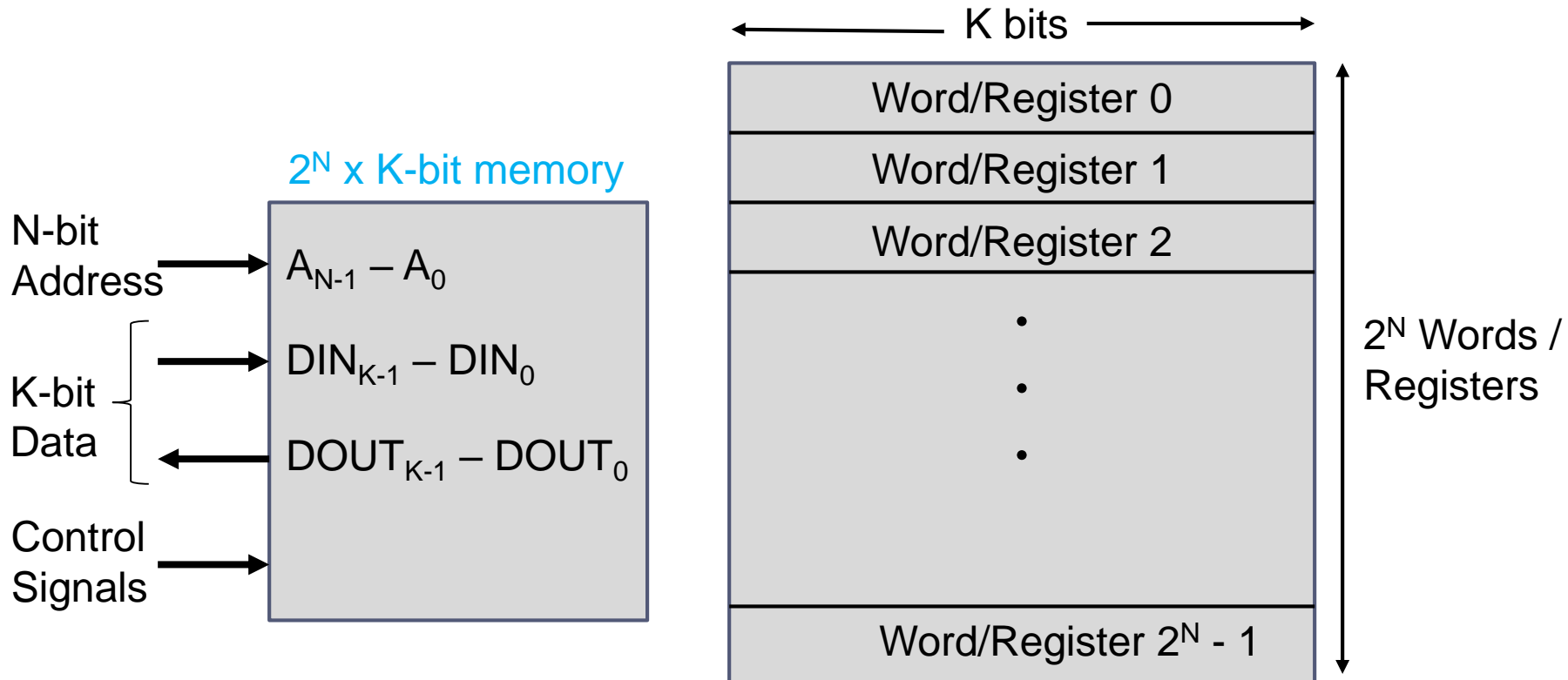


-- $2^N \times K\text{-bit memory}$ VHDL struture

signal MemArray: array (0 to $2^{**}N - 1$) of std_logic_vector(K-1 downto 0);

-- ARM register file is 16 32-bit registers

signal ARMregisterFile: array (0 to 15) of std_logic_vector(31 downto 0);

Example: 4 x n-bit register file

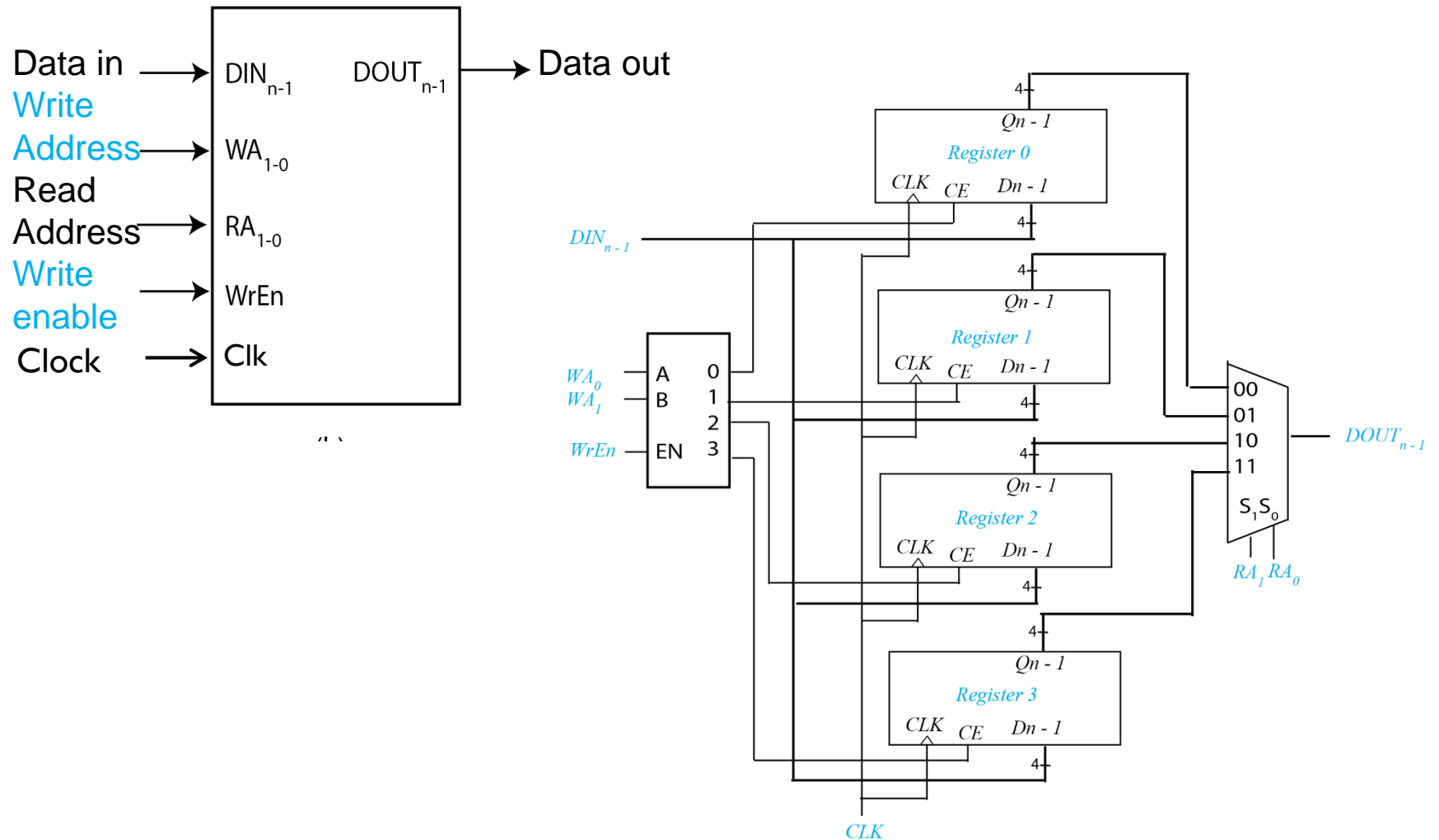

Technology-independent RAM Models


-- N x K RAM is 2-dimensional array of N K-bit words

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_numeric_std.all;
```

entity RAM is

```
    generic (K: integer:=8;           -- number of bits per word  
             W: integer:=8);         -- number of address bits; N = 2^W  
    port (  
        WR:    in std_logic;         -- active high write enable  
        ADDR: in std_logic_vector (W-1 downto 0); -- RAM address  
        DIN:   in std_logic_vector (K-1 downto 0); -- write data  
        DOUT:  out std_logic_vector (K-1 downto 0)); -- read data
```

end entity RAM;

 

RAM Models in VHDL

architecture RAMBEHAVIOR of RAM is

```
    subtype WORD is std_logic_vector ( K-1 downto 0);    -- define size of WORD
    type MEMORY is array (0 to 2**A-1) of WORD;        -- define size of MEMORY
    signal RAM256: MEMORY;                            -- RAM256 as signal of type MEMORY
```

begin

```
    process (WR, DIN, ADDR)
```

```
        variable RAM_ADDR_IN: natural range 0 to 2**W-1; -- translate address to integer
```

```
    begin
```

```
        RAM_ADDR_IN := to_integer(UNSIGNED(ADDR));        -- convert address to integer
```

```
        if (WR='1') then                                  -- write operation to RAM
```

```
            RAM256 (RAM_ADDR_IN) <= DIN ;
```

```
        end if;
```

```
        DOUT <= RAM256 (RAM_ADDR_IN);                    -- continuous read operation
```

```
    end process;
```

```
end architecture RAMBEHAVIOR;
```

Multi-port RAM (two parallel outputs):

```
    DOUT1 <= RAM256(to_integer(UNSIGNED(ADDR1)));
```

```
    DOUT2 <= RAM256(to_integer(UNSIGNED(ADDR2)));
```

Initialize RAM at start of simulation

```
process (WR, DIN, ADDR)
```

```
  variable RAM_ADDR_IN: natural range 0 to 2**W-1; -- to translate address to integer
```

```
  variable STARTUP: boolean := true; -- temp variable for initialization
```

```
begin
```

```
  if (STARTUP = true) then -- for initialization of RAM during start of simulation
```

```
    RAM256 <= (0 => "00000101", -- initializes first 4 locations in RAM
```

```
              1 => "00110100", -- to specific values
```

```
              2 => "00000110", -- all other locations in RAM are
```

```
              3 => "00011000", -- initialized to all 0s
```

```
              others => "00000000");
```

```
    DOUT <= "XXXXXXXXX"; -- force undefined logic values on RAM output
```


```
    STARTUP :=false; -- now this portion of process will only execute once
```

```
  else
```

```
    -- "Normal" RAM operations
```

RAM with bidirectional data bus

FIGURE 8-14: Block Diagram of Static RAM

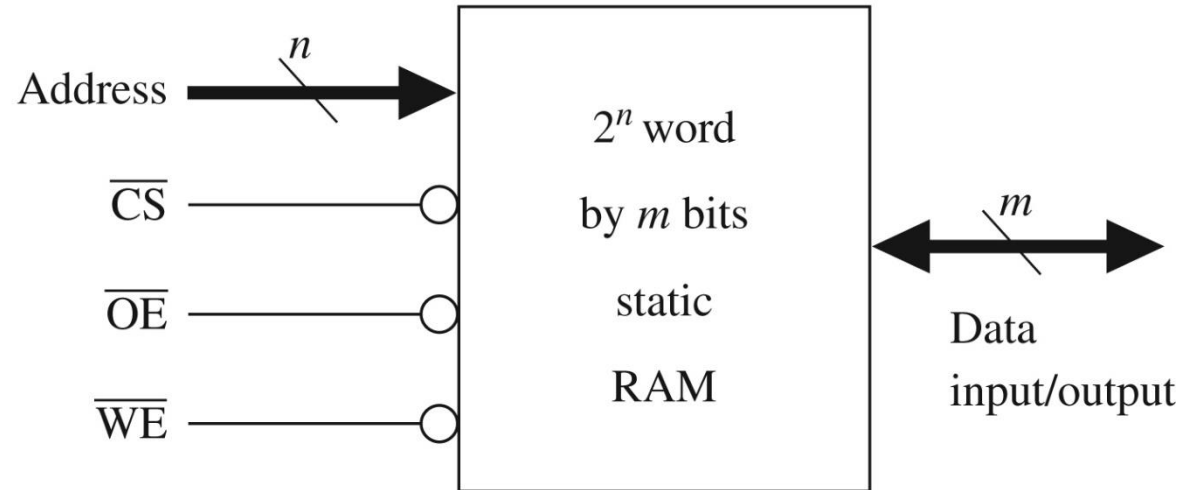

**TABLE 8-7:
Truth Table for
Static RAM**


\overline{CS}	\overline{OE}	\overline{WE}	Mode	I/O pins
H	X	X	not selected	high-Z
L	H	H	output disabled	high-Z
L	L	H	read	data out
L	X	L	write	data in

Single-port distributed RAM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity rams_04 is
  port (
    clk : in std_logic;
    we : in std_logic;
    a : in std_logic_vector(5 downto 0);
    di : in std_logic_vector(15 downto 0);
    do : out std_logic_vector(15 downto 0));
end rams_04;
```
 
```
architecture syn of rams_04 is
  type ram_type is array (63 downto 0) of std_logic_vector (15 downto 0);
  signal RAM : ram_type;
begin
  process (clk)
  begin
    if (clk'event and clk = '1') then
      if (we = '1') then
        RAM(conv_integer(a)) <= di;
      end if;
    end if;
  end process;
  do <= RAM(conv_integer(a));
end syn;
```



From Xilinx "Synthesis and Simulation Design Guide"

FIGURE 6-18: Behavioral VHDL Code That Typically Infers LUT-Based Memory

```
Library IEEE;
use IEEE.numeric_bit.all;

entity Memory is
  port(Address: in unsigned(6 downto 0);
        CLK, MemWrite: in bit;
        Data_In: in unsigned(31 downto 0);
        Data_Out: out unsigned(31 downto 0));
end Memory;

architecture Behavioral of Memory is
  type RAM is array (0 to 127) of unsigned(31 downto 0);
  signal DataMEM: RAM; -- no initial values
begin
  process(CLK)
  begin
    if CLK'event and CLK = '1' then
      if MemWrite = '1' then
        DataMEM(to_integer(Address)) <= Data_In; -- Synchronous Write
      end if;
    end if;
  end process;

  Data_Out <= DataMEM(to_integer(Address)); -- Asynchronous Read
end Behavioral;
```


Block RAM inferred

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity rams_01 is
  port (
```

```
    clk : in std_logic;
    we : in std_logic;
    en : in std_logic;
    addr : in std_logic_vector(5 downto 0);
    di : in std_logic_vector(15 downto 0);
    do : out std_logic_vector(15 downto 0));
```

```
end rams_01;
```

```
architecture syn of rams_01 is
```

```
  type ram_type is array (63 downto 0) of std_logic_vector (15 downto 0);
  signal RAM: ram_type;
```

```
begin
```

```
  process (clk)
  begin
```

```
    if clk'event and clk = '1' then
```

```
      if en = '1' then
```

```
        if we = '1' then
```

```
          RAM(conv_integer(addr)) <= di;
```

```
        end if;
```


```
        do <= RAM(conv_integer(addr)); -- read-first operation
```

```
      end if;
```

```
    end if;
```

```
  end process;
```

```
end syn;
```

 

From Xilinx “Synthesis and Simulation Design Guide”


FIGURE 6-19: Behavioral VHDL Code That Typically Infers Dedicated Memory

```
Library IEEE;
use IEEE.numeric_bit.all;

entity Memory is
  port(Address: in unsigned(6 downto 0);
        CLK, MemWrite: in bit;
        Data_In: in unsigned(31 downto 0);
        Data_Out: out unsigned(31 downto 0));
end Memory;

architecture Behavioral of Memory is
  type RAM is array (0 to 127) of unsigned(31 downto 0);
  signal DataMEM: RAM; -- no initial values
begin
  process(CLK)
  begin
    if CLK'event and CLK = '1' then
      if MemWrite = '1' then
        DataMEM(to_integer(Address)) <= Data_In; -- Synchronous Write
      end if;
      Data_Out <= DataMEM(to_integer(Address)); -- Synchronous Read
    end if;
  end process;
end Behavioral;
```

Register File in Verilog

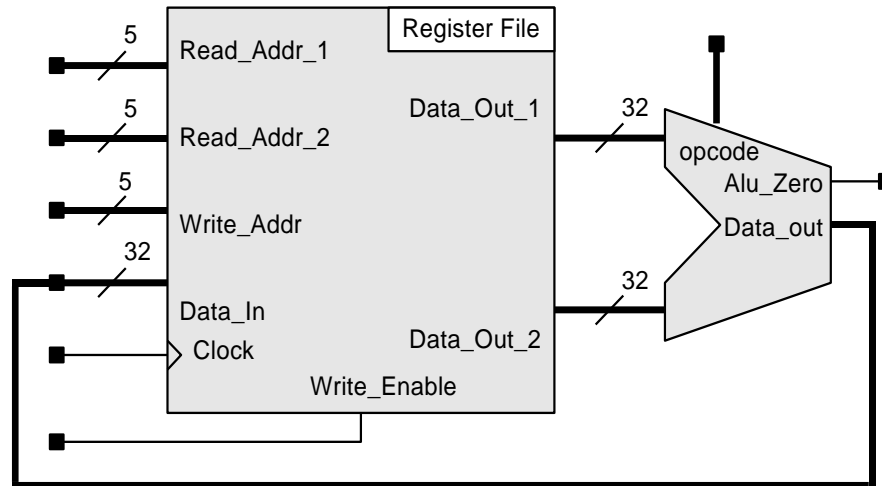


```
module Register_File (Data_Out_1,Data_Out_2,Data_in,  
                    Read_Addr_1,Read_Addr_2,Write_Addr,Write_Enable,Clock);  
output [31: 0]    Data_Out_1, Data_Out_2;  
input  [31: 0]    Data_in;  
input  [4: 0]     Read_Addr_1, Read_Addr_2, Write_Addr;  
input  Write_Enable, Clock;  
reg    [31: 0]    Reg_File [31: 0];    // 32bit x32 word memory declaration  
  
assign Data_Out_1 = Reg_File[Read_Addr_1];  
assign Data_Out_2 = Reg_File[Read_Addr_2];  
always @ (posedge Clock) begin  
    if (Write_Enable) Reg_File [Write_Addr] <= Data_in;  
end  
endmodule
```

“Concept of Memory” in Verilog

- Memory
 - Declaration an array of words
 - E.g. `reg [31:0] data_out; // one 32-bit word`
`reg [31:0] Reg_file [31:0]; // 32x32 bit word memory`
- Verilog does not support 2-dimensional array
 - However, a word in a Verilog memory can be addressed directly
 - E.g., `Reg_file [12]`
 - A cell bit in a word can also be addressed indirectly by first loading the word into a buffer register then addressing the bit of the word
 - E.g. `Data_out = Reg_file [12];`
`Data_out [1:0]`
- Decoder are synthesized automatically by synthesis tool in `Reg_file[]` to decode the address which locates a specific register

Bus Interface


■ Unidirectional Bus

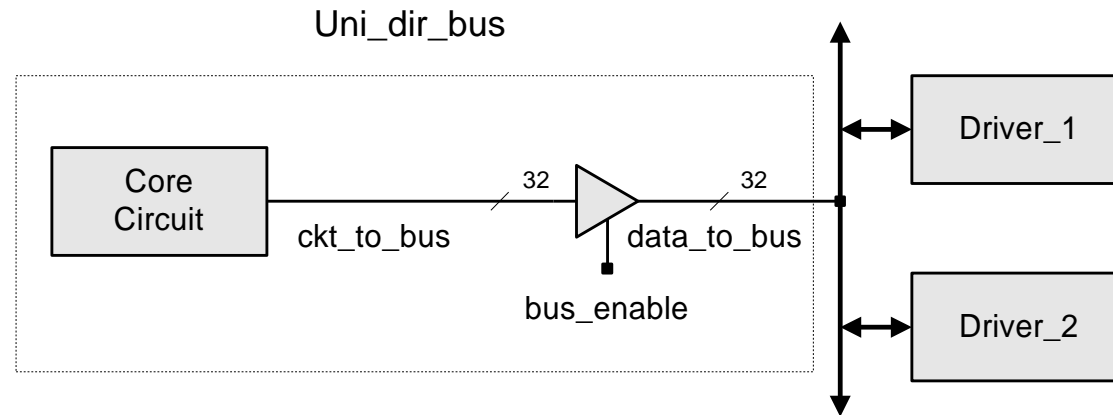

```
module Uni_dir_bus ( data_to_bus, bus_enable);  
Input          bus_enable;  
output [31: 0]  data_to_bus;  
reg [31: 0]    ckt_to_bus;  
assign data_to_bus = (bus_enable)? ckt_to_bus: 32'bz;  
// Description of core circuit goes here to drive ckt_to_bus  
endmodule
```

Bus Interface

■ Bidirectional Bus

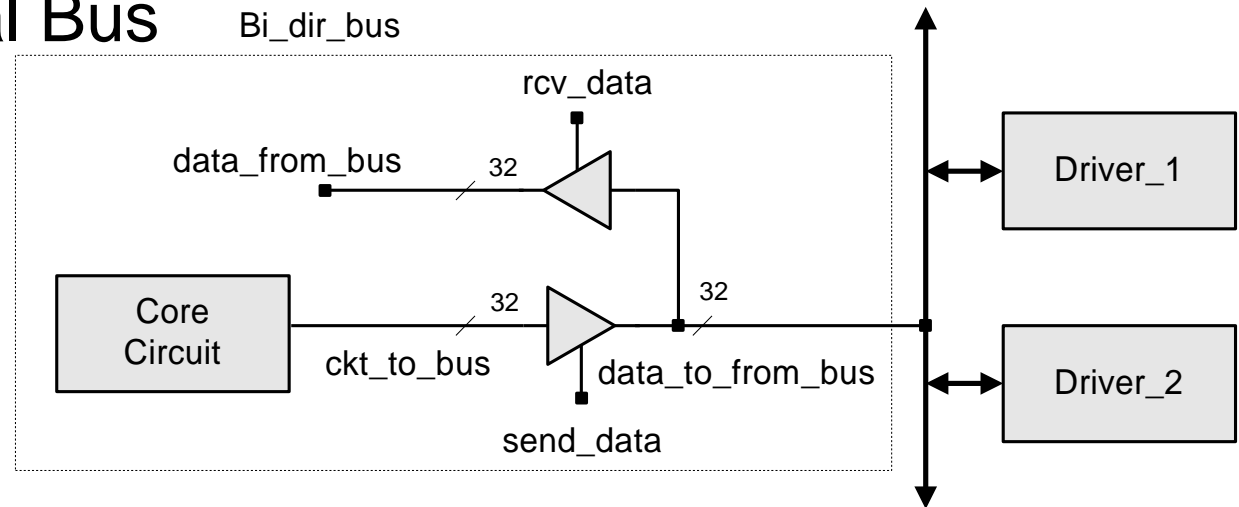

```
module Bi_dir_bus (data_to_from_bus, send_data, rcv_data);  
inout [31: 0] data_to_from_bus;  
Input send_data, rcv_data;  
wire [31: 0] ck_t_to_bus;  
wire [31: 0] data_to_from_bus, data_from_bus;  
assign data_from_bus = (rcv_data)? data_to_from_bus: 32'bz;  
assign data_to_from_bus = (send_data)? ck_t_to_bus: data_to_from_bus;  
// Behavior using data_from_bus and generating  
// ck_t_to_bus goes here  
endmodule
```